

AN-1178 Practical Use of GreenPAK™ Pulse Counter: Frequency Counter, Thermometer, Voltmeter

This application note is created to show some of the capabilities of digital and analog macrocells within the SLG46533V GreenPAK IC.

Part 1 describes how to build a frequency counter capable to measure frequency from 1 Hz to tens of MHz. Easy to scale and output up to eight 7-segment displays.

Part 2 describes how to turn a frequency counter into a thermometer using an external NTC resistor.

It is also possible to measure a DC voltage. Such a voltmeter is described in Part 3.

Part 1. Frequency Counter

The GreenPAK frequency counter works by using a counter which accumulates the number of pulses occurring within a specific period of time, 1 second for example. After this preset period, known as "Gate Time", the value in the counter is transferred to a display and the counter is reset to zero. It is easy to build such a counter using internal blocks of the SLG46533V, see figure 1. It consists of four DFFs connected in series in order to get a binary code (inverted) of counted pulses on their four outputs - see Table 1.

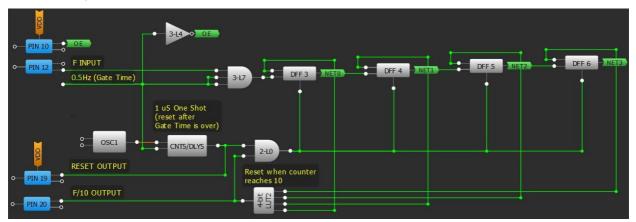


Figure 1. Frequency counter 0...9 Hz, Part of GreenPAK Designer Project

Count	NET3	NET2	NET1	NET0	Binary Code
0	1	1	1	1	0000
1	1	1	1	0	0001
2	1	1	0	1	0010
3	1	1	0	0	0011
4	1	0	1	1	0100
5	1	0	1	0	0101
6	1	0	0	1	0110
7	1	0	0	0	0111
8	0	1	1	1	1000
9	0	1	1	0	1001
10 (Reset)	0	1	0	1	1010

Table 1. Pulse Counter Truth Table

This pulse counter is capable of counting from 0 to 15, but only 0 to 9 is needed, so the 4-Bit LUT is used to reset count to 0 when the counter reaches 10 - see Figure 2 for LUT settings. The reset signal appears once in ten pulses and can be used as an input signal of F/10 for the next (decade) counter and so on.



	4-bit LUT2							
IN3	IN2	IN1	IN0	OUT				
0	0	0	0	1				
0	0	0	1	1				
0	0	1	0	1				
0	0	1	1	1				
0	1	0	0	1				
0	1	0	1	0				
0	1	1	0	1				
0	1	1	1	1				
1	0	0	0	1				
1	0	0	1	1				
1	0	1	0	1				
1	0	1	1	1				
1	1	0	0	1				
1	1	0	1	1				
1	1	1	0	1				
1	1	1	1	1				

Figure 2. Reset LUT settings

To use this scheme as an accurate frequency counter, an accurate gate time is needed. For this purpose, a crystal oscillator is used. Its frequency is divided down to 0.5 Hz. For timing diagram refer to Figure 3.

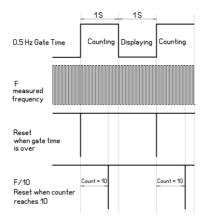


Figure 3. Timing Diagram

In order to display the counted value "The binary to 7 segment" decoder is needed, which is easy to build using LUTs within the GreenPAK. See Figure 4 below. This decoder is used for common cathode 7 segment display.

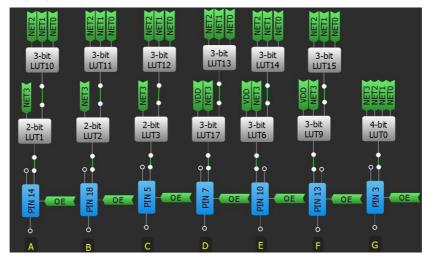


Figure 4. Binary to 7 Segment Decoder, Part of GreenPAK Designer Project

The LUTs must be configured according to Pulse Counter Truth Table so the display indicates the number of counted pulses. See Figures 5 and 6 for example of configuration of the LUTs for segments A and B respectively.



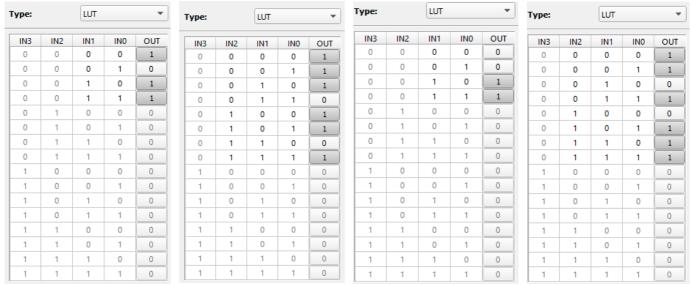


Figure 5. Segment A 2-bit LUT and 3-bit LUT configuration

Figure 6. Segment B 2-bit LUT and 3-bit LUT configuration

Since there are only three 4-bit LUTs, for segments A, B, C, D, E and F, two LUTs are combined in order to create a 4-bit LUT logical equivalent.

All inputs are configured as Digital input with Schmitt trigger and outputs as Digital output 2x push pull. See Figure 7 for full GreenPAK Designer project of the first stage of the frequency counter.

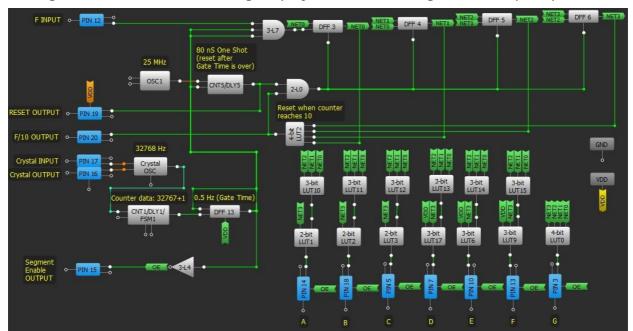


Figure 7. Frequency Counter First Stage, GreenPAK Designer Project

To ensure stability and high counting accuracy, the Crystal Oscillator is used. It's frequency of 32768 Hz is divided by 32768 using CNT/DLY in counter mode. The counter provides short pulses with a frequency of 1 Hz which go to DFF to be divided by 2, there for creating a 0.5 Hz Gate Time, see Figure 7 and 9. The accuracy depends only on the crystal itself and cannot be higher than 1 LSB.

The next (and all following) stages of the freq. counter are much simpler and require fewer macrocells, see Figure 8.



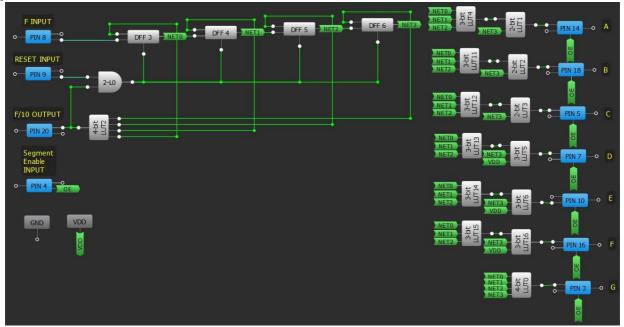


Figure 8. Frequency Counter Second and All Following Stages, GreenPAK Designer Project

This schematic allows to connect in series up to 8 stages allowing to measure frequency up to tens of Mega Hertz. See full device schematic diagram in Figure 9.

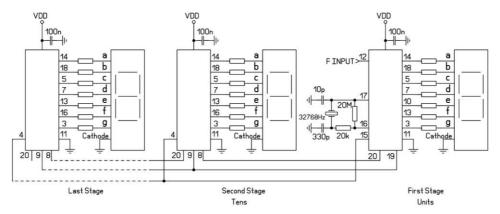


Figure 9. Frequency Counter Full Schematic Diagram



Part 2. Thermometer

It is easy to turn a frequency counter into the thermometer using a temperature dependent oscillator. The easiest way is to use a Schmitt inverter as RC oscillator with NTC resistor. See schematic diagram in Figure 10.

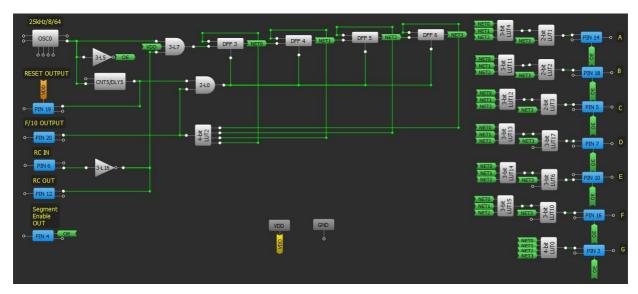


Figure 10. Thermometer Schematic Diagram, GreenPAK Designer Project

This device does not require any external oscillators. An internal RC OSC (25k/8/64=48.8Hz) is used as a Gate Time generator. All other parts of the project are the same as in freq. counter, see Figures 4 to 6 and 8. For full schematic diagram refer to Figure 11.

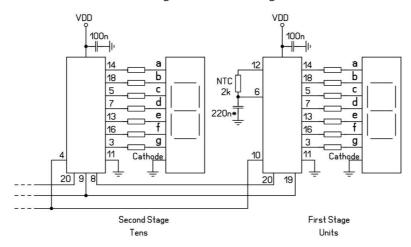


Figure 11. Full Thermometer Schematic Diagram

This thermometer is able to measure and indicate temperature in a range of 0°C to 99°C. However, it is easy to add one more stage and increase the resolution up to 0.1°C. This requires to increase ten times the frequency of the measuring oscillator by using a capacitor with ten times less capacitance (22nF). Also, it should be noted that the device needs a calibration before use. Using a precision thermometer, adjust readings by selecting a frequency setting capacitor. Despite using an internal oscillator, the accuracy of the 3-digit thermometer is better than 0.5°C, which is more than enough to measure room temperature.



Part 3. Voltmeter

It is also possible to modify the frequency counter into a voltmeter. Unlike previous devices the voltmeter uses two fixed frequencies with a difference of 1024. Both clocks are formed from the internal 25 kHz oscillator. The first high frequency clock 50 kHz is formed by One Shot CNT/DLY with settings as follows:

Mode: One shot Counter data: 249 Edge select: Both

Output polarity: Non-inverted

Clock: OSC1 CLK

(OSC1 must be set to Force Power On)

The second low frequency clock is formed by dividing 25 kHz by 512 using two dividers: OUT0 second divider by 64 and Pipe Delay set to divide by 8 (OUT0 PD num: 4 and OUT1 PD num: 4).

The low frequency clock is used to form a PWM signal, which will be used as a Gate Time to count pulses of the high frequency clock, see Figure 13.

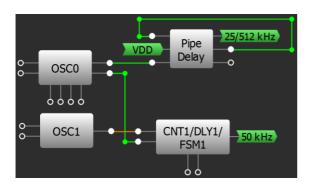


Figure 12. Voltmeter's Clock Schematic Diagram, part of GreenPAK Designer Project

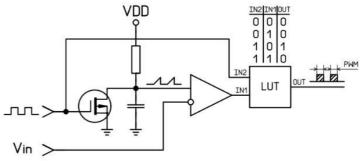


Figure 13. PWM



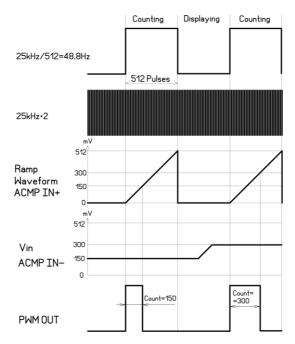


Figure 14. Voltmeter timing diagram

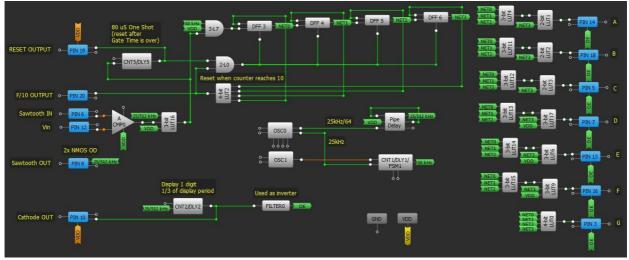


Figure 15. Voltmeter First Stage Schematic Diagram, GreenPAK Designer Project

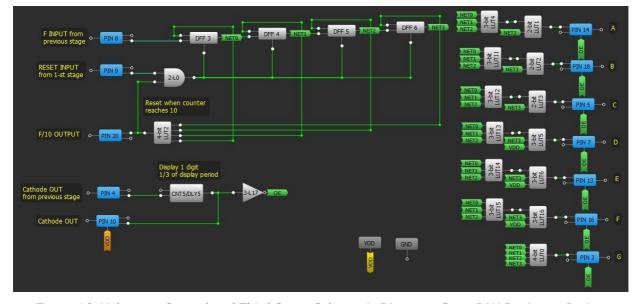


Figure 16. Voltmeter Second and Third Stage Schematic Diagram, GreenPAK Designer Project



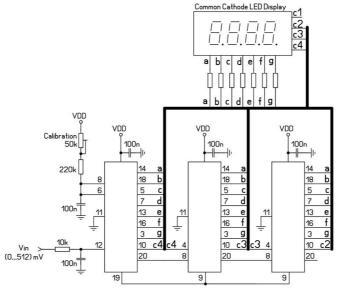


Figure 17. Voltmeter Full Schematic Diagram

This device uses three digits of the 4-digit Common Cathode 7-segment LED Display. Unlike previous projects this display cannot display all digits at once, they must be switched on alternately. For this purpose, the display period (10 mS) is divided in three parts for each digit. Each stage of the device has a One Shot counter that generates a 3.24 mS pulse to display its digit, refer to Figures 15 and 16. Each next One Shot counter is triggered by the previous one, see Figures 18 and 19 for settings.

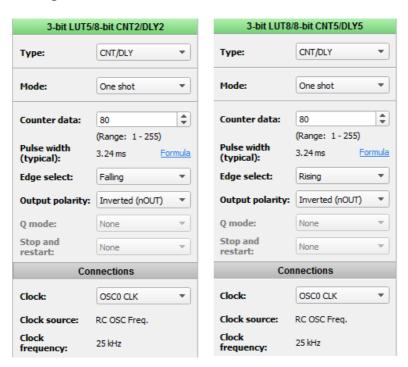


Figure 18. First Stage One Shot Settings

Figure 19. Second and Third Stage One Shot Settings



This Voltmeter is designed to measure voltage in a range of 0 to 512 mV. Since this project is just a demonstration of GreenPAK's capabilities, some improvements can be made. This device uses the Ramp Waveform as a voltage reference (see Figure 13), therefore the accuracy depends on VDD and external components (resistors and the capacitor). To improve accuracy, a stabilized current source must be used instead of resistors, Its current and the capacitance of the capacitor must be selected so the amplitude of the Ramp Waveform corresponds to max number of pulses that can be counted, in this case 512 (see Figure 14). Also, it is recommended to use a film capacitor due to higher temperature stability. The fluctuation of the internal oscillator has no influence on the accuracy of the voltmeter because both frequencies are taken from the same oscillator. This voltmeter can be used in low precision applications such as power supplies. In this case a voltage divider on the input is needed, 1:10 to measure voltage up to 5.12 V or 1:100 to measure up to 51.2 V. Also, the decimal point must be indicated, which is easy to implement with unused macrocells.

Conclusion

This pulse counter can be used to measure any frequency dependent parameter such as capacitance, resistance, inductance, distance (using Ultrasonic Ranging Module HC-SR04) etc., see Figure 20.

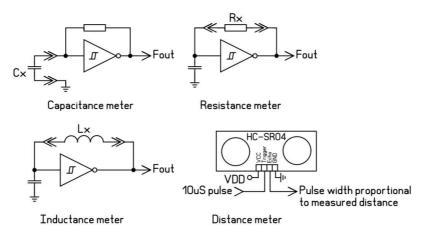


Figure 20. Suggested Projects Using GreenPAK Pulse Counter

The multistage structure makes all projects very flexible and easy to scale.

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01 Jan 2024)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu, Koto-ku, Tokyo 135-0061, Japan www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.