

Introduction

Sometimes it may be necessary to display some digits on a 7-segment display indicator. This can be easily accomplished with a GreenPAK SLG46531V IC thanks to 8-states Asynchronous State Machine (ASM) with configurable outputs for every state.

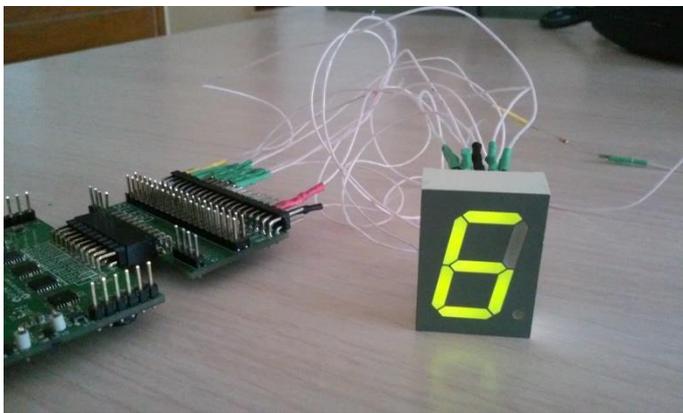


Figure 1. ASM counter appearance

ASM Counter Circuit Design

If we use a 7-segment indicator, we need only 7 logic signals to output any digit by switching on the necessary segments. To do this we may configure 7 of 8 ASM outputs (High or Low) for each state (0..7) in such a way to display some numbers (see Figure 2, Figure 1).

To output number "1" we need to switch on segments B and C, "2" – A, B, G, E, D and so on.

Let's connect indicators' anodes (3 and 8 on the Figure 2) to the Vdd and control the indicator applying Low level to segments' cathodes to switch them on and High level to switch them off.

ASM outputs configuration and outputs: segments connection scheme is shown in Figure 4.

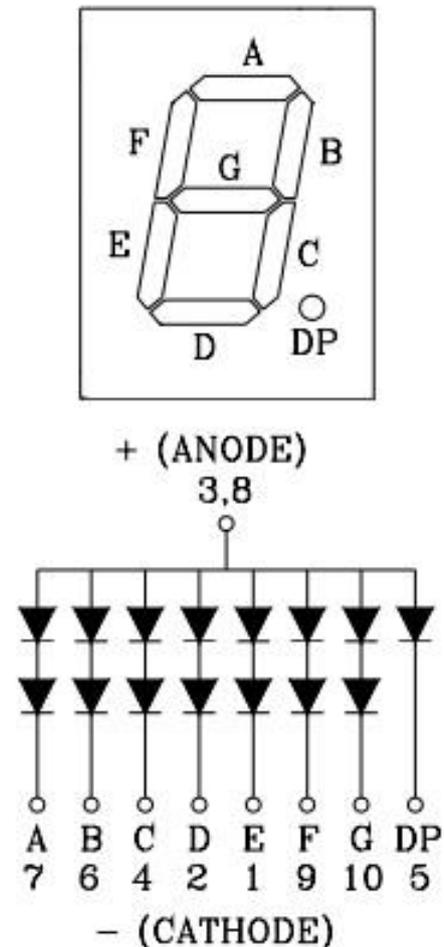


Figure 2. 7- segments Indicator

Such a system is able to display 8 digits: 0, 1, 2, 3, 4, 5, 6 and 7.

PIN#3 is used to switch system On/Off.

To switch ASM on we need to apply High level signal on its nReset input. After ASM reset it starts operating from the initial state (state 0 in our case).

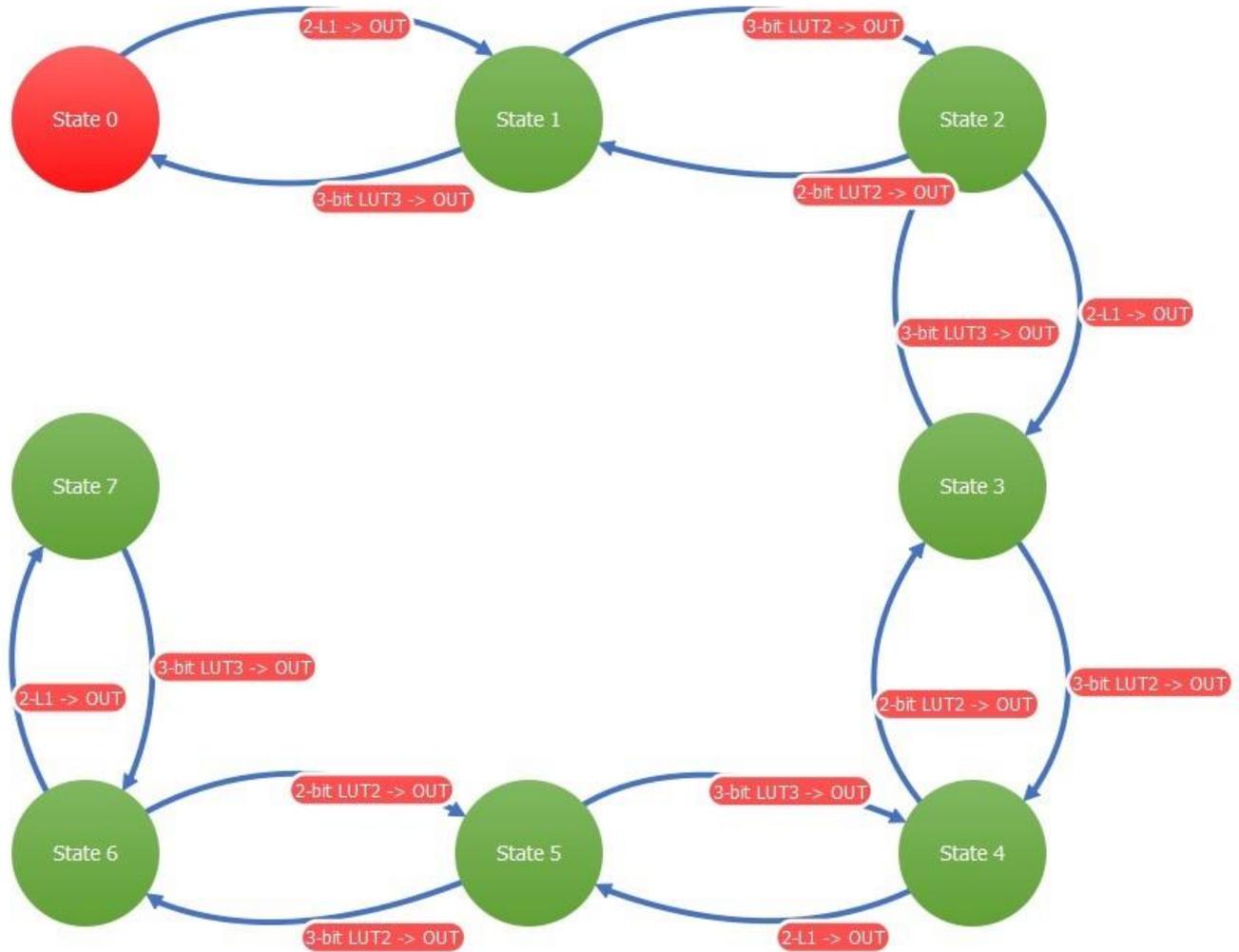


Figure 3. ASM State diagram

ASM state diagram is displayed in Figure 3.

From each state we can move to the next or previous state depending on PIN#4 (Up/Down) level, so it is possible to count up or down.

ASM state transition happens on a High level input signal. If we use one button for transitions and connect it directly, we may jump over some states even if we use an edge detector.

That's why it is necessary to use a circuit which consists of the DFF and LUTs and makes transitions only on the rising edge of the Button (PIN#2) pressing. Each time the Button is pressed, DFF's output will change from High (for even states) to Low (for odd states) and vice versa. 2-L1 and 2-L2 LUTs are used to monitor DFF3 output and Up/Down – PIN#4 input. They initiate transitions from even states: 2-L1 - from lower to higher, 2-L2 - from higher to lower. 3-bit LUTs (3-L2 and 3-L3) have similar function, but in addition, they check 2-bit LUTs (mentioned above) outputs and initiate transitions from odd states: 3-L2 - from lower to higher, 3-L3 - from higher to lower.

To indicate overload, we may use a 5th input (DP) of the 7-segment display, and ASM Out 7, which isn't used for digits' indication. Let's configure this output to be High in the last state (see Figure 4) and configure 3-L4 to latch High, when ASM is in the last state and DFF3 output is High, which means we tried to move into the next after the last state. This LUT will be unlatched on the Low level from the ASM Out 7 (any state except for the last one). Filter 0 is used as an inverter, because active level for this indicator is Low.

State name	Connection Matrix Output RAM							
	OUT7	OUT6	OUT5	OUT4	OUT3	OUT2	OUT1	OUT0
State 0	0	0	0	0	0	0	1	0
State 1	0	1	1	0	1	0	1	1
State 2	0	0	0	0	1	1	0	0
State 3	0	0	1	0	1	0	0	0
State 4	0	1	1	0	0	0	0	1
State 5	0	0	1	1	0	0	0	0
State 6	0	0	0	1	0	0	0	0
State 7	1	0	1	0	1	0	1	1

Segment		A	E	B	F	C	G	D
ASM Out	7	6	5	4	3	2	1	0

Figure 4. ASM RAM Configuration



Figure 5. Different digits displayed

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES (“RENESAS”) PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.