
Schematic Checklist - DA9213/14/15, DA9213-A/14-A/15-A, DA9223-A/24-A

Contents

Contents	1
Tables.....	1
1. Terms and Definitions	2
2. References.....	2
3. Introduction	3
4. Schematic Checklist.....	4
5. Further Assistance	5
6. Revision History	6

Tables

Table 1. Checklist	4
--------------------------	---

1. Terms and Definitions

BGA	Ball grid array
CPU	Central processing unit
GUI	Graphical user interface
IC	Integrated circuit
OTP	One-time programmable memory
PCB	Printed circuit board
PMIC	Power management integrated circuit
WLCSP	Wafer level chip scale packaging

2. References

- [1] DA9213_14_15 Datasheet, Renesas Electronics
- [2] DA9213_14_15 Auto Datasheet, Renesas Electronics
- [3] DA9223_24 Auto Datasheet, Renesas Electronics.

Note 1 References are for the latest published version, unless otherwise indicated.

3. Introduction

DA9213, DA9214, DA9215, DA9223-A, and DA9224-A are PMUs optimized for the supply of CPUs, GPUs, and DDR memory rails in smartphones, tablets and other portable applications. The fast transient response (10 A/ μ s) and load regulation are optimized for the latest generation of multi core application processors.

DA9213 operates as a single four-phase buck converter delivering up to 20 A output current.

DA9214 integrates two dual-phase buck converters, capable of delivering 2 x 10 A output current.

DA9215 integrates a three-phase buck converter capable of delivering 15 A and a single-phase buck converter delivering 5 A output current.

DA9223 operates as a single four-phase buck converter delivering up to 16 A output current.

DA9224 integrates two dual-phase buck converters, capable of delivering 2 x 8 A output current.

This checklist is intended to help a hardware engineer identify common errors that can arise in schematics containing DA9213_14_15_23_24. The checklist is only a reference to common errors, and is not a substitute for rigorous system development and an understanding of the PMUs behaviour as described in the DA9213/4/5 datasheet.

This checklist can also be used for DA9213-A, DA9214-A, and DA9215-A PMUs.

4. Schematic Checklist

Table 1. Checklist

General	Comments				
Design Name					
Schematic Version					
Review Date					
Circle sub PMIC being used	DA9213	DA9214	DA9215	DA9223	DA9224

OTP Variant	Notes	Checked (Y/N)	Comments
Which OTP variant is being used			
OTP Version Number			

Core Operation	Notes	Checked (Y/N)	Comments
V _{sys}	2.8 V to 5.5 V		
V _{DDIO}	1.2 V to 3.6 V Note 1		
V _{DDCORE} capacitor	150 nF		
V _{DDIO} capacitor	100 nF		
V _{sys} capacitor	1 μ F		
V _{DD_BUCKx} capacitor	10 μ F per phase		
V _{OUT_BUCKx} capacitor	47 μ F per phase		
BUCKx inductor	0.22 μ H		
Phase connection	DA9213: BuckA: all phases Pins B1-B4, B8-B11, E1-E4, E8-E11		
	DA9214: BuckA: Phases A1/A2 Pins B1-B4, E1-E4 BuckB: Phases B1/B2 Pins B8-B11, E8-E11		
	DA9215: BuckA: Phases A1/A2/B2 Pins B1-B4, E1-E4, E8-E11 BuckB: Phase B1 Pins B8-B11		
FBAP/FBAN remote sense	Connect to output capacitor Pins C5, D5		
FBBP/FBBN remote sense	For DA9214/5 only. Pins C7, D7 Leave floating for DA9213		
FBAP/FBAN glitch capacitor	2.2 nF		

Core Operation	Notes	Checked (Y/N)	Comments
FBBP/FBBN glitch capacitor	2.2 nF (for DA9214/5 only) Leave floating for DA9213		
V _{SS} to V _{SS_ANA} resistor	1 k between pin E5 to E6		
Q _{GND} separate from P _{GND}	Connect V _{SYS} , V _{DDIO} and V _{SS_ANA} capacitors to Q _{GND} Pin E6, E7 and F6		
Resistive Divider	Total resistance < 30 k from FBxP to FBxN and 1 nF capacitor across upper resistor if used.		
I ² C pull up resistors	Pin A5 and A6. Each signal has < 4k7 pull-up if used.		
nIRQ pull up resistor	Pin F5. Required if used and Open Drain output in OTP		
IC_EN	Pin F7. Needs to be pulled high to enable device operation		
GPIO0	Pin A7. Do OTP settings match GPIO connections		
GPIO1	Pin B7. Do OTP settings match GPIO connections		
GPIO2	Pin B6. Do OTP settings match GPIO connections		
GPIO3	Pin C6. Do OTP settings match GPIO connections		
GPIO4	Pin D6. Do OTP settings match GPIO connections		

Note 1 V_{DDIO} is not allowed to be higher than V_{SYS}

5. Further Assistance

For further assistance on debugging and for a detailed schematic and OTP check, please refer to the combined DA9213/4/5 or DA9223/4 datasheets found on the Renesas website (<https://www.renesas.com>) or contact your local FAE.

6. Revision History

Revision	Date	Description
01.00	Nov 21, 2025	First version.

STATUS DEFINITIONS

Status	Definition
DRAFT	The content of this document is under review and subject to formal approval, which may result in modifications or additions.
APPROVED or unmarked	The content of this document has been approved for publication.

ROHS COMPLIANCE

Renesas Electronics' suppliers certify that its products are in compliance with the requirements of Directive 2011/65/EU of the European Parliament on the restriction of the use of certain hazardous substances in electrical and electronic equipment. RoHS certificates from our suppliers are available on request.

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES (“RENESAS”) PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall be responsible for determining what licenses are required from any third parties, and obtaining such licenses for the lawful import, export, manufacture, sales, utilization, distribution or other disposal of any products incorporating Renesas Electronics products, if required.
5. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
6. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
 - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
 - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.
- Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
7. No semiconductor product is absolutely secure. Notwithstanding any security measures or features that may be implemented in Renesas Electronics hardware or software products, Renesas Electronics shall have absolutely no liability arising out of any vulnerability or security breach, including but not limited to any unauthorized access to or use of a Renesas Electronics product or a system that uses a Renesas Electronics product. RENESAS ELECTRONICS DOES NOT WARRANT OR GUARANTEE THAT RENESAS ELECTRONICS PRODUCTS, OR ANY SYSTEMS CREATED USING RENESAS ELECTRONICS PRODUCTS WILL BE INVULNERABLE OR FREE FROM CORRUPTION, ATTACK, VIRUSES, INTERFERENCE, HACKING, DATA LOSS OR THEFT, OR OTHER SECURITY INTRUSION ("Vulnerability Issues"). RENESAS ELECTRONICS DISCLAIMS ANY AND ALL RESPONSIBILITY OR LIABILITY ARISING FROM OR RELATED TO ANY VULNERABILITY ISSUES. FURTHERMORE, TO THE EXTENT PERMITTED BY APPLICABLE LAW, RENESAS ELECTRONICS DISCLAIMS ANY AND ALL WARRANTIES, EXPRESS OR IMPLIED, WITH RESPECT TO THIS DOCUMENT AND ANY RELATED OR ACCOMPANYING SOFTWARE OR HARDWARE, INCLUDING BUT NOT LIMITED TO THE IMPLIED WARRANTIES OF MERCHANTABILITY, OR FITNESS FOR A PARTICULAR PURPOSE.
8. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
12. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
13. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
14. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Disclaimer Rev.5.0-1)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/