

To our customers,

Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <http://www.renesas.com>

April 1st, 2010
Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (<http://www.renesas.com>)

Send any inquiries to <http://www.renesas.com/inquiry>.

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: “Standard”, “High Quality”, and “Specific”. The recommended applications for each Renesas Electronics product depends on the product’s quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as “Specific” without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as “Specific” or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is “Standard” unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - “Standard”: Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - “High Quality”: Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - “Specific”: Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.

(Note 1) “Renesas Electronics” as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.

(Note 2) “Renesas Electronics product(s)” means any product developed or manufactured by or for Renesas Electronics.

SH7262/SH7264

Guidelines for Hi-Speed USB 2.0 Board Design

Summary

This document describes the guidelines for Hi-Speed USB 2.0 board design.

Target Device

The application explained in this document applies to the following LSIs.

- SH7262/SH7264 (In this document, SH7264/SH7262 are described as "SH7264".)

Note: The contents in this document are provided as a reference example based on the USB specification, and the signal system quality is not guaranteed. When implementing this example into an existing system, the overall system should be thoroughly evaluated, and the user should integrate at their own discretion.

Contents

1. Introduction	2
2. USB Transmission Line	3
3. Power Supply and Ground Pattern	5
4. Oscillation Circuit	6
5. VBUS Power Supply Circuit.....	8
6. REFRIN Pin.....	10
7. EMI/ESD Workarounds.....	11
8. References.....	12

1. Introduction

This document is described by using the pin names of the USB 2.0 host/function module. Table 1 lists the outline of the USB 2.0 host/function module pin.

Table 1 Outline of the USB 2.0 Host/Function Module Pin

Pin Number		Pin Name	I/O	Name	Function
SH7262	SH7264				
71	83	DP	I/O	USB D+ data	USB bus D+ data
70	82	DM	I/O	USB D- data	USB bus D- data
72	84	VBUS	I	VBUS input	Connected to USB bus VBUS
75	87	REFRIN	I	Reference input	Connected to USBAPVss via a 5.6 kΩ ± 1% resistor
65	77	USB_X1	I	USB crystal resonator/ External clock	Connected the USB crystal resonator. An external clock can also be input to the USB_X1 pin.
66	78	USB_X2	O		
76	88	USBAPVcc	I	Transceiver analog pin power supply	3.3 V analog power supply for pins
77	89	USBAPVss	I	Transceiver analog pin ground	3.3 V analog ground for pins
68	80	USBDPVcc	I	Transceiver digital pin power supply	3.3 V digital power supply for pins
69	81	USBDPVss	I	Transceiver digital pin ground	3.3 V digital ground for pins
78	90	USBAVcc	I	Transceiver analog core ground	1.2 V analog power supply for core
79	91	USBAVss	I	Transceiver analog core ground	1.2 V analog ground for core
73	85	USBDVcc	I	Transceiver digital core power supply	1.2 V digital power supply for core
74	86	USBDVss	I	Transceiver digital core ground	1.2 V digital ground for core
80	92	USBUVcc	I	480 MHz power supply for the USB 2.0 host/function module	Power supply for 480 MHz sections
81	93	USBUVss	I	480 MHz ground for the USB 2.0 host/function module	Ground for 480 MHz sections
Note		PVcc	I	Power supply for I/O circuits	3.3 V power supply for I/O pins
		Vcc	I	Power supply	1.2 V power supply for CPU internal core
		Vss	I	Ground for I/O circuit/ Ground	3.3 V ground for I/O pins and 1.2 V ground for CPU internal core

Note: PVcc, Vcc, and Vss pins are LSI I/O power supply and power supply for core other than USB power supply.

2. USB Transmission Line

The USB transmission line indicates the wiring pattern that connects the USB connector and the SH7264 embedded USB transceiver.

USB 2.0 has three communication modes: Hi-Speed, Full-Speed, and Low-Speed modes. The Hi-Speed mode has a 480 Mbps communication speed. Therefore, the USB transmission lines must be designed as a high-frequency circuit. Impedance control is required for the USB transmission lines.

Notes on designing the wiring pattern of the USB transmission lines are described below.

- The characteristic impedance required for the USB transmission lines is the differential impedance $90 \Omega \pm 15\%$.
- The pattern width and pattern pitch for impedance control vary depending on board thickness, material, and layer configuration. Contact the board manufacturer for more details.
- The wiring pattern length of the USB transmission lines from the SH7264 to the USB connector must be designed not to exceed the maximum delay time which is regulated by the USB specification. To stabilize the waveform quality for High-Speed communication, design the wiring pattern length as short as possible. Table 2 lists the recommended values for the wiring pattern length of the USB transmission lines not to exceed the maximum delay time on typical PCB.

Table 2 Recommended Values For the Wiring Pattern Length Not to Exceed the Maximum Delay Time

	Maximum Delay Time (USB specification)	Wiring Pattern Length	D+ and D- Wiring Differential
Host controller	3 ns	300 mm or less	2.5 mm or less
Function controller	1 ns	100 mm or less	2.5 mm or less

Note: This is the example for the wiring delay is 100 ps/cm.

- The lower layer of the USB transmission lines must be a ground plane. The ground plane must be at least 2 mm wider than the USB transmission lines. The power supply for the ground plane is USBDPVss.
- Do not allocate other signal lines near the USB transmission lines. Particularly, lines of heavily fluctuating signals, such as clock and data bus lines must be allocated far from the USB transmission lines. Moreover, the USB transmission lines and other lines must not cross.
- The same layer (surface layer) as the USB transmission lines should be allocated 2 mm far from the USB transmission lines, and grounded with a guard ring.
- The USB transmission lines should be allocated on the same layer without passing through a hole. In addition, wiring should not be divaricated.
- The USB transmission lines should be wired with uniform spaces.
- The USB transmission lines should be allocated far from the oscillator, power supply circuit, and other I/O connectors.
- The USB transmission lines should be wired with straight lines. If they are bent, they should be bent gently in an arc or up to 135 degrees, and should not be bent at acute angles (right angles).
- It is recommended that the clock, reset, read, write and chip select signals should be grounded with a guard ring.

Figure 1 shows a design example of a Host controller USB transmission line pattern, and Figure 2 shows a design example of a function controller USB transmission line pattern.

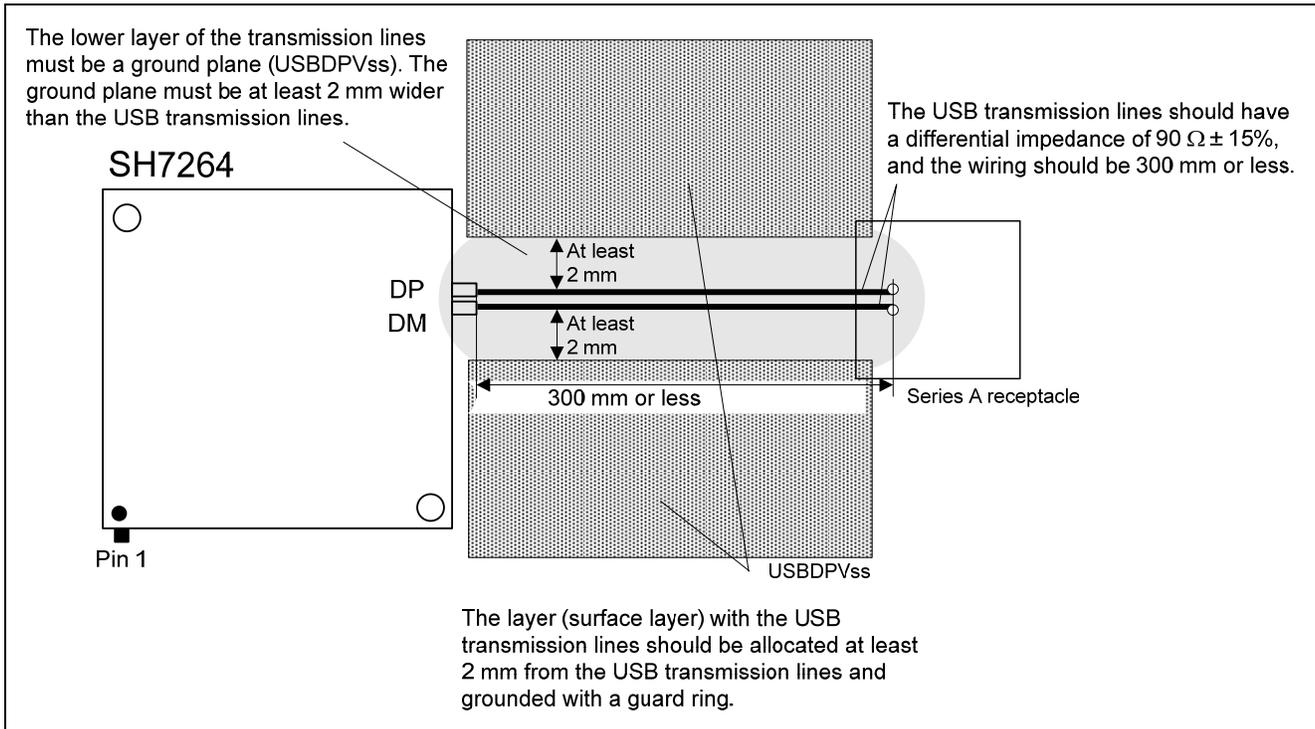


Figure 1 Design Example of the Host Controller USB Transmission Line Pattern

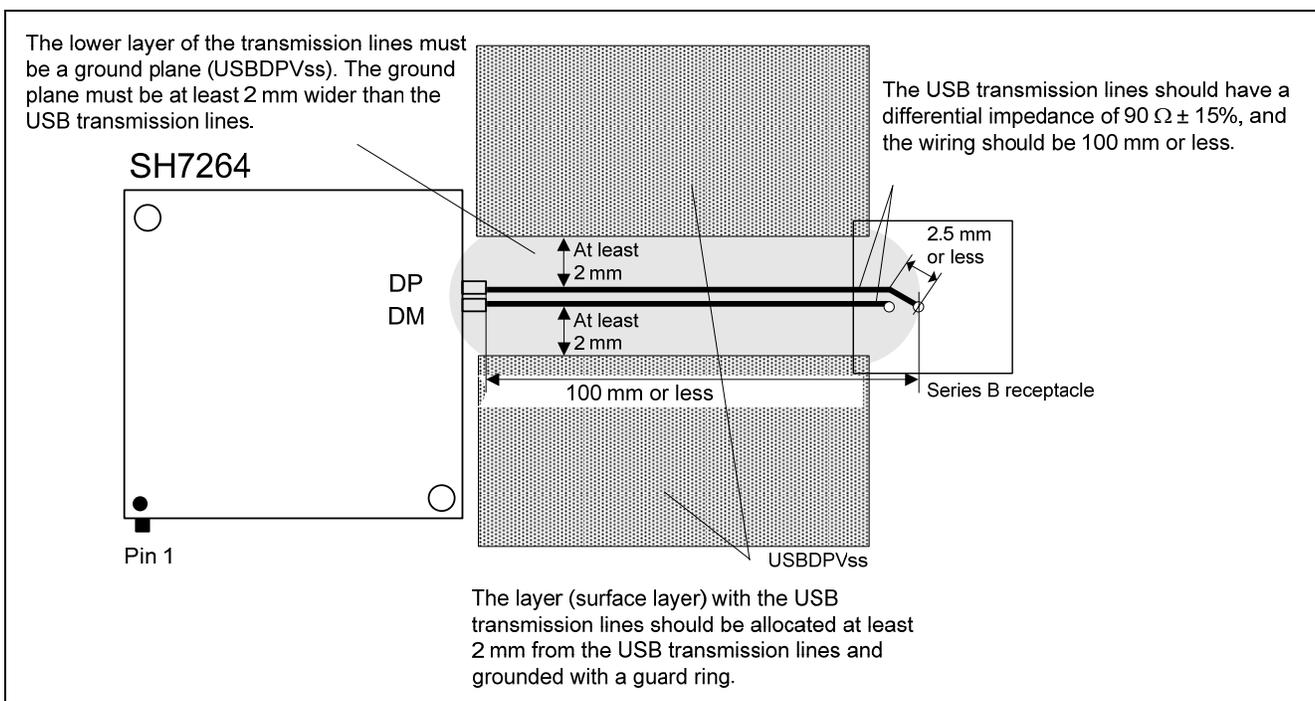


Figure 2 Design Example of the Function Controller USB Transmission Line Pattern

3. Power Supply and Ground Pattern

Notes on designing a power supply/ground pattern are described below.

- Power supplies and ground patterns should be separated into digital and analog. Table 3 and Table 4 list the power supply and ground classifications.

Table 3 USB Power Supply Classifications

Pin Name	Power Supply Classifications			
	Analog Power Supply (1.2 V)	Digital Power Supply (1.2 V)	Analog Power Supply (3.3 V)	Digital Power Supply (3.3 V)
USBAVcc	○			
USBDVcc		○ ^{*1}		
USBUVcc		○ ^{*1}		
USBAPVcc			○	
USBDPVcc				○ ^{*2}
Vcc		○ ^{*1}		
PVcc				○ ^{*2}

○ indicates power supply to use.

- Notes: 1. USBDVcc, USBUVcc, and Vcc pins are connected internally.
 2. USBDPVcc and PVcc pins are connected internally.

Table 4 USB Ground Classifications

SH7264 Pin Name/ USB connector	Ground Classifications	
	Analog Ground (AGND)	Digital Ground (DGND)
USBAVss	○ ^{*3}	
USBDVss		○ ^{*4}
USBUVss		○ ^{*4}
USBAPVss	○ ^{*3}	
USBDPVss		○ ^{*4}
Vss		○ ^{*4}
USB connector ground (including Frame Ground)		○

○ indicates ground to use.

- Notes: 3. USBAVss, and USBAPVss pins are connected internally.
 4. USBDPVss, USBDVss, USBUVss, and Vss pins are connected internally.

- Pins internally-connected should be low-impedance on the board.
- The patterns of power supplies and grounds should be designed with as wide a surface layer as possible.
- Tantalum capacitors or ceramic capacitors having excellent high-frequency characteristics are recommended as power supply capacitors.
- Aluminum electrolytic capacitors affect the jitter value when measuring the EYE pattern. The capacitors should be thoroughly designed and tested before use.
- As the capacitance value of decoupling capacitor, it is recommended that the capacities for 0.001 μF, 0.01 μF, 0.1 μF, and 10 μF are allocated closest to the USB power supply pin. Figure 3 shows an example of decoupling capacitor allocation.

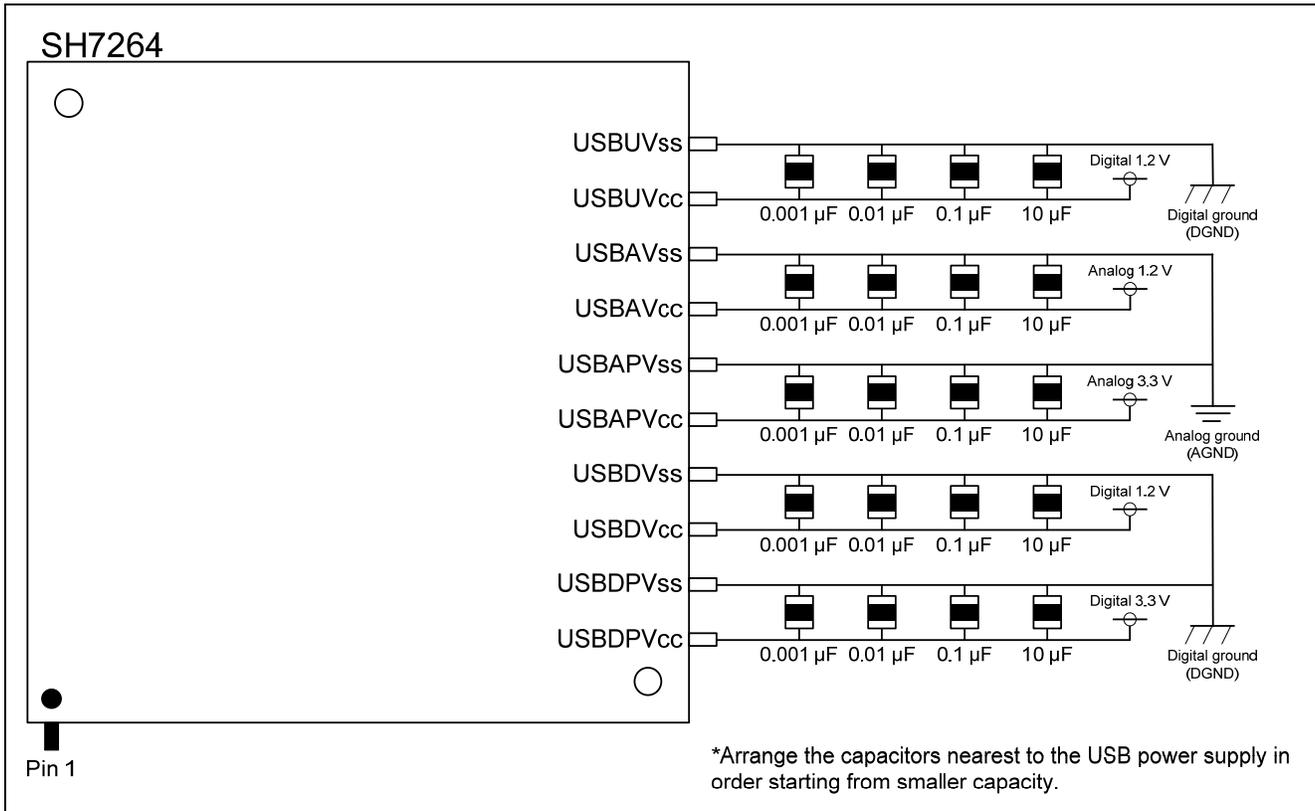


Figure 3 Example of the Decoupling Capacitor Allocation

4. Oscillation Circuit

Notes on designing an oscillation circuit are described below.

- The oscillation circuit should be allocated near the USB_X1 pin, the USB clock input pin. Grounding the USB_X1 pin with a guard ring is recommended.
- Oscillation components that fulfill the frequency shown in Table 5 should be used.

Table 5 USB_X1 Clock Input Frequency

Function	Frequency (fEX)
High-speed transfer used	48 MHz \pm 100 ppm
Host controller used (high-speed transfer is not used)	48 MHz \pm 500 ppm
Neither the high-speed transfer nor the host controller used	48 MHz \pm 2500 ppm

- When using a crystal resonator, the manufacturer should be consulted before deciding the circuit constant.

Figure 4 shows a connection example when the crystal resonator is used, and Figure 5 shows a connection example when the oscillator is used.

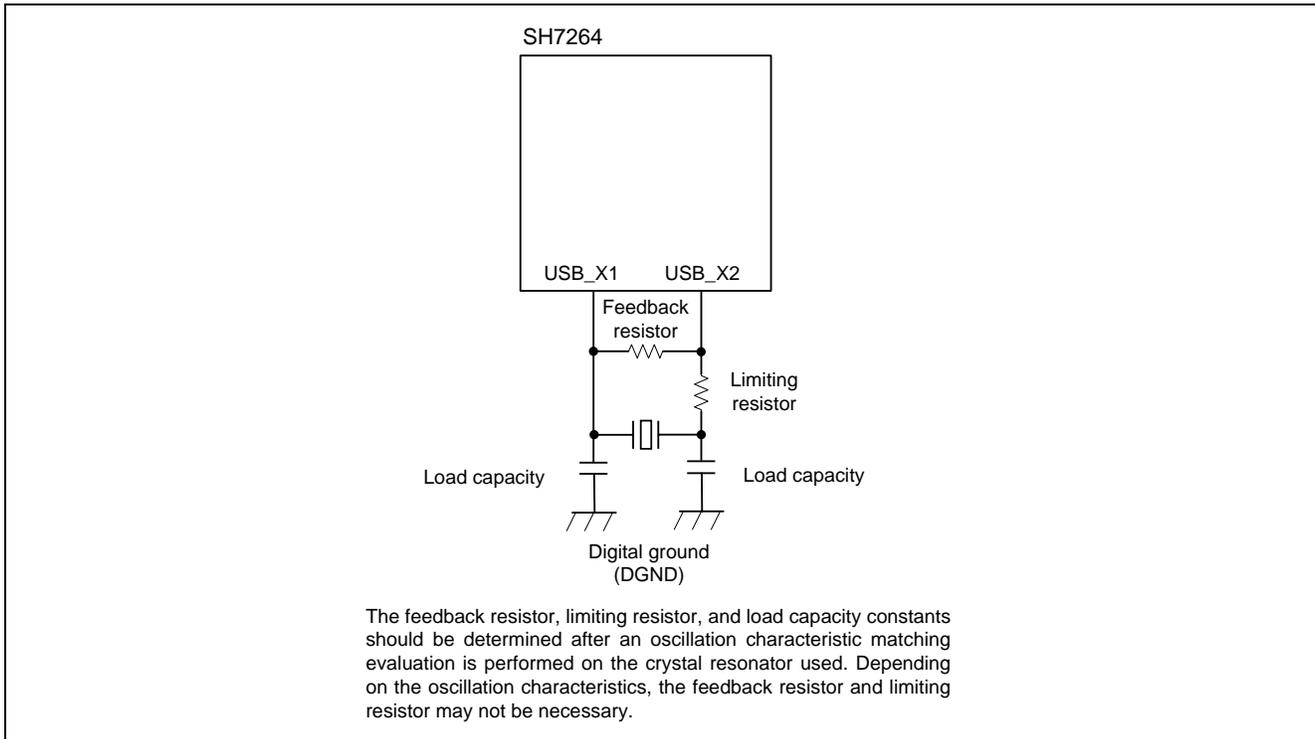


Figure 4 Example of the Crystal Resonator Connection

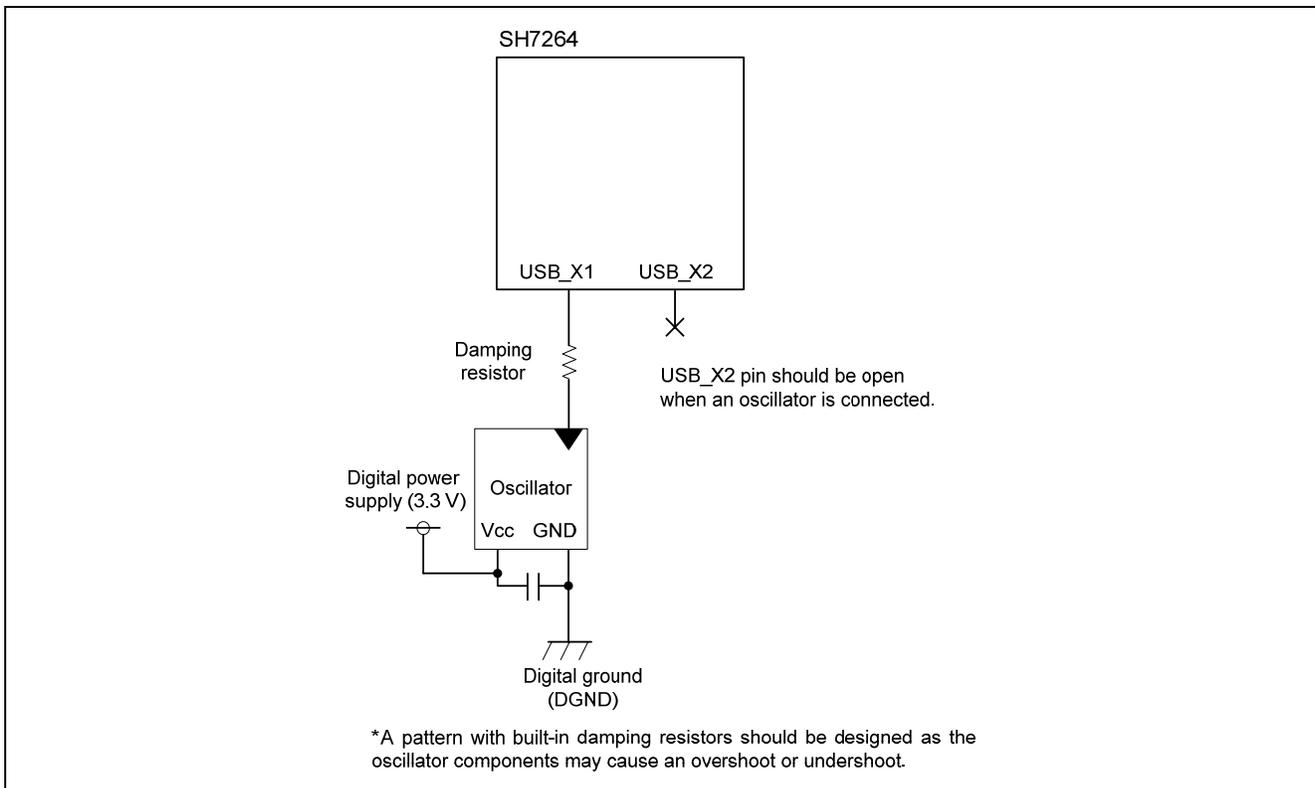


Figure 5 Example of the Oscillator Connection

5. VBUS Power Supply Circuit

Notes on designing the VBUS power supply circuit are described below.

- When the SH7264 is used as a host controller, the additional capacity of the VBUS line should be designed to be 120 μ F or more.
- When the SH7264 is used as a function controller, the additional capacity of the VBUS line should be designed to be within 1.0 μ F to 10 μ F.
- The VBUS line should include a filter circuit as an overshoot may be caused by inconsistent impedance when the USB cable is connected. The 1.0 μ F to 10 μ F capacitor and the 100 Ω to 1 k Ω resistor should be added as a filter circuit. The constants should be defined after confirming that an overshoot has not occurred on the board. Also, a resistor of more than 1 k Ω should not be added.
- When the SH7264 is used as a host controller, the VBUS power should be supplied to the function devices. A power switch IC with over-current protection for the USB power bus (hereinafter called “USB power switch IC”) is recommended for the VBUS power supply control. Make sure to consider the limitation value of the current of VBUS power supply line based on the current value used by the system power supply applied and the USB function devices communicated. In addition, refer to the USB power switch IC datasheet used for the VBUS power supply control circuit.

Figure 6 shows an example of the VBUS power supply circuit when the SH7264 is used as a host controller.

Figure 7 shows an example of the VBUS power supply circuit when the SH7264 is used as a function controller.

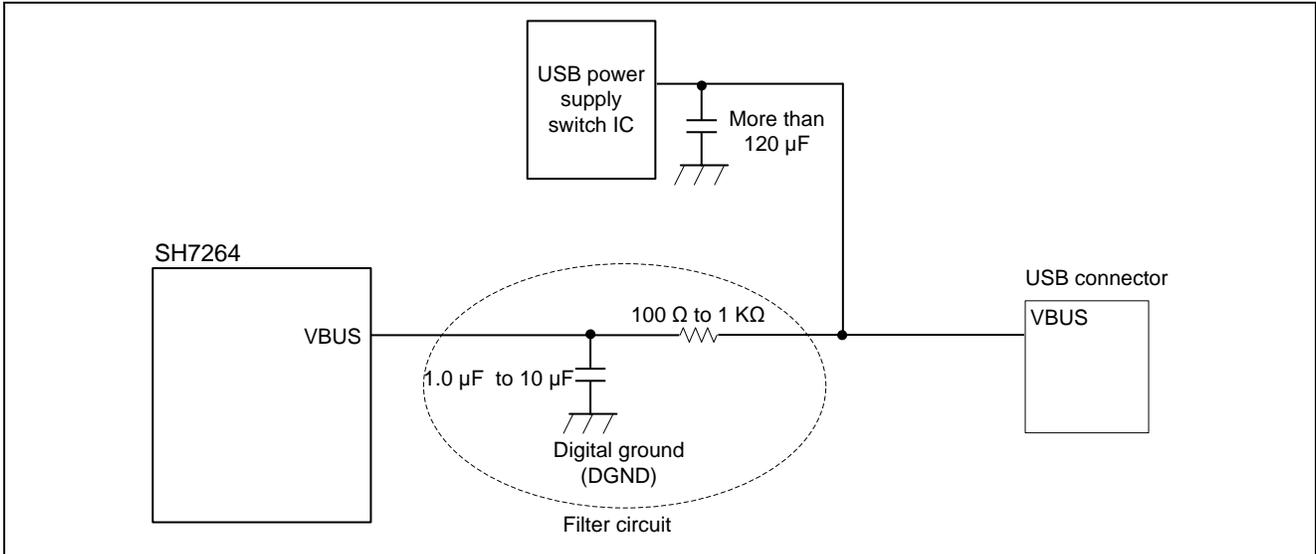


Figure 6 Example of the Host Controller VBUS Power Supply Circuit

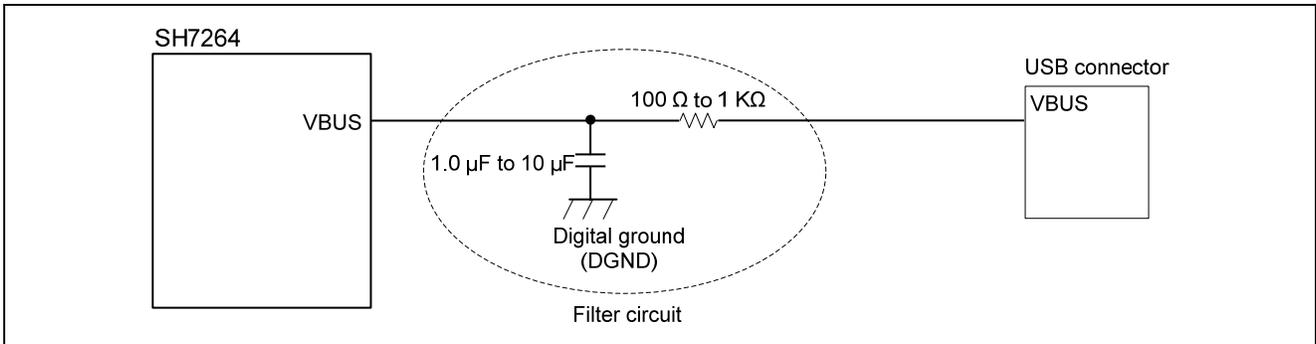


Figure 7 Example of the Function Controller VBUS Power Supply Circuit

6. REFRIN Pin

Notes on designing the circuit around the REFRIN pin are described below.

- A resistor of $5.6\text{ k}\Omega \pm 1\%$ (hereinafter called “reference resistor”) should be allocated between the REFRIN pin and USBAPVss.
- A reference resistor should be allocated as close as possible to the SH7264.
- The REFRIN pin, the reference resistor, and USBAPVss should be connected with a bold, minimal pattern.
- The reference resistor and USBAPVss should be connected in an exclusive pattern, and then connected to the analog ground. The pattern should be designed to avoid common impedance with other signals.
- To prevent cross talk, heavily fluctuating signals such as DP, DM, clocks, address data, and control signals should neither cross nor go side by side with reference resistor and patterns. It is recommended that reference resistor and patterns be grounded with a guard ring.

Figure 8 shows the block diagram of the pin connection and the design example of pattern around the REFRIN pin.

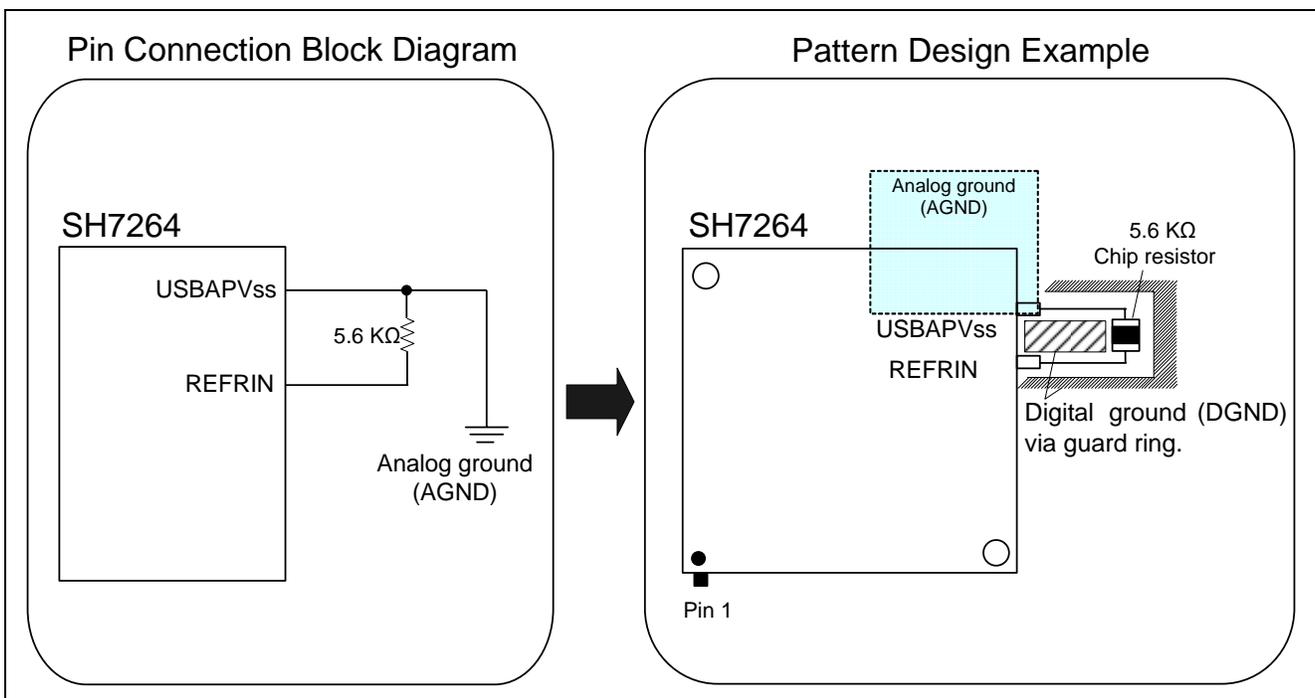


Figure 8 Pin Connection and Design Example of the Pattern Around the REFRIN Pin

7. EMI/ESD Workarounds

Notes on EMI/ESD workarounds are described below.

- When components for EMI/ESD workarounds such as coils and diodes are mounted on the USB transmission lines, they should be allocated near the USB transmission lines and the wiring should be as short as possible.
- The components for the EMI/ESD workarounds must be USB 2.0 compliant. Also, by mounting EMI/ESD workaround components, inconsistent impedance may occur on the USB transmission lines, and the waveform may become distorted. Components for use should be selected after thorough evaluation.

Figure 9 shows the block diagram of a connection example when the components for EMI/ESD workarounds are used.

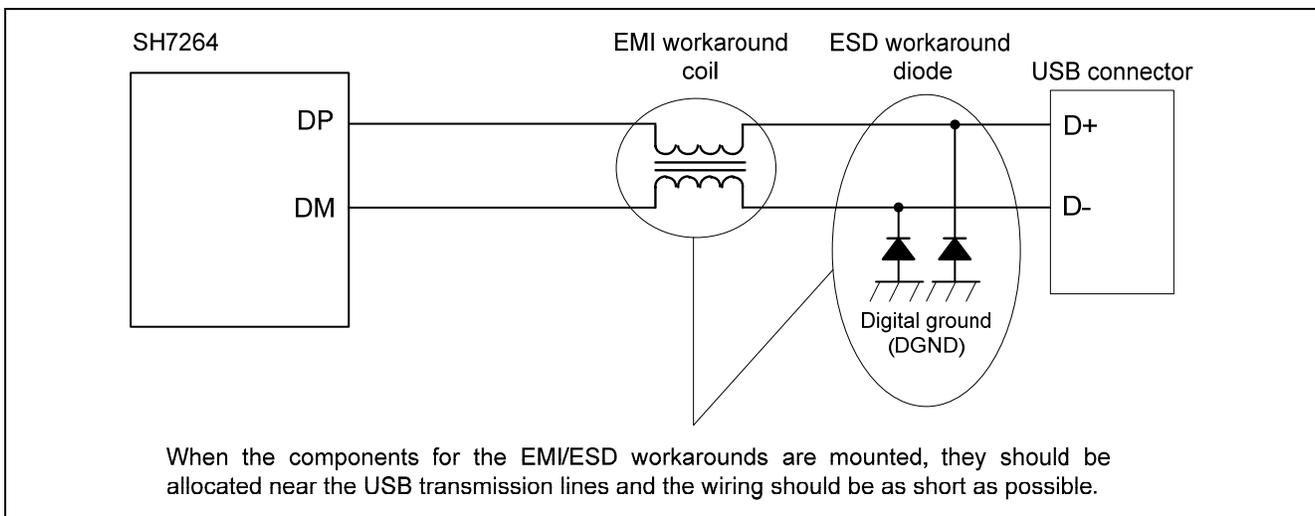


Figure 9 Connection Example When Components for EMI/ESD Workarounds are Used

8. References

- Hardware Manual
SH7262 Group, SH7264 Group Hardware Manual Rev. 1.00
(Download the latest version from the Renesas website.)

Website and Support

Renesas Technology Website

<http://www.renesas.com/>

Inquiries

<http://www.renesas.com/inquiry>

csc@renesas.com

Revision History

Rev.	Date	Description	
		Page	Summary
1.0	Mar. 13, 2009	—	First edition issued

All trademarks and registered trademarks are the property of their respective owners.

Notes regarding these materials

1. This document is provided for reference purposes only so that Renesas customers may select the appropriate Renesas products for their use. Renesas neither makes warranties or representations with respect to the accuracy or completeness of the information contained in this document nor grants any license to any intellectual property rights or any other rights of Renesas or any third party with respect to the information in this document.
2. Renesas shall have no liability for damages or infringement of any intellectual property or other rights arising out of the use of any information in this document, including, but not limited to, product data, diagrams, charts, programs, algorithms, and application circuit examples.
3. You should not use the products or the technology described in this document for the purpose of military applications such as the development of weapons of mass destruction or for the purpose of any other military use. When exporting the products or technology described herein, you should follow the applicable export control laws and regulations, and procedures required by such laws and regulations.
4. All information included in this document such as product data, diagrams, charts, programs, algorithms, and application circuit examples, is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas products listed in this document, please confirm the latest product information with a Renesas sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas such as that disclosed through our website. (<http://www.renesas.com>)
5. Renesas has used reasonable care in compiling the information included in this document, but Renesas assumes no liability whatsoever for any damages incurred as a result of errors or omissions in the information included in this document.
6. When using or otherwise relying on the information in this document, you should evaluate the information in light of the total system before deciding about the applicability of such information to the intended application. Renesas makes no representations, warranties or guaranties regarding the suitability of its products for any particular application and specifically disclaims any liability arising out of the application and use of the information in this document or Renesas products.
7. With the exception of products specified by Renesas as suitable for automobile applications, Renesas products are not designed, manufactured or tested for applications or otherwise in systems the failure or malfunction of which may cause a direct threat to human life or create a risk of human injury or which require especially high quality and reliability such as safety systems, or equipment or systems for transportation and traffic, healthcare, combustion control, aerospace and aeronautics, nuclear power, or undersea communication transmission. If you are considering the use of our products for such purposes, please contact a Renesas sales office beforehand. Renesas shall have no liability for damages arising out of the uses set forth above.
8. Notwithstanding the preceding paragraph, you should not use Renesas products for the purposes listed below:
 - (1) artificial life support devices or systems
 - (2) surgical implantations
 - (3) healthcare intervention (e.g., excision, administration of medication, etc.)
 - (4) any other purposes that pose a direct threat to human life
 Renesas shall have no liability for damages arising out of the uses set forth in the above and purchasers who elect to use Renesas products in any of the foregoing applications shall indemnify and hold harmless Renesas Technology Corp., its affiliated companies and their officers, directors, and employees against any and all damages arising out of such applications.
9. You should use the products described herein within the range specified by Renesas, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas shall have no liability for malfunctions or damages arising out of the use of Renesas products beyond such specified ranges.
10. Although Renesas endeavors to improve the quality and reliability of its products, IC products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Please be sure to implement safety measures to guard against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other applicable measures. Among others, since the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
11. In case Renesas products listed in this document are detached from the products to which the Renesas products are attached or affixed, the risk of accident such as swallowing by infants and small children is very high. You should implement safety measures so that Renesas products may not be easily detached from your products. Renesas shall have no liability for damages arising out of such detachment.
12. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written approval from Renesas.
13. Please contact a Renesas sales office if you have any questions regarding the information contained in this document, Renesas semiconductor products, or if you have any other inquiries.