
R8A66593 / R8A66597

R19AN0016EJ0200

Rev.2.00

Dec 7, 2012

Guidelines for Hi-Speed USB 2.0 Board Design

Summary

This document describes the guidelines for Hi-Speed USB 2.0 board design.

Operation Check Devices

The application explained in this document applies to the following ASSP.

- R8A66593 USB Peripheral Controller
- R8A66597 USB Host & Peripheral Controller

This document is described as “R8A66593 / 7” about “R8A66593” and “R8A66597”.

Note: The contents in this document are provided as a reference example based on USB specification, and the signal system quality is not guaranteed. When implementing this example into an existing system, the overall system should be thoroughly evaluated, and the user should integrate at their own discretion.

Contents

| | |
|--|----|
| 1. Introduction | 2 |
| 2. USB Transmission Line | 4 |
| 3. Power Supply and Ground Pattern | 6 |
| 4. Oscillation Circuit | 8 |
| 5. VBUS Power Supply Circuit | 9 |
| 6. REFRIN Pin | 11 |
| 7. EMI/ESD Workarounds | 12 |

1. Introduction

This document is described by using the pin names of R8A66593/7. Table 1.1 lists the outline of R8A66593 USB2.0 module pin and Table 1.2 lists the outline of R8A66597 USB 2.0 module pin.

Table1.1 Outline of R8A66593 USB2.0 Module Pin

| Pin number | Pin Name | I/O | Name | Function |
|---|----------|-----|--|--|
| 40(J9) | DP0 | I/O | USB D+ data | Connect to D+ pin of USB bus. |
| 39(J8) | DM0 | I/O | USB D- data | Connect to D- pin of USB bus. |
| 41(H9) | VBUS | I | VBUS input | Connect directly to Vbus of USB bus. Can detect Vbus connection/disconnection. Connect to 5V when not connecting to Vbus. |
| 27(J4) | REFRIN | I | Reference input | Connect to AGND pin through 5.6kΩ±1% resistor. |
| 23(H3) | XIN | I | USB crystal resonator/ External clock | Connect crystal oscillator between XIN and XOUT. Connect external clock signal to XIN in order to input external clock, and leave open XOUT. |
| 24(J3) | XOUT | O | | |
| 25(G3) | AVCC | I | Transceiver analog pin power supply | 3.3V analog power supply for pins. |
| 26(H4) | AGND | I | Transceiver analog pin ground | 3.3V analog ground for pins. |
| 22,35,43 (G9),(H5),(J2) | VCC | I | Transceiver digital pin power supply | 3.3V digital power supply for pins. |
| 11,21,29,32, 33,34,38,42, 45,50,61,71, 80 (A1),(A5),(A9), (E1),(E5),(E9), (F7),(G5),(G7), (H6),(H7),(H8), (J1),(J7) | GND | I | Transceiver digital pin ground | 3.3V digital ground for pins. |
| 1,20,60,70 (B1),(B5), (B9),(H1) | VIF | I | Power supply for I/O circuit | 3.3V or 1.8V power supply for I/O pin. |
| 10,51 (E2),(E8) | VDD | O | Core power | Connect the 4.7uF and 0.1uF capacitor between GND. |

Note: In () of the pin number, the pin number for the R8A66593BG package.

Table1.2 Outline of R8A66597 USB2.0 Module Pin

| Pin number | Pin Name | I/O | Name | Function |
|------------|----------|-----|-------------|---|
| 40(J9) | DP0 | I/O | USB D+ data | Connect to D+ pin of USB bus. |
| 37(J6) | DP1 | | | |
| 39(J8) | DM0 | I/O | USB D- data | Connect to D- pin of USB bus. |
| 36(J5) | DM1 | | | |
| 41(H9) | VBUS | I | VBUS input | <Host Controller> Leave open or connect directly to Vbus of USB bus. *This pin cannot supply Vbus to the connected device. <Peripheral Controller> |

| Pin number | Pin Name | I/O | Name | Function |
|---|----------|-----|---|--|
| | | | | Connect directly to Vbus of USB bus. Can detect Vbus connection/disconnection. Connect to 5V when not connecting to Vbus. |
| 27(J4) | REFRIN | I | Reference input | Connect to AGND pin through 5.6kΩ±1% resistor. |
| 23(H3) | XIN | I | USB crystal resonator/ External clock | Connect crystal oscillator between XIN and XOUT. Connect external clock signal to XIN in order to input external clock, and leave open XOUT. |
| 24(J3) | XOUT | O | | |
| 25(G3) | AVCC | I | Transceiver analog pin power supply | 3.3V analog power supply for pins. |
| 26(H4) | AGND | I | Transceiver analog pin ground | 3.3V analog ground for pins. |
| 22,35,43 (G9),(H5),(J2) | VCC | I | Transceiver digital pin power supply | 3.3V digital power supply for pins. |
| 11,21,38,42, 45,50,61,71, 80 (A1),(A5),(A9), (E1),(E5),(E9), (F7),(H8),(J1), (J7) | GND | I | Transceiver digital pin ground | 3.3V digital ground for pins. |
| 1,20,60,70 (B1),(B5), (B9),(H1) | VIF | I | Power supply for I/O circuit | 3.3V or 1.8V power supply for I/O pin. |
| 10,51 (E2),(E8) | VDD | O | Core power | Connect the 4.7μF and 0.1μF capacitor between GND. |
| 30(F5) | VBOU0 | O | External power on | Used for ON/OFF output to external power supply circuit. Connect to external power supply circuit for Vbus supply. VBOU1 pin cannot be used when using DP0, DM0 as OTG. |
| 28(G4) | VBOU1 | O | | |
| 33(H7) | OVCUR0A | I | Overcurrent input for Port0 | Used for input of over-current detection from external power supply circuit. Connect to PORT0 external power supply circuit. When input for over-current detection from external power supply circuit is one pin, connect to OVCUR0A and fix OVCUR0B to High or Low. |
| 34(H6) | OVCUR0B | I | | |
| 29(G5) | OVCUR1 | I | Overcurrent input for Port1 | Used for input of over-current detection from external power supply circuit. Connect to PORT1 external power supply circuit. OVCUR1 pin cannot be used when using DP0, DM0 as OTG. |
| 31(G6) | EXTLP0 | O | Control of external power for low power consumption | Used for low-power consumption mode ON/OFF switch when external power supply circuit has low-consumption mode. Connect to PORT0 external power supply circuit. |
| 32(G7) | ID0 | I | ID input | When using USB Micro-AB receptacle, connect to ID pin. |

Note: In () of the pin number, the pin number for the R8A66597BG package.

2. USB Transmission Line

The USB transmission line indicates the wiring pattern that connects the USB connector and the R8A66593 / 7 embedded USB transceiver.

USB 2.0 has three communication modes: Hi-Speed, Full-Speed and Low-Speed modes. The Hi-Speed mode has a 480Mbps communication speed. Therefore, the USB transmission lines must be designed as a high-frequency circuit. Impedance control is required for the USB transmission lines.

Notes on designing the wiring pattern of USB transmission lines are described below.

- The characteristic impedance required for the USB transmission lines is the differential impedance $90\Omega \pm 15\%$.
- The pattern width and pattern pitch for impedance control vary depending on board thickness, material, and layer configuration. Contact the board manufacturer for more details.
- The wiring pattern length of USB transmission lines from the R8A66593 / 7 to the USB connector must be designed not to exceed the maximum delay time which is regulated by the USB specification. Table 2 lists the recommended values for the wiring pattern length of USB transmission lines for host and Peripheral.

Table 2 Recommended Value for the Wiring Pattern Length of USB Transmission Line

| | Maximum Delay Time (USB Specification) | Wiring Length | D+ and D- Wiring Length Differential |
|--------------------------|---|---------------|---|
| Host Controller | 3ns | 300mm or less | 2.5mm or less |
| Peripheral Controller | 1ns | 100mm or less | 2.5mm or less |

- The lower layer of the USB transmission lines must be a ground plane. The ground plane must be at least 2mm wider than the USB transmission lines. The power supply for the ground plane is GND
- Do not allocate other signal lines near the USB transmission lines. Particularly lines of heavily fluctuating signals, such as clock and data bus lines, must be allocated far from the USB transmission lines. Moreover, the USB transmission lines and other lines must not cross.
- The same layer (surface layer) as the USB transmission lines should be allocated 1mm from the USB transmission lines, and grounded with a guard ring.
- USB transmission lines should be allocated on the same layer without passing through a hole. In addition, wiring should not be divaricated.
- The USB transmission lines should be wired with uniform spaces.
- The USB transmission lines should be allocated far from the oscillator, power supply circuit, and other I/O connectors.
- The USB transmission lines should be wired with straight lines. If they are bent, they should be bent gently in an arc or up to 135 degrees, and not bent at acute angles (right angles).
- It is recommended that the clock, reset, read, write and chip select signals should be grounded with a guard ring.

Figure 1 shows a design example of a Host controller USB transmission line pattern, and figure 2 shows a design example of a Peripheral controller USB transmission line pattern.

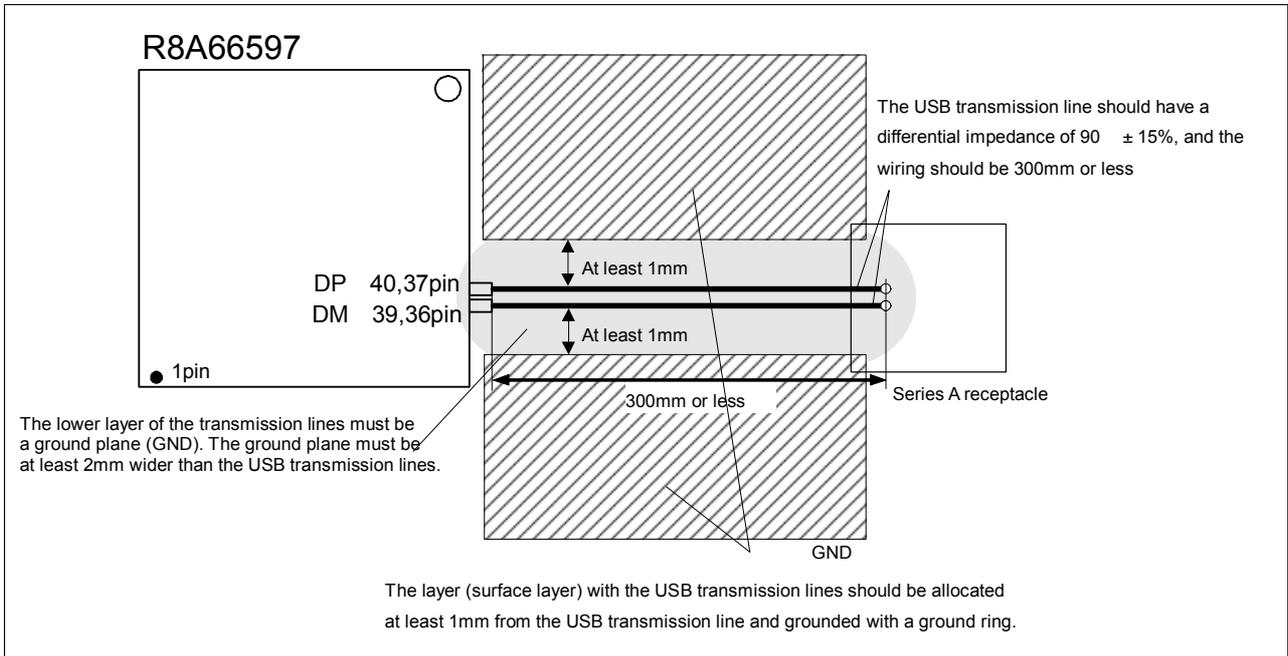


Figure 1 Design Example of a Host Controller USB Transmission Line Pattern

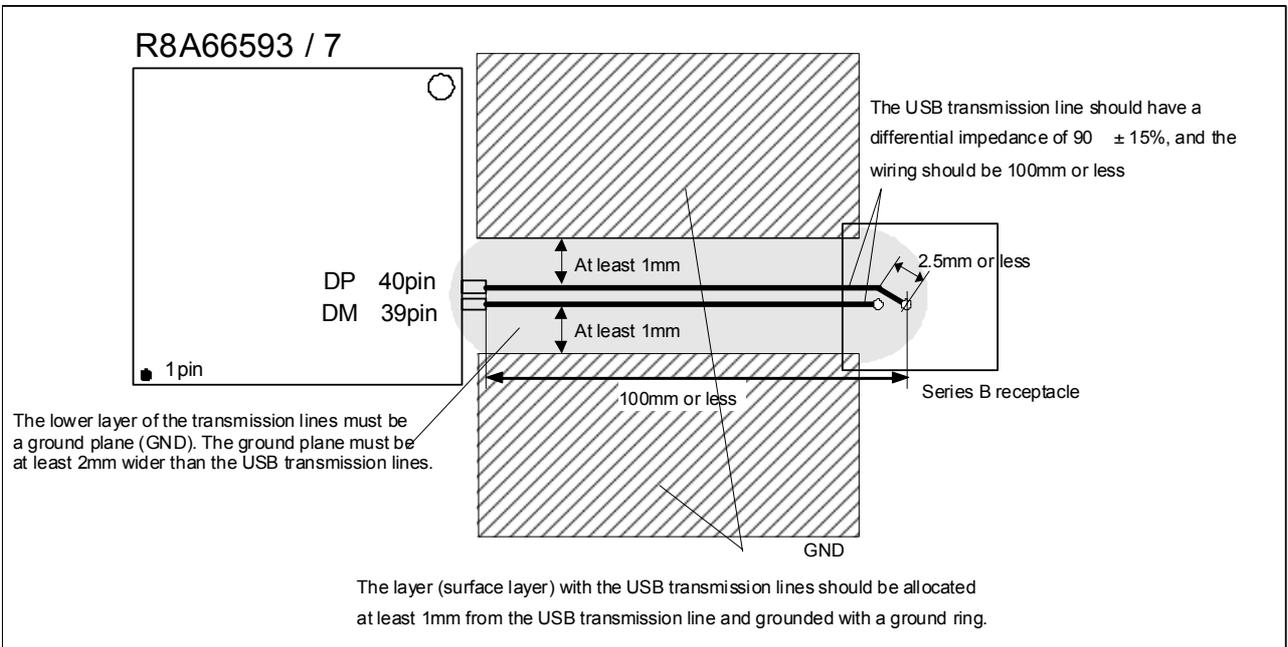


Figure 2 Design Example of a Peripheral Controller USB Transmission Line Pattern

3. Power Supply and Ground Pattern

Notes on designing a power supply/ground pattern are described below.

- Power supplies and ground patterns should be separated into digital and analog. Table 3 and Table 4 list the power supply and ground classifications.

Table 3 USB Power Supply Classifications

| R8A66593 / 7 Pin Name | Power Supply Classifications | | | |
|-----------------------|-------------------------------|--------------------------------|--------------------------------|------------------------------|
| | Analog Power Supply (3.3V) | Digital Power Supply (3.3V) | Digital Power Supply (1.8V) | Digital Core Power Supply |
| AVCC | ○ | | | |
| VCC | | ○ | | |
| VIF | | ○ | ○ | |

○: Indicates power used.

Table 4 USB Ground Classifications

| R8A66593 / 7 Pin Name/ USB Connector | Ground Classifications | |
|--|------------------------|----------------------|
| | Analog Ground (AGND) | Digital Ground (GND) |
| AGND | ○ | |
| GND | | ○ |
| USB Connector Ground (Including Frame Ground) | | ○ |

○: Indicates the ground used.

- The patterns of power supplies and grounds should be designed with as wide a surface layer as possible.
- Tantalum capacitors or ceramic capacitors having excellent high-frequency characteristics are recommended as power supply capacitors.
- Aluminum electrolytic capacitors affect the jitter value when measuring the EYE pattern. The capacitors should be thoroughly designed and tested before use.
- As the capacitance value of decoupling capacitor, it is recommended that the capacities for 0.001uF, 0.01uF, 0.1uF, and 10uF are allocated closest to the USB power supply pin. Figure 3 shows an example of decoupling capacitor allocation.
- Please connect digital ground and analog ground by one point near R8A66593 / 7.

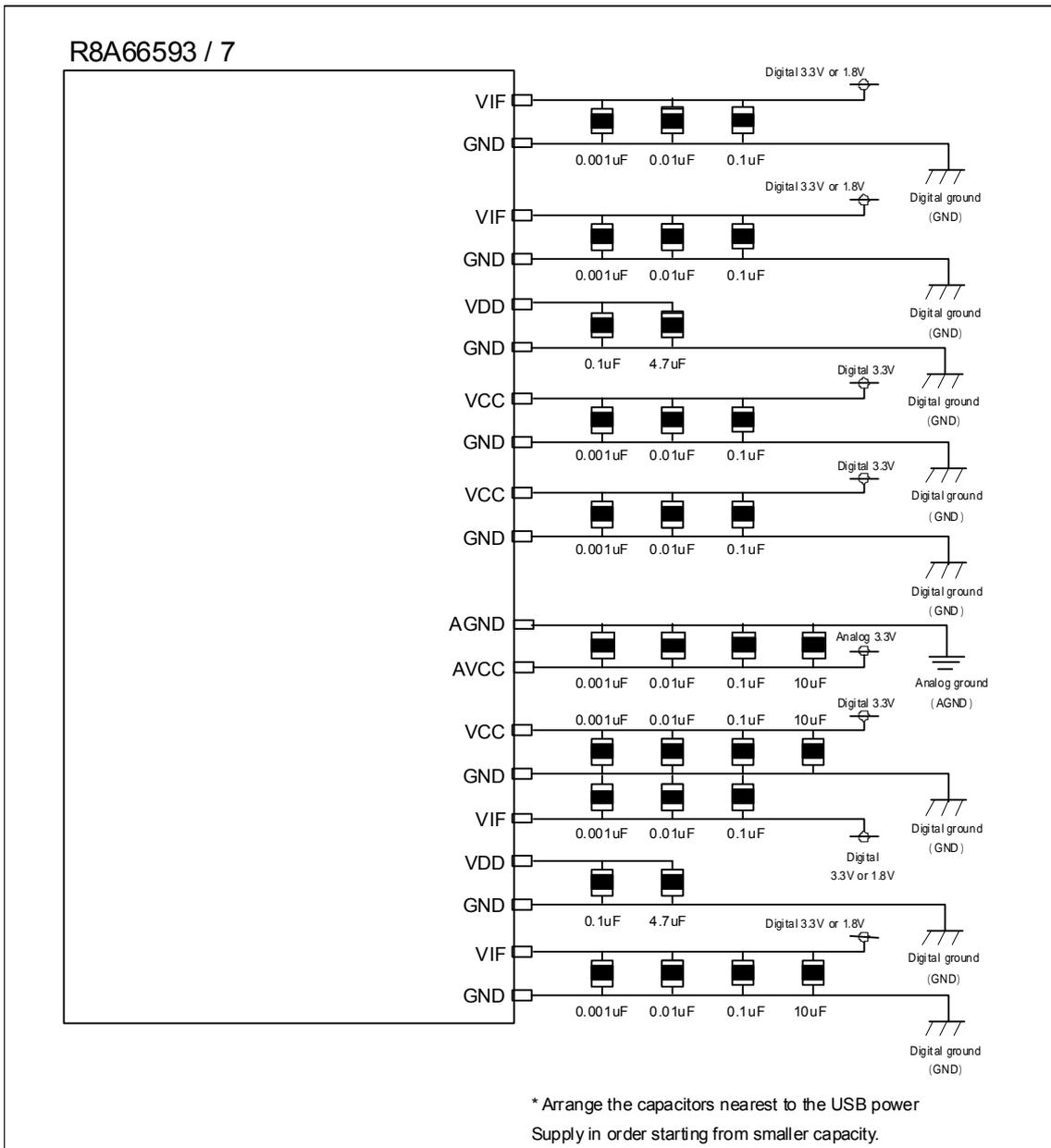


Figure 3 Example of Decoupling Capacitor Allocation

4. Oscillation Circuit

Notes on designing an oscillation circuit are described below.

- The oscillation circuit should be allocated near the XIN clock input pin. Grounding the XIN with a guard ring is recommended.
- Oscillation components that fulfill a 12, 24, 48 MHz \pm 100ppm frequency specification should be used.
- When using a crystal resonator, the manufacturer should be consulted before deciding the circuit constant.

Figure 4 shows a connection example when the crystal resonator is used, and Figure 5 shows a connection example when an oscillator is used.


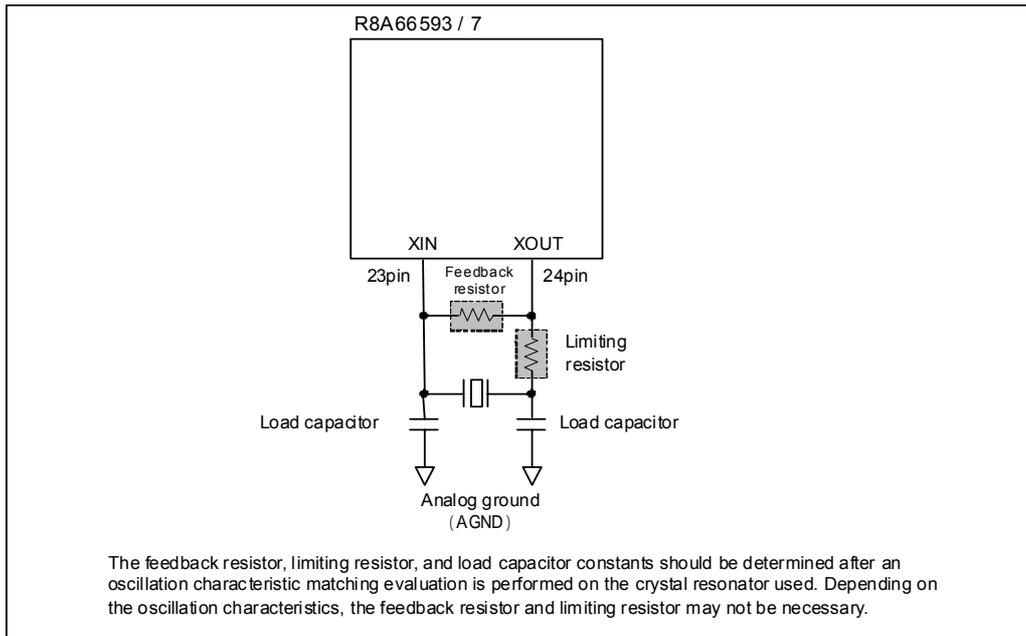


Figure 4 Example of a Crystal Resonator Connection

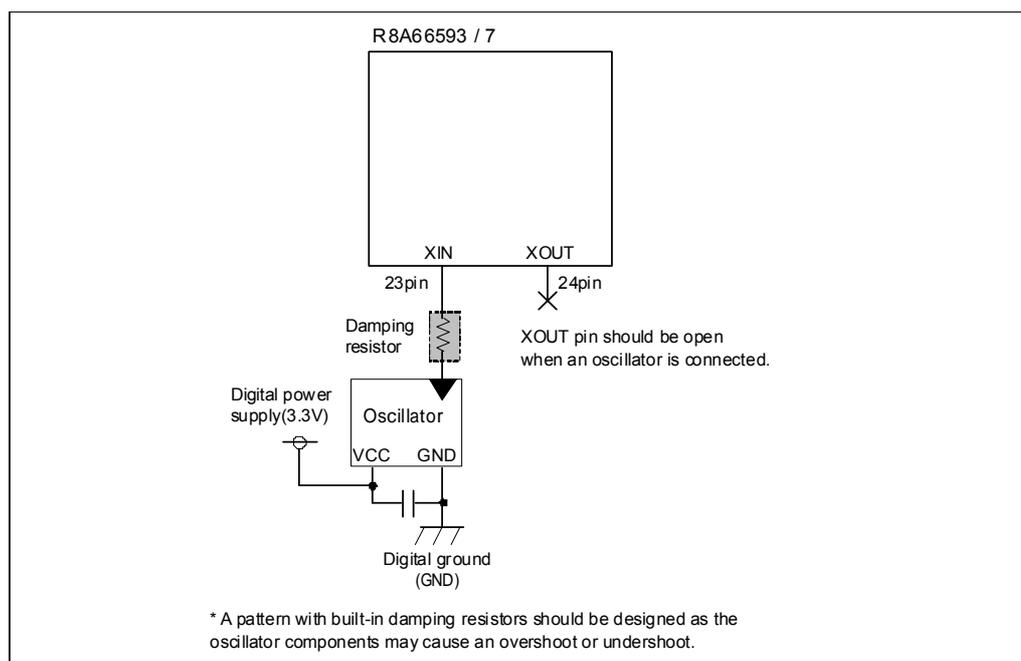

Example of an Oscillator Connection

Figure 5

5. VBUS Power Supply Circuit

Notes on designing the VBUS power supply circuit are described below.

- When the R8A66597 is used as a host controller, the additional capacity of the VBUS line should be designed to be 120uF or more.
- When the R8A66593 / 7 is used as a Peripheral controller, the additional capacity of the VBUS line should be designed to be within 1.0uF to 10uF.
- The VBUS line should include a filter circuit as an overshoot may be caused by inconsistent impedance when the USB cable is connected. The 1.0uF to 10uF capacitor and 100Ω to 1kΩ resistor should be added as a filter circuit. The constant should be defined after confirming that an overshoot has not occurred on the board. Also, a resistor of more than 1kΩ should not be added.
- When the R8A66597 is used as a host controller, the VBUS power should be supplied to the Peripheral devices. A power supply switch IC with over-current protection for the USB power bus (hereinafter called “USB power supply switch IC”) is recommended for the VBUS power supply control. Make sure to consider the limitation value of the current of VBUS power supply line based on the current value used by the system power supply applied and the USB Peripheral devices communicated. In addition, refer to the USB power supply switch IC datasheet used for VBUS power supply control circuit.

Figure 6 shows an example of the VBUS power supply circuit when it is used as a host controller, and Figure 7 shows an example of the VBUS power supply circuit when it is used as a Peripheral controller.

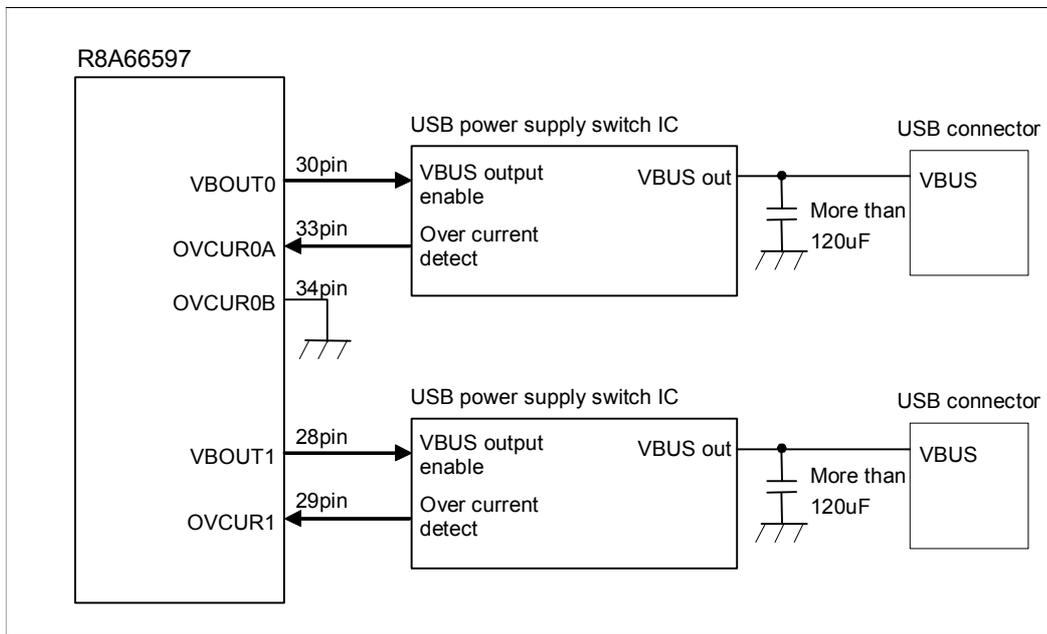


Figure 6 Example of Host Controller VBUS Power Supply Circuit

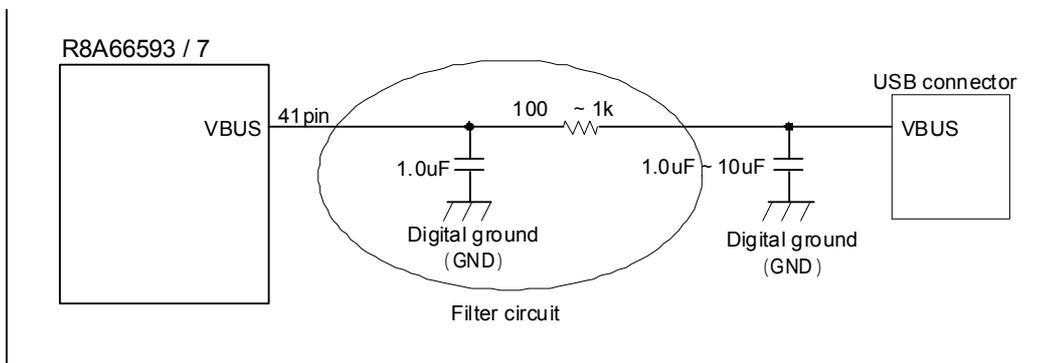


Figure 7 Example of Peripheral Controller VBUS Power Supply Circuit

6. REFRIN Pin

Notes on designing the circuit around the REFRIN pin are described below.

- A resistor of $5.6\text{k}\Omega \pm 1\%$ (hereinafter called “standard resistor”) should be allocated between the REFRIN pin and AGND.
- A standard resistor should be allocated as close as possible to the R8A66593 / 7.
- The REFRIN pin, the standard resistor, and AGND should be connected with a bold, minimal pattern.
- The standard resistor and AGND should be connected in an exclusive pattern, and then connected to the analog ground. The pattern should be designed to avoid common impedance with other signals.
- To prevent cross talk, heavily fluctuating signals such as DP, DM, clocks, address data, and control signals should neither cross nor go side by side with standard resistor and patterns. It is recommended that standard resistor and patterns be grounded with a guard ring.

Figure 8 shows the block diagram of the pin connection and the design example of pattern around the REFRIN pin.

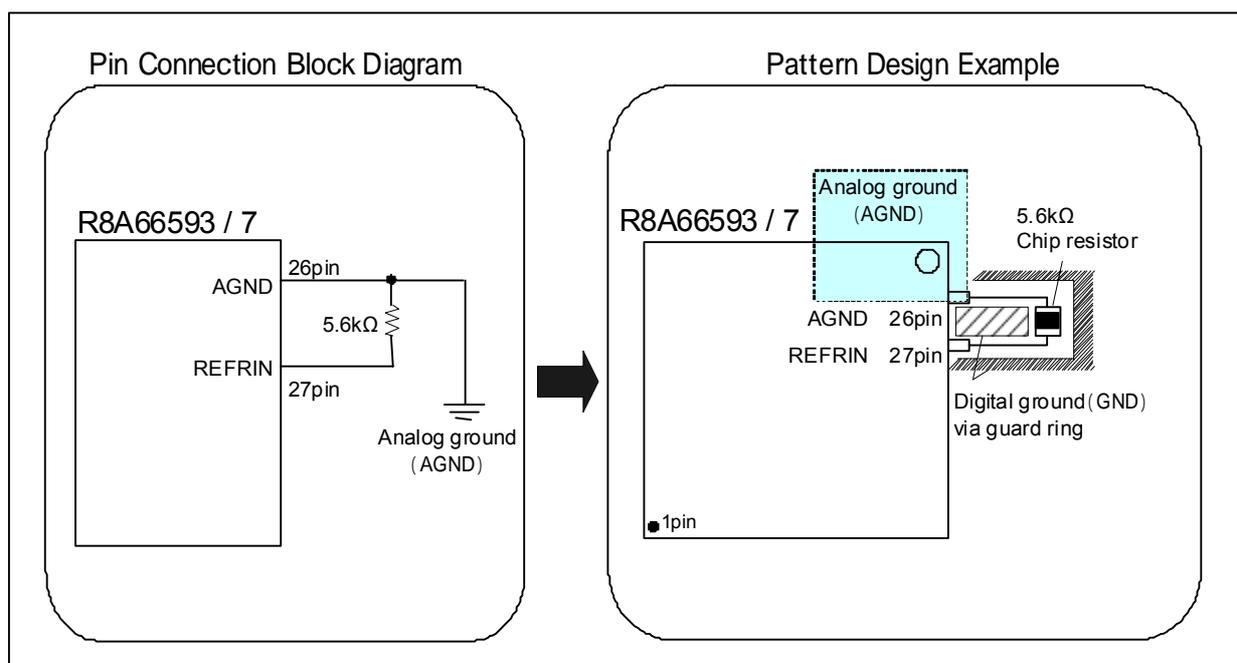


Figure 8 Pin Connection and Design Example of Pattern Around the REFRIN Pin

7. EMI/ESD Workarounds

Notes on EMI/ESD workarounds are described below.

- When components for EMI/ESD workarounds such as coils and diodes are mounted on the USB transmission lines, they should be allocated near the USB transmission lines and the wiring should be as short as possible.
- The components for the EMI/ESD workarounds must be USB 2.0 compliant. Also, by mounting EMI/ESD workaround components, an inconsistent impedance may occur on the USB transmission lines, and the waveform may become distorted. Components for use should be selected after thorough evaluation.

Figure 9 shows the block diagram of a connection example when the components for EMI/ESD workarounds are used.

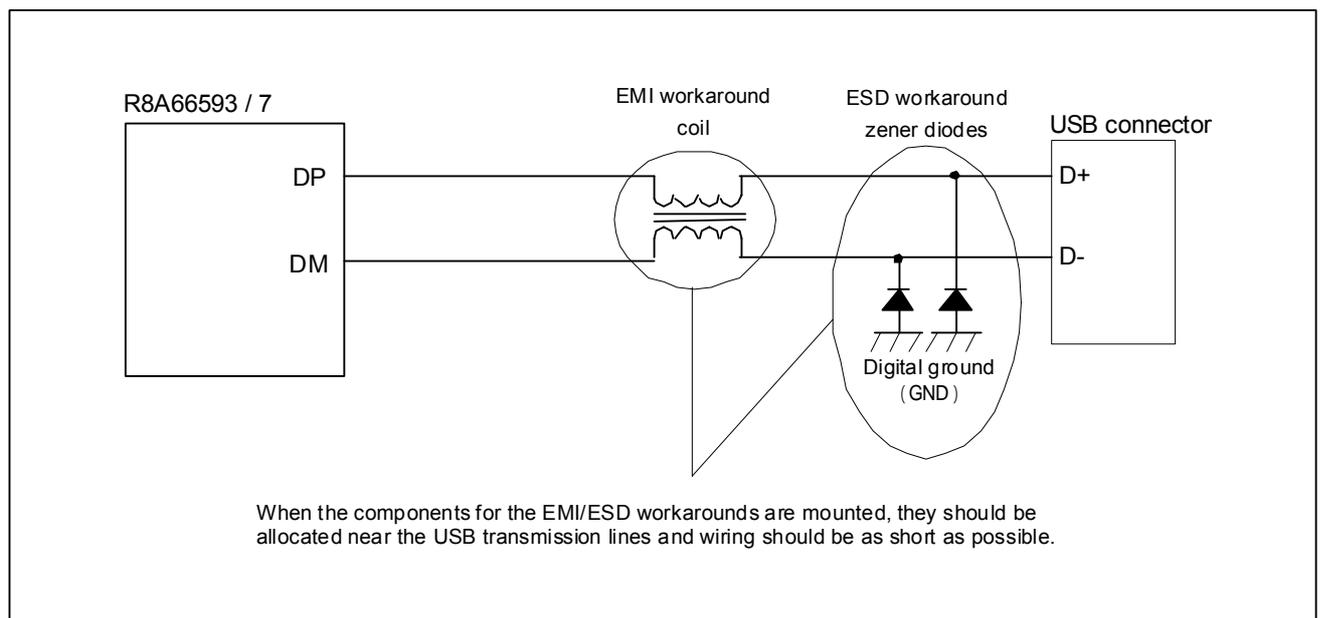


Figure 9 Connection Example When Components for EMI/ESD Workarounds are Used

Website and Support

Renesas Electronics Website

<http://www.renesas.com/>

Inquiries

<http://www.renesas.com/inquiry>

All trademarks and registered trademarks are the property of their respective owners.

Revision History

| Revision | Date | Description | |
|----------|---------------|-------------|---|
| | | Page | Summary |
| 1.0RC1 | July 28, 2008 | - | First edition issued |
| 1.0RC2 | July 31, 2008 | all | "function" -> "peripheral" |
| | | P5 | Figure1 change FONT |
| | | P6 | Table3 delete VDD |
| | | P2 | Table1 (E8) -> (H1) |
| | | all | "USB power switch IC" -> "USB power supply switch IC" |
| | | P12 | Figure9 coil -> zener diodes |
| | | P3 | Figure1 "DP0/DM0" -> "DP0,DM0" |
| | | P3 | Figure1 "Mini-AB" -> "Micro-AB" |
| | | all | "resistance" -> "resistor" |
| 2.00 | Dec.7 ,2012 | - | Add R8A66593 information |
| | | P.2 | Add Table 1.1 |
| | | P.12 | Figure7.1 delete Pin number of DP and DM. |
| | | - | UpdateR Nummer: REJ05F0024 ->R19AN0016EJ0200 |

General Precautions in the Handling of MPU/MCU Products

The following usage notes are applicable to all MPU/MCU products from Renesas. For detailed usage notes on the products covered by this manual, refer to the relevant sections of the manual. If the descriptions under General Precautions in the Handling of MPU/MCU Products and in the body of the manual differ from each other, the description in the body of the manual takes precedence.

1. Handling of Unused Pins

Handle unused pins in accord with the directions given under Handling of Unused Pins in the manual. The input pins of CMOS products are generally in the high-impedance state. In operation with an unused pin in the open-circuit state, extra electromagnetic noise is induced in the vicinity of LSI, an associated shoot-through current flows internally, and malfunctions occur due to the false recognition of the pin state as an input signal become possible. Unused pins should be handled as described under Handling of Unused Pins in the manual.

2. Processing at Power-on

The state of the product is undefined at the moment when power is supplied.

The states of internal circuits in the LSI are indeterminate and the states of register settings and pins are undefined at the moment when power is supplied.

In a finished product where the reset signal is applied to the external reset pin, the states of pins are not guaranteed from the moment when power is supplied until the reset process is completed.

In a similar way, the states of pins in a product that is reset by an on-chip power-on reset function are not guaranteed from the moment when power is supplied until the power reaches the level at which resetting has been specified.

3. Prohibition of Access to Reserved Addresses

Access to reserved addresses is prohibited.

The reserved addresses are provided for the possible future expansion of functions. Do not access these addresses; the correct operation of LSI is not guaranteed if they are accessed.

4. Clock Signals

After applying a reset, only release the reset line after the operating clock signal has become stable. When switching the clock signal during program execution, wait until the target clock signal has stabilized.

When the clock signal is generated with an external resonator (or from an external oscillator) during a reset, ensure that the reset line is only released after full stabilization of the clock signal. Moreover, when switching to a clock signal produced with an external resonator (or by an external oscillator) while program execution is in progress, wait until the target clock signal is stable.

5. Differences between Products

Before changing from one product to another, i.e. to one with a different type number, confirm that the change will not lead to problems.

The characteristics of MPU/MCU in the same group but having different type numbers may differ because of the differences in internal memory capacity and layout pattern. When changing to products of different type numbers, implement a system-evaluation test for each of the products.

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
 3. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from such alteration, modification, copy or otherwise misappropriation of Renesas Electronics product.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots etc.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; and safety equipment etc.
Renesas Electronics products are neither intended nor authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems, surgical implantations etc.), or may cause serious property damages (nuclear reactor control systems, military equipment etc.). You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application for which it is not intended. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for which the product is not intended by Renesas Electronics.
 6. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You should not use Renesas Electronics products or technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. When exporting the Renesas Electronics products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, who distributes, disposes of, or otherwise places the product with a third party, to notify such third party in advance of the contents and conditions set forth in this document, Renesas Electronics assumes no responsibility for any losses incurred by you or third parties as a result of unauthorized use of Renesas Electronics products.
 11. This document may not be reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.

2880 Scott Boulevard Santa Clara, CA 95050-2554, U.S.A.
Tel: +1-408-588-6000, Fax: +1-408-588-6130

Renesas Electronics Canada Limited

1101 Nicholson Road, Newmarket, Ontario L3Y 9C3, Canada
Tel: +1-905-898-5441, Fax: +1-905-898-3220

Renesas Electronics Europe Limited

Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH

Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-65030, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.

7th Floor, Quantum Plaza, No.27 ZhiChunLu Haidian District, Beijing 100083, P.R.China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.

Unit 204, 205, AZIA Center, No.1233 Lujiazui Ring Rd., Pudong District, Shanghai 200120, China
Tel: +86-21-5877-1818, Fax: +86-21-6887-7858 / -7898

Renesas Electronics Hong Kong Limited

Unit 1601-1613, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2886-9318, Fax: +852-2886-9022/9044

Renesas Electronics Taiwan Co., Ltd.

13F, No. 363, Fu Shing North Road, Taipei, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.

80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.

Unit 906, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics Korea Co., Ltd.

11F., Samik Lavied' or Bldg., 720-2 Yeoksam-Dong, Kangnam-Ku, Seoul 135-080, Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5141