

RAA271084 Board Layout Guidelines

Introduction

This application note provides guidelines for the RAA271084 board layout.

The RAA271084 is a general-purpose power management integrated circuit (PMIC) with a high voltage front-end, optimized for providing MCU power in automotive applications. The RAA271084 contains a high voltage primary buck/boost controller, a low voltage synchronous buck controller, and five low-dropout linear regulators (LDO), two of which can be used as trackers. The RAA271084 is available in a 48-lead SCQFN or 48-lead LQFP-EP. Proper PCB layout is an important design practice to ensure a satisfactory electrical and thermal performance.

Contents

1.	RAA271084 Pinout and PCB Footprint	2
2.	RAA271084 PCB Layout Guidelines	3
2.1	DCDC1 and DCDC2 Power Stage Components	3
2.2	MOSFET Gate Drive Traces	4
2.3	DCDC1 and DCDC2 Bootstrap Components	4
2.4	DCDC1 and DCDC2 Current Sensing	6
2.5	RAA271084 Ground	6
2.6	Output Voltage Feedback Traces	7
2.7	Other Components and PCB Routing	7
3.	Quick Summary of the PCB Layout Practice	7
4.	Revision History	8

1. RAA271084 Pinout and PCB Footprint

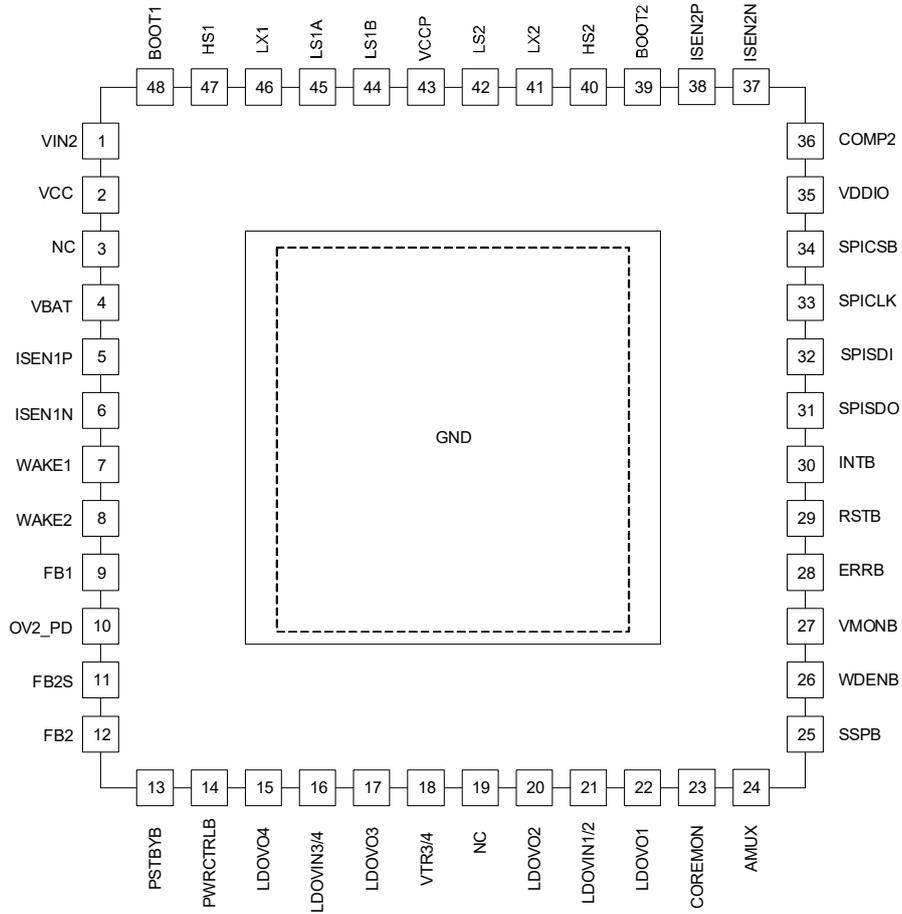


Figure 1. Pin Assignments - Top View

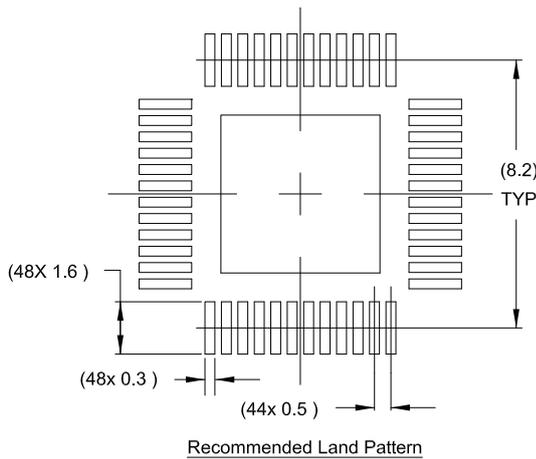


Figure 2. Recommended Land Pattern – Q48.7x7D

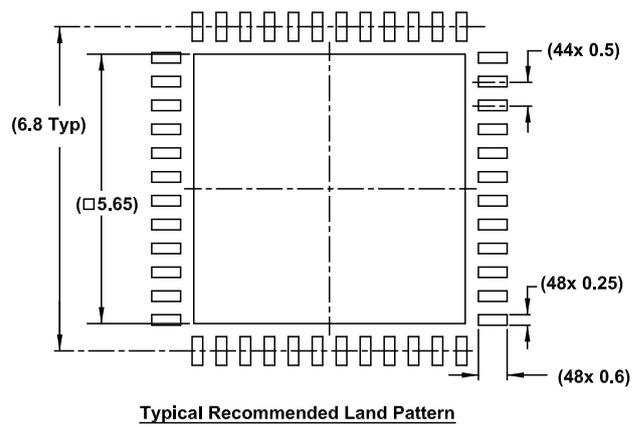


Figure 3. Typical Recommended Land Pattern – L48.7x7N

2. RAA271084 PCB Layout Guidelines

For the DCDC1 and DCDC2 switching regulators, the power delivery loop consists of the input capacitors C_{IN} , the MOSFETs, the LX switching node pin, the inductor L, the output capacitor C_{OUT} , and the GND pin. As [Figure 1](#) illustrates, it is important to make the power delivery or current flow loop as small as possible. The PCB connecting traces among those components and pins should be direct, short, and wide. The PCB copper should be wide enough to minimize the current conduction loss and the parasitic inductance. Multiple solid ground layers are helpful to reduce the current flow resistance, have better thermal dissipation, and for a good EMI performance. Use enough vias to connect all the GND layers.

2.1 DCDC1 and DCDC2 Power Stage Components

[Figure 4](#) illustrates a typical power stage components placement and layout pattern with respect to RAA271084. Dual FETs in one package can be used while the illustration uses single/standalone FET. The components are arranged to minimize the current flow path/loop, with the input capacitor, low side MOSFET, and the output capacitor connected with low impedance ground copper plane. A solid ground plane is helpful for a good EMI performance, current conduction, and thermal dissipation. Even if the DCDC1 and DCDC2 components cannot be placed close to each other, their placement should follow the illustrated pattern in [Figure 5](#), as shown in the pink dot line frame.

- The input capacitor, low-side FET, and output capacitor should have low impedance ground connection.
- Use the wide and/or multiple layer ground copper plane to create low impedance current flow path.
- Minimize the copper area connecting to the inductor two terminals.
- Use the wide copper plane for the MOSFET to reduce the PCB parasitic and to have better thermal dissipation for the MOSFET.
- If there are multiple ground layers, use enough vias connecting them together.

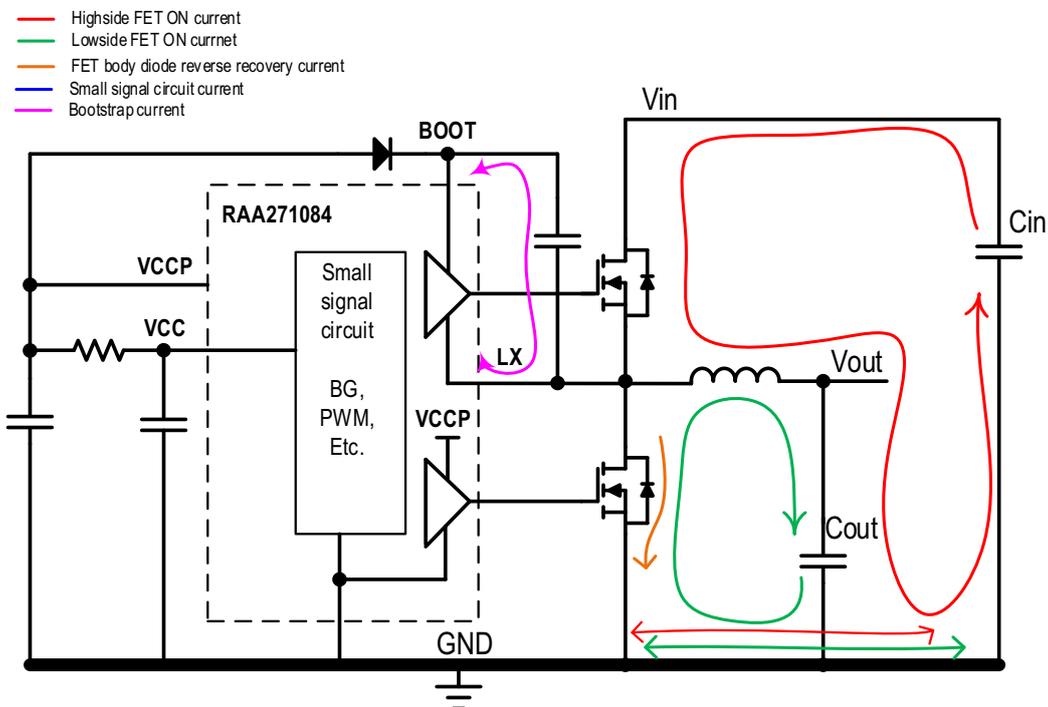


Figure 4. Component Placement and Layout Pattern

2.2 MOSFET Gate Drive Traces

Run MOSFET gate drive traces on a dedicated layer.

- For DCDC1, run HS1 and LX1 traces in parallel.
- For DCDC2, run HS2 and LX2 traces in parallel.

Use at least 10mil width for these traces. For all other signals, use ground copper to shield them from or keep distance from HS, LS, and LX via/trace/copper because they are noisy.

2.3 DCDC1 and DCDC2 Bootstrap Components

Place the bootstrap capacitor (and the resistor in series if any) close to BOOT pin and LX pin. Minimize the loop and PCB trace of Boot pin > Boot trace > Cboot > LX trace.

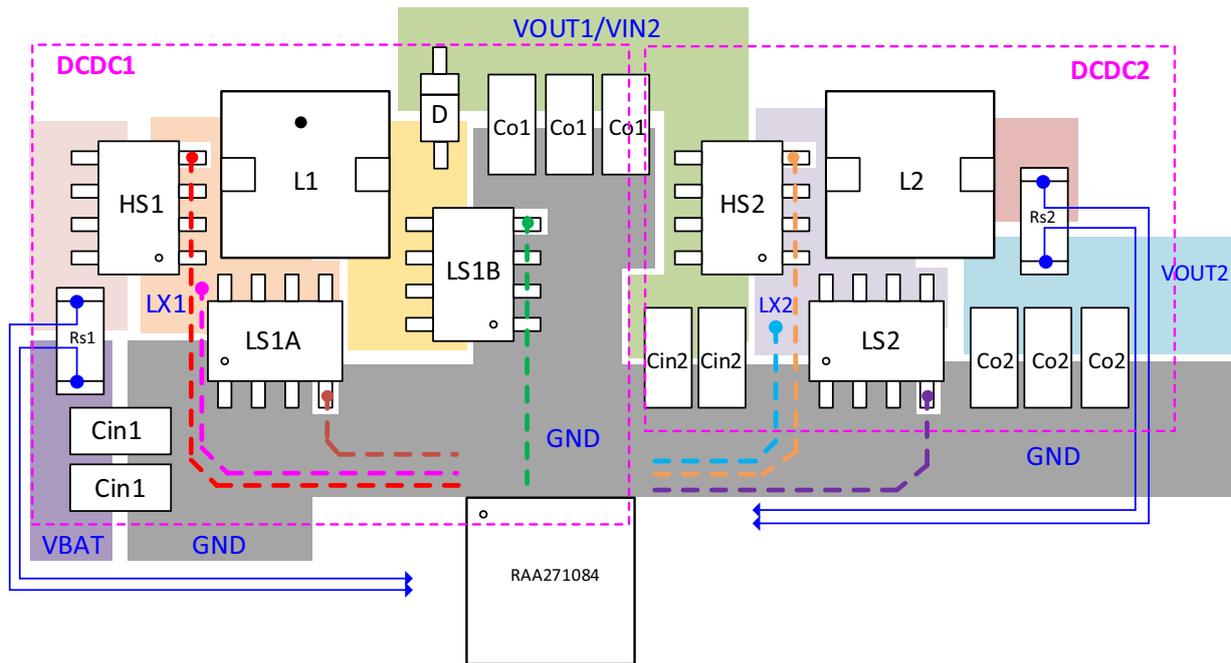


Figure 5. Bootstrap Components (1 of 2)

Use at least 10mil width trace for the Boot trace and LX trace to conduct the high-side FET driving current.

For all other signals, use ground copper to shield them or keep distance from VCCP, BOOT, and LX traces, because they carry the high-side FET driving current and are noisy.

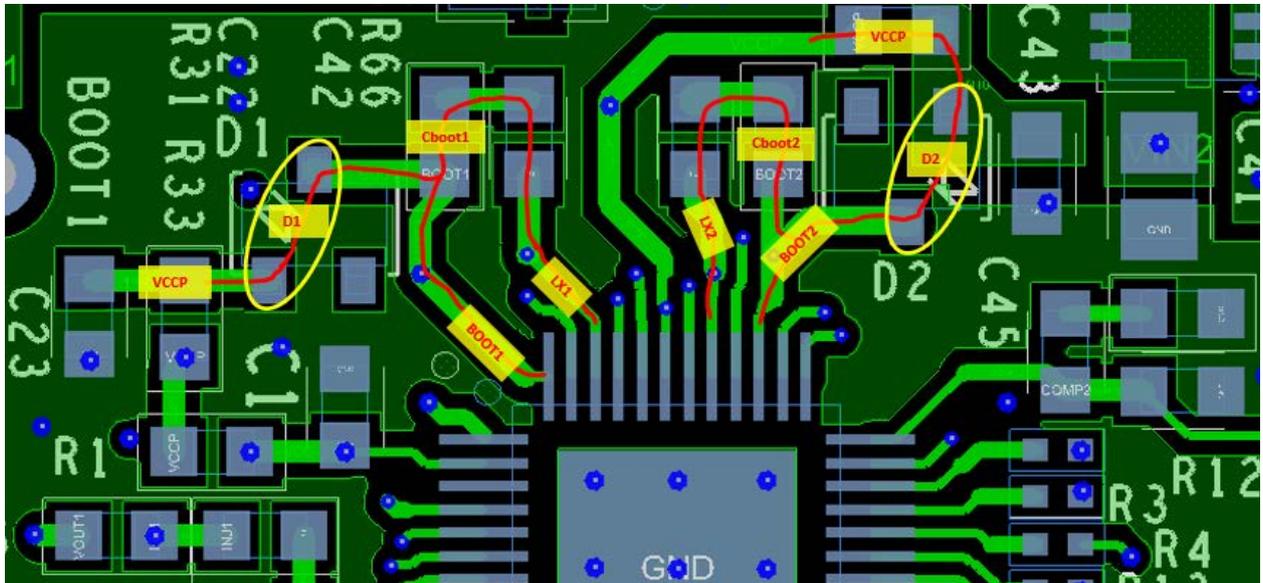
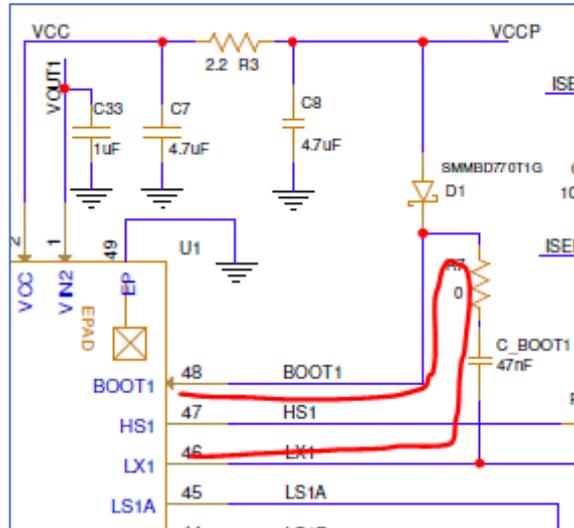


Figure 6. Bootstrap Components (2 of 2)

2.4 DCDC1 and DCDC2 Current Sensing

Run the current-sensing traces ISEN1P/ISEN1N (or ISEN2P/ISEN2N) from the current-sensing shunt resistor to RAA271084 in parallel. Shield them with ground copper. Place the RC filter resistor and capacitor close to the RAA271084 package.

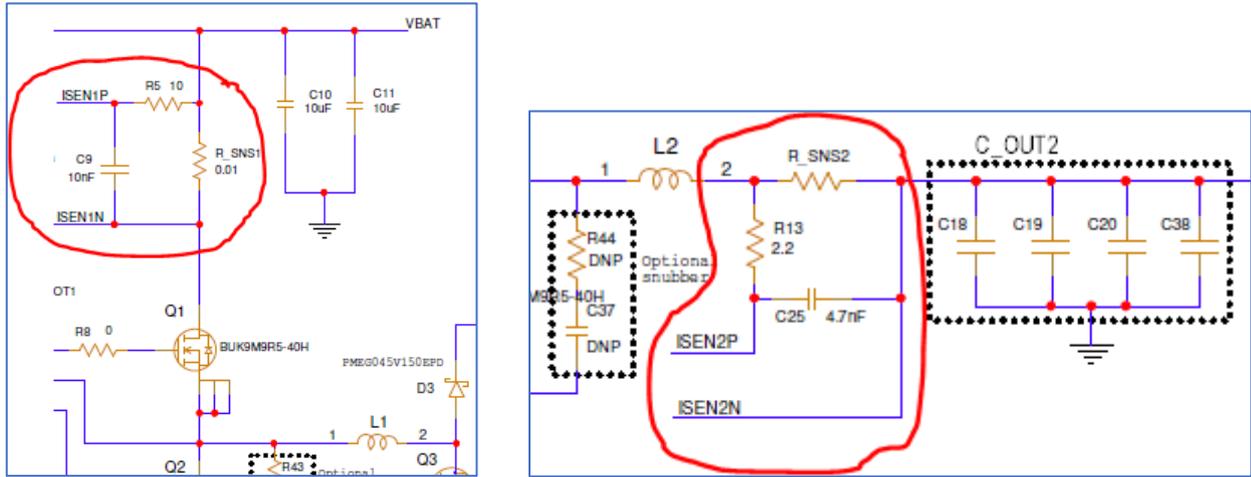


Figure 7. Current-Sensing Traces

2.5 RAA271084 Ground

Use multiple vias connecting the RAA271084 ground pad to the internal ground copper plane for lower ground impedance and better thermal dissipation.

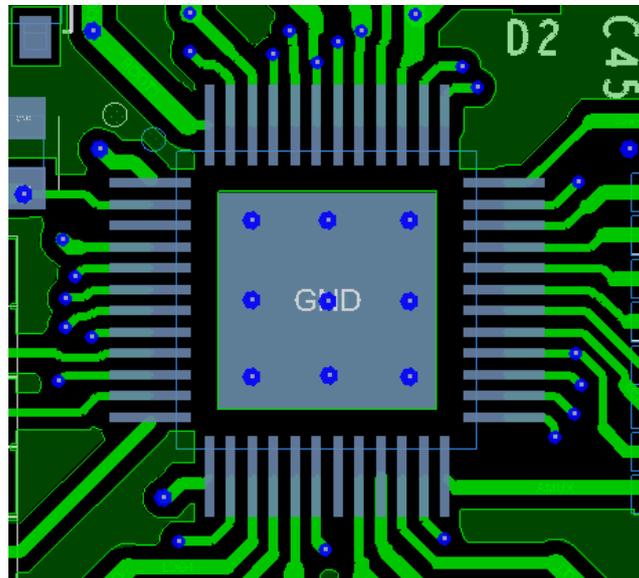


Figure 8. Ground Pad

2.6 Output Voltage Feedback Traces

Run the FB1 and FB2/FB2S output voltage feedback away from the FET gate drive related traces (HS, LS, LX, BOOT, VCCP). Also, stay away from any high-speed digital signals such as SPI communication lines. Shield them with ground copper. Place the FB2/FB2S voltage divider resistors close to RAA271084 package.

2.7 Other Components and PCB Routing

- Place the decoupling capacitors close to VBAT, VCC, VCCP, VIN2, VDDIO, VTR3/4, LDOIN1/2, and LDOIN3/4 pins with a good ground copper connection.
- Place DCDC2 loop compensation components close to the COMP2 pin, with good ground copper connection.
- All other digital or logic signals such as WAKE1/2, SSPB, RSTB, and INTB are not a big concern in the PCB layout.

As shown in Figure 9, place the resistors and capacitors close to RAA271084, connect them to the ground copper surrounding the RAA271084, and connect the ground copper to the ground copper on other layers multiple vias.

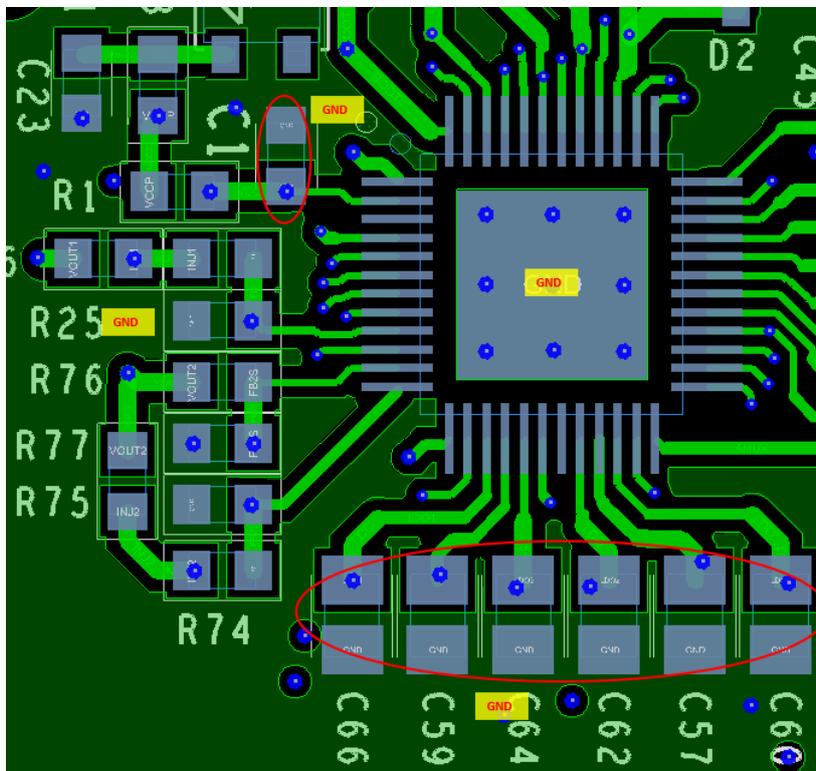


Figure 9. PCB Routing

3. Quick Summary of the PCB Layout Practice

- Place the DCDC1 and DCDC2 power stage components in a compact fashion with low impedance copper plane and good ground connection.
- Route FET gate drive related traces with short, wide traces, and avoid any sensitive signals.
- Route output voltage feedback sensing traces to the load point and the high frequency ceramic bank to minimize the feedback noise. Shield or stay away from the switching related signals.
- Route the current sensing traces in parallel and shield with ground copper.
- Use enough vias connecting to the different layers and enough PCB copper width for low impedance current flow and minimized parasitic inductance

4. Revision History

Revision	Date	Description
1.00	Jun 23, 2025	Initial release.

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall be responsible for determining what licenses are required from any third parties, and obtaining such licenses for the lawful import, export, manufacture, sales, utilization, distribution or other disposal of any products incorporating Renesas Electronics products, if required.
5. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
6. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
 - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
 - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
7. No semiconductor product is absolutely secure. Notwithstanding any security measures or features that may be implemented in Renesas Electronics hardware or software products, Renesas Electronics shall have absolutely no liability arising out of any vulnerability or security breach, including but not limited to any unauthorized access to or use of a Renesas Electronics product or a system that uses a Renesas Electronics product. RENESAS ELECTRONICS DOES NOT WARRANT OR GUARANTEE THAT RENESAS ELECTRONICS PRODUCTS, OR ANY SYSTEMS CREATED USING RENESAS ELECTRONICS PRODUCTS WILL BE INVULNERABLE OR FREE FROM CORRUPTION, ATTACK, VIRUSES, INTERFERENCE, HACKING, DATA LOSS OR THEFT, OR OTHER SECURITY INTRUSION ("Vulnerability Issues"). RENESAS ELECTRONICS DISCLAIMS ANY AND ALL RESPONSIBILITY OR LIABILITY ARISING FROM OR RELATED TO ANY VULNERABILITY ISSUES. FURTHERMORE, TO THE EXTENT PERMITTED BY APPLICABLE LAW, RENESAS ELECTRONICS DISCLAIMS ANY AND ALL WARRANTIES, EXPRESS OR IMPLIED, WITH RESPECT TO THIS DOCUMENT AND ANY RELATED OR ACCOMPANYING SOFTWARE OR HARDWARE, INCLUDING BUT NOT LIMITED TO THE IMPLIED WARRANTIES OF MERCHANTABILITY, OR FITNESS FOR A PARTICULAR PURPOSE.
8. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
12. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
13. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
14. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Disclaimer Rev.5.0-1)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/