

signal will appear as input to the ground referenced video differential amplifier, EL5172.

CMV Conversion Voltage (V_{CONVT})

The receiver solution uses a differential amplifier across the cable, allowing the CMV on the shield to have light loading. This configuration minimizes CMV conversion to the video signal. If the coax cable shield is viewed as a simple resistor (R_{SHIELD}), the line CMV currents ($I_{LINECMV}$) running through the cable shield will generate a differential voltage across the cable. This differential voltage is called CMV Conversion Voltage (V_{CONVT}).

$$V_{CONVT} = I_{LINECMV} \times R_{SHIELD} \quad (EQ. 1)$$

Equation 1 is CMV generated by the ground differentials and is added to the video signal. Thus, you will need to keep this line CMV current to a minimum by limiting the loading.

Addressing the high frequency noise induced onto the shield is simple. As in Figure 1, a single ceramic capacitor (CS) to ground of about 0.1 μ F, will short high frequency noise while not having any loading effect on the line noise.

Reducing the $V_{LINECMV}$

If the shield is terminated through a resistor to ground, R_S , the noise voltage can be reduced by lowering the $I_{LINECMV}$. We cannot go directly to ground without developing the full differential ground voltage across the shield as previously stated. We cannot eliminate it but we can limit this $I_{LINECMV}$ to where CMV conversion voltage is not noticeable on the video display.

Determining R_S

The shield impedance is typically about 15 times smaller than the conductor impedance. Since the conductor is typically 24 Ω /1kft, the shield impedance would be about 1.67 Ω /1kft. We need to maintain maximum CMV range of $\pm 3V$ as noted in "Receiver CMV Rejection" on page 1. It was determined, empirically, back in the B/W TV days, if less than 20mV of CMV on a 1V video signal is maintained, the CMV impact would not be visible on a display.

As previously stated in "CMV Conversion Voltage (V_{CONVT})" on page 2, Equation 2 shows:

$$V_{CONVT} = I_{LINECMV} \times R_{SHIELD} \quad (EQ. 2)$$

Let's pick a V_{CONVT} that would not impact the signal but keep R_S small enough to suppress noise voltage, say 4mV:

$$V_{CONVT} = I_{NOISE} \times R_{SHIELD} \quad (EQ. 3)$$

$$4mV = I_{NOISE} \times 1.67\Omega$$

$$I_{LINECMV} = 2.4mA$$

$$R_S = CMV / (I_{LINECMV})$$

$$R_S = 3V / 2.4mA = 1.25k\Omega$$

The R_S shield termination is 1.25k Ω to prevent noise pick-up.

The receiver and transmitter CMV are both limited to 2.4mA if we use $R_S = 1.25k\Omega$. If you use both the transmitter rejection and receiver rejection circuits, then the CMV will divide proportionally to the CMV input range of both circuits. Thus, you will extend the CMV rejection range when using both the transmitter and receiver rejection circuits together.

Transmitter CMV Rejection

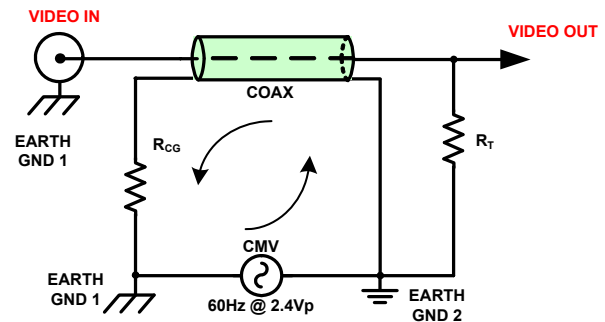


FIGURE 2. CONCEPT OF GROUND DIFFERENCE

If the system CMV can be detected at the transmitter, we can use this level to compensate and offset the video before it is sent to the receiver. Figure 2 shows a simple loop concept which places the CMV across R_{CG} . Now we can buffer this CMV and apply it back to the transmitting Video Amp. This will add the CMV to the incoming video.

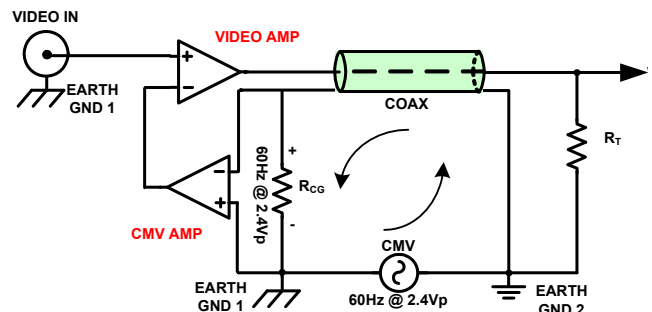


FIGURE 3. CONCEPT OF TRANSMITTER REJECTION CIRCUIT

DETAILED TRANSMITTER CIRCUIT

For NTSC/PAL, selected were the EL5260 and EL5261, dual channel 200MHz low-power current feedback amplifiers for their bandwidth, supply range and footprint (Figure 4).

For RGB, selected were the EL5363, a triple, 500MHz bandwidth video amp, and the EL5160, a single op amp for the CMV amp (Figure 5).

This detailed discussion will be for the NTSC/PAL implementation (single op amp) as the RGB is a minor

extension of the NTSC design. We will discuss those unique differences in detail in the following sections.

NTSC/PAL Rejection Network (Figure 4)

To detect the Earth CMV and compensate the incoming video signal, we used an inverting unity gain amplifier (CMV Amp, A_1). By generating the -CMV signal at the output of A_1 , the -CMV is summed with the video input at the Video Amp stage, A_2 .

NOTE: A_1 's inputs are at the local virtual ground and the output will drive to maintain this virtual ground. Thus, the system's CMV will appear across RCG.

We apply the output of A_1 , -CMV, to the difference node, '-' input of A_2 . This effectively inverts the -CMV to +CMV. The output of A_2 is shown in Equation 4:

$$A2_{\text{OUTPUT}} = 2 \times \text{Video}_{\text{IN}} + \text{CMV} \quad (\text{EQ. 4})$$

The coax shield on the transmitter end will have the same CMV as the coax shield on the receiver end. Now, with the input to the coax being $\text{Video}_{\text{IN}} + \text{CMV}$, the receiver end of the coax to the shield is just the Video_{IN} with the CMV compensated.

A_2 's configuration is the typical gain of 2 to overcome the output termination loss at the receiver.

The transmitter end of the cable shield should be terminated to prevent noise pick-up from a floating shield. Since we use a unity gain buffer to detect the Line Frequency CMV voltage or V_{LINECMV} , we need to ensure the receiver CMV current termination is matched with the transmitter current termination of $I_{\text{LINECMV}} = 2.4\text{mA}$.

The selected EL5261 is a dual supply, dual video amp that can be used for both the CMV amplifier as well as the video amp. Since we need to balance the I_{LINECMV} at both ends, use a DC termination resistor of $1\text{k}\Omega$ to generate a CMV within the limits at the transmitter and the receiver ends ($\text{CMV} = \pm 2.4\text{V}$). The $1\text{k}\Omega$ would also limit the current to 2.4mA , preventing CMV conversion to diff signal in the shield as described previously in the "Determining R_S " section on page 2.

Thus, looking back from the transmitter end of the coax shield, the impedance must be $1\text{k}\Omega$. Since A_1 's input is at the local ground, you have RCG of $1\text{k}\Omega$ to ground and the shield source to ground. Thus, an additional R_S is not needed and is left open. For AC termination and HF filtering, we used a standard $0.1\mu\text{F}$ for C_S to local ground.

RGB Design

We only need to detect the Line Frequency CMV by connecting the three shields in the same circuit as with the NTSC/PAL design (Figure 4).

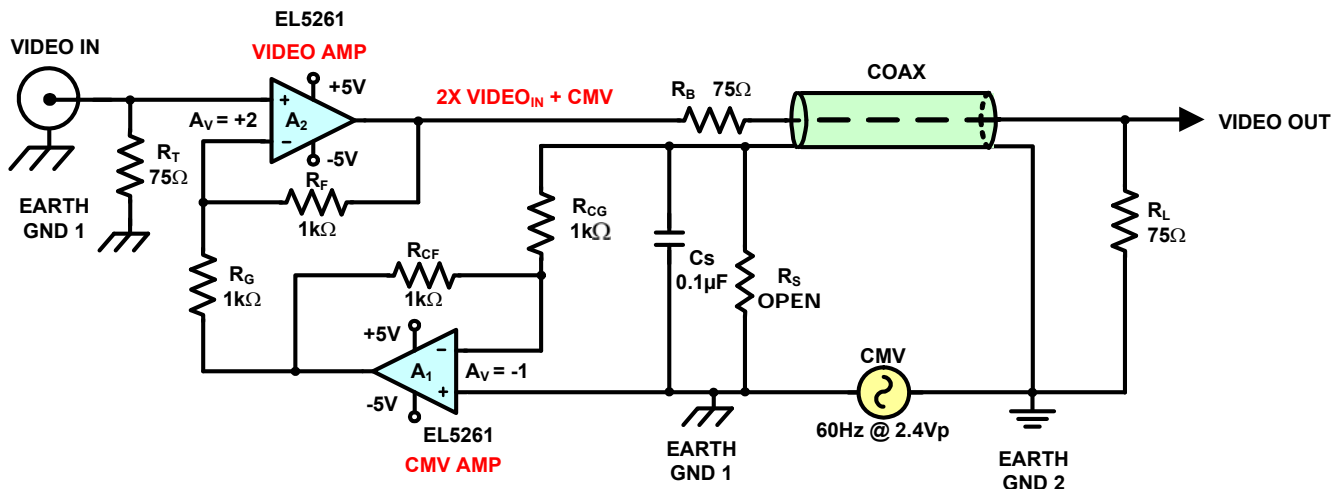


FIGURE 4. NTSC/PAL DESIGN

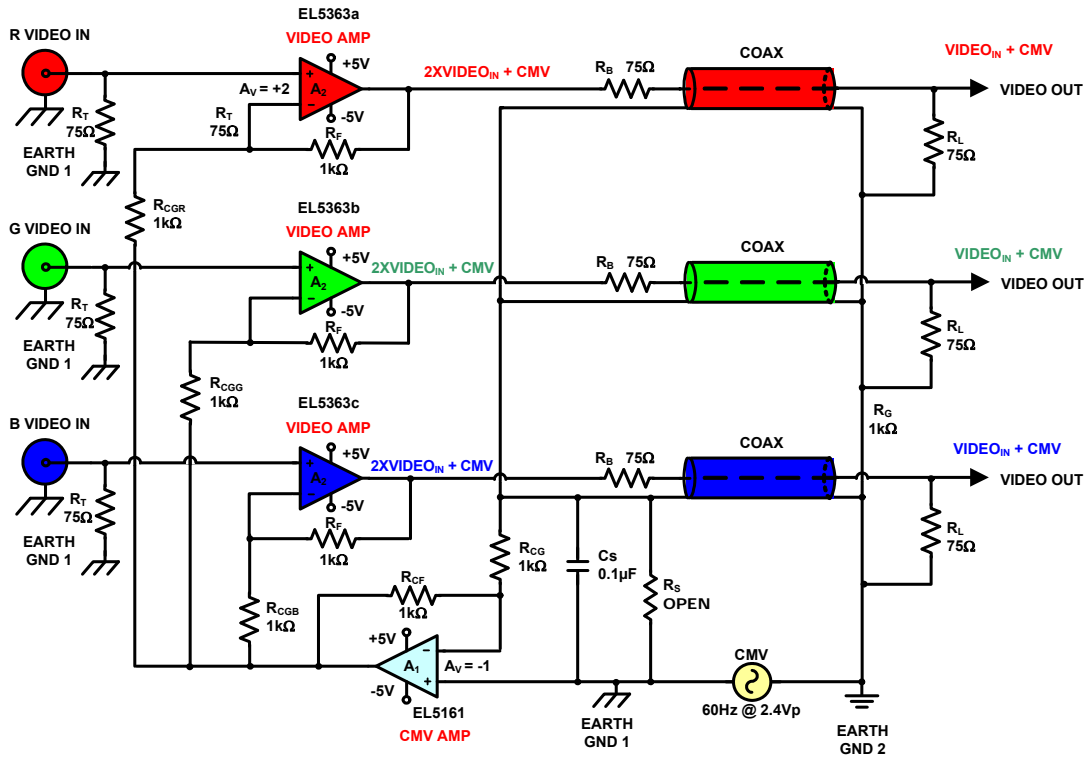


FIGURE 5. COMPLETE RGB TRANSMITTER REJECTION NETWORK

Test Results from Figure 5 for CMV Cable Driver

Before Rejection (Figure 6)

Explain: Which circuit did you test to get these results?

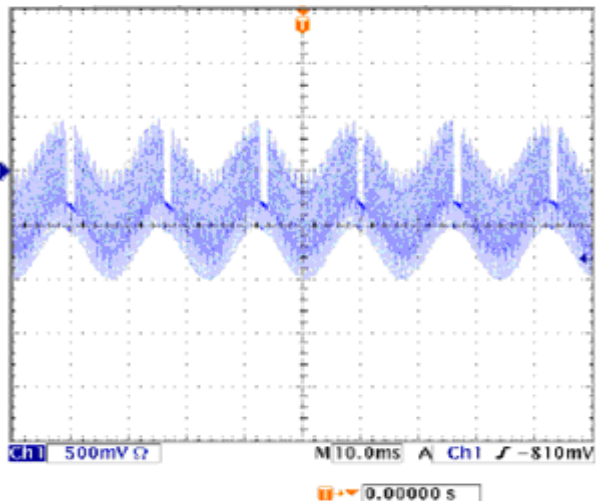


FIGURE 6. VIDEO WITHOUT CMV REJECTION

After Rejection (Figure 7)

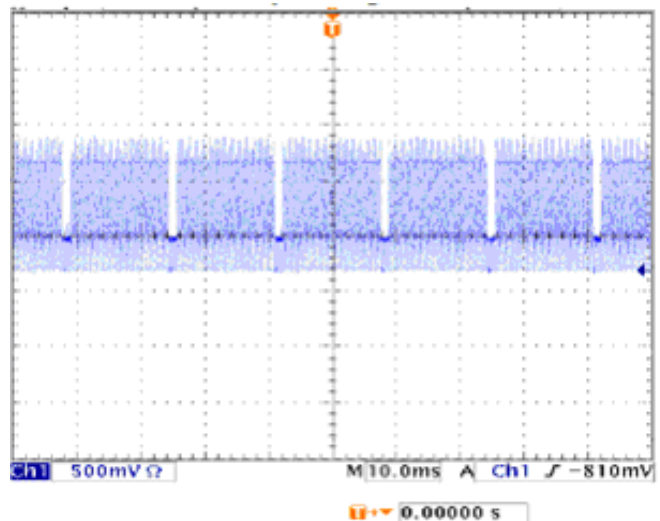


FIGURE 7. VIDEO WITH CMV REJECTION

VIDEO ISOLATION TRANSFORMER FOR UP TO 120V_{AC} CMV

The NTSC/PAL isolation transformer circuit uses a low cost Panasonic ELF-17N030A Iso-transformer in current mode with a voltage mode op amp. The basic circuit is a typical input impedance match with AC-coupling at the front-end (Figure 8). The video is fed to the

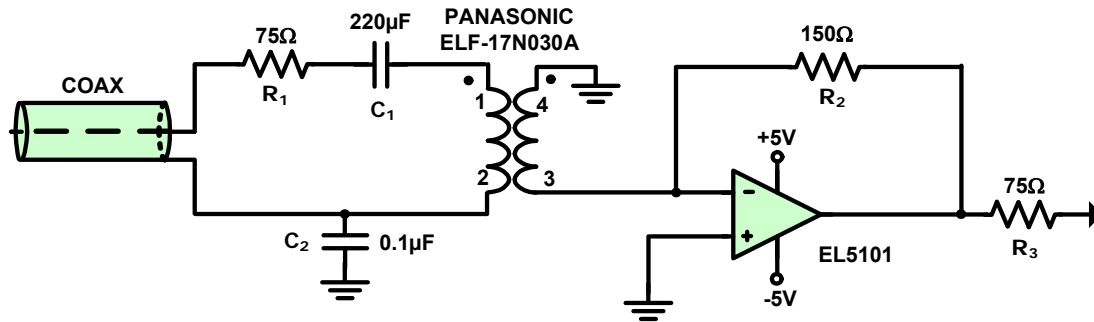


FIGURE 8. DUAL SUPPLY 120V_{CMV} - HV ISOLATION TRANSFORMER

Iso-transformer and to a simple voltage amplifier. In this example, we used the EL5101, a 200MHz Slew Enhanced Voltage Feedback Amplifier (VFA).

DUAL SUPPLY OP AMP CIRCUIT DETAILS (Figure 8)

The video signal coming into the receiver must be properly terminated to the cable impedance. Since the transformer will appear to the video as a short, we can use the standard 75Ω in series with the primary of the transformer.

Any DC on the incoming video will limit the transformer linearity. This DC can cause early saturation of the core and induce distortion. To block the DC but allow the video, you need a large series capacitor. It is common to use a 220μF coupling capacitor for such applications. The transformer input coupling capacitor, C₁, may not be needed if there is only a small DC current across the primary winding.

We still need to consider the common mode HF noise that might be present on the incoming signal. Since the Iso-Transformer is a differential receiver, we can easily remove any common mode HF noise by simply connecting the coax shield to the input of the Iso-transformer. Now, connect a 0.1μF ceramic capacitor from the shield/transformer tie point to ground to help to eliminate the HF noise.

Voltage Mode vs Current Mode Amplifier

Why a voltage mode feedback amplifier (VFBA) and not a Current mode (CFBA) when the Iso-transformer is a current device? The input to the amplifier is effectively 75Ω. The amplifier's gain needs to be 2 to recover the impedance matching loss. The feedback resistor would be 150Ω for a gain of 2. If used with a current mode FBA, this would cause the amplifier to become unstable, as with a gain of two, its gain bandwidth would be in the GHz region and any noise could cause the amplifier to break into HF oscillations.

We need the low impedance to maintain the bandwidth, 0MHz to 5MHz, of the Iso-transformer. Since it is easier to peak the higher frequency, we focused on a transformer with the better low frequency response and with minimal HF loss. The transformer selected has a good response at low bandwidth but a -6dB/Dec roll off

at the high end of the video signal BW. We selected the Isolation Transformer (Panasonic ELF17N030A) for its low input impedance characteristic, good bandwidth and high isolation, up to 120V_{AC}.

Operation

The input and the Iso-Transformer feeds the voltage mode EL5101 forming a gain of 2 with the feedback resistor of 150Ω. The EL5101 gain of 2 has a gain bandwidth of 75MHz, which shows there are more than enough BW, but not so much as to induce instabilities. The amplifier cancels the primary current by driving the secondary winding with a canceling current as it maintains its input delta at 0V. Some small error current will remain as the amplifier's inputs are not perfect and its gain-BW is not perfectly flat over the 0MHz to 5MHz. Yet, the current is small and will not cause saturation of the core, even with a full power signal applied. If you saturate the core, you lose the signal and generate signal distortion.

However, operating the voltage mode FBA in current mode induces heavy loading on the secondary of the transformer since you have a near short on the transformer's secondary. This loading of the secondary will increase the leakage inductance on the primary. This leakage inductance is effectively in series with the input signal. As a series inductance, it will attenuate high frequencies and reduce the bandwidth by about 6dB at 5MHz. This BW loss can be recovered with a peaking network in the feedback loop resulting in a very flat frequency response out to 5MHz.

The peaking circuit needs to be in the feedback loop but also must be isolated from the op amp's output and input (Figure 9). Using two 75Ω series resistors, R₂ and R₃, to replace the 150Ω effectively isolates the rejection network from the '-' input and output of the EL5101 while maintaining the gain of 2. R₂ + R₃ is 150Ω and functions as the feedback resistor to the amplifier summing node. The R₁ is 75Ω and is the input cable termination and the summing node gain resistor for the op amp.

The peaking circuit needs to add gain at the high end to recover the losses induced by the leakage inductance, -6dB at 5MHz. Connecting the series R₄ (15Ω) and C₃ (1500μF) to ground from the common point, forms the

RC peaking circuit. This circuit will recover the -6dB and give us a flat response from 0MHz to 5MHz.

SINGLE SUPPLY OP AMP CIRCUIT DETAILS (Figure 10)

There is a second variation of this design using a single +5V supply for the EL8101 op amp. The coax input to single-ended single supply +5V op amp will require you offset the input to the op amp to prevent clipping. We need to level shift the iso-transformer output to the mid range of the op amp's CMV. If we level shift the iso-transformer off ground to about 2V, the EL8101 amplifier will be able to support unipolar swings. The circuit description is the same as for the dual supply except for the level shifter.

By using a simple voltage divider, R_6 (2k Ω) and R_7 (3k Ω) from +5V to ground, we can generate a level shift of 2V. To insure stability and not induce more CMV on the input, we bypass R_7 with a large 220 μ F cap.

NOTE: The previous circuits are DC-coupled but the Iso-transformer is an AC coupling device so the output will always be at the average value of the input signal. Therefore, you cannot expect the sync tip to be at a fixed DC level since the input video signal is asymmetric and has a signal dependant average value. The amplifier output will have a DC level change (300mV for a standard video 1V_{P-P} signal) if the input video changes from black to white.

Also, this circuit's output DC level change rate is less than 80mV/ms in order to be compatible with typical DC Clamp circuits.

TEST RESULTS

The circuit was tested using a signal generator set to 18V_P at 6MHz with no degradation to the video signal. The actual CMV limitation would be that of the transformer itself, 120V_{AC} line. However, the transformer could withstand 1500VP non-repetitive spikes.

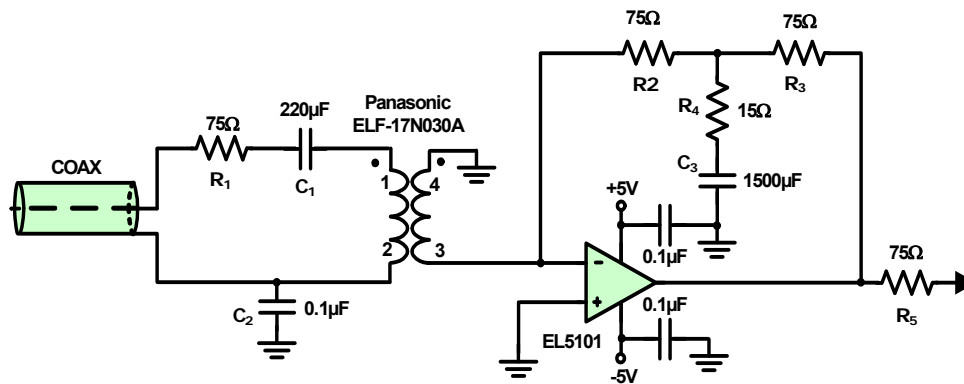


FIGURE 9. DUAL SUPPLY 120V_{CMV} - HV ISOLATION TRANSFORMER

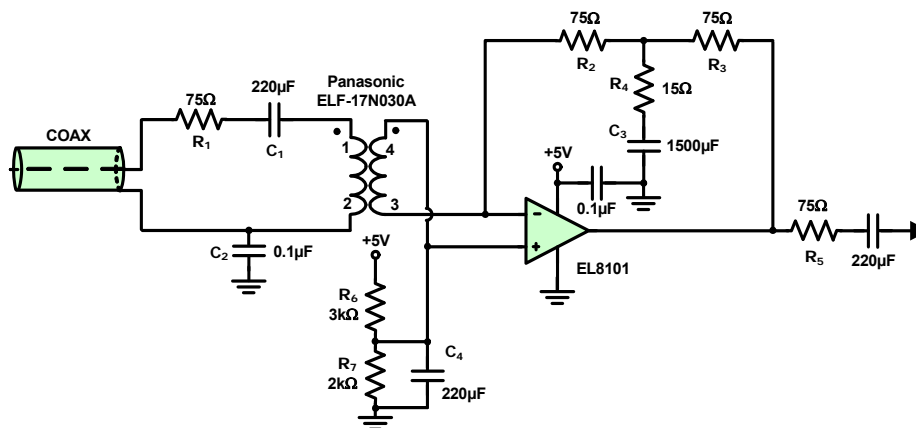


FIGURE 10. COMPLETE SINGLE SUPPLY 120V_{CMV} - HV ISOLATION TRANSFORMER

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338