

To our customers,

Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <http://www.renesas.com>

April 1st, 2010
Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (<http://www.renesas.com>)

Send any inquiries to <http://www.renesas.com/inquiry>.

Not recommended
for new design

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: “Standard”, “High Quality”, and “Specific”. The recommended applications for each Renesas Electronics product depends on the product’s quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as “Specific” without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as “Specific” or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is “Standard” unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - “Standard”: Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - “High Quality”: Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - “Specific”: Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.

(Note 1) “Renesas Electronics” as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.

(Note 2) “Renesas Electronics product(s)” means any product developed or manufactured by or for Renesas Electronics.

HA17902 Series

Quad Operational Amplifier

REJ03D0685-0100
(Previous: ADE-204-045)
Rev.1.00
Jun 15, 2005

Description

The HA17902 is an internal phase compensation quad operational amplifier that operates on a single-voltage power supply and is appropriate for use in a wide range of general-purpose control equipment.

Features


- Wide usable power-supply voltage range and single-voltage supply operation
- Internal phase compensation
- Wide common-mode voltage range and operation for inputs close to the 0 level

Ordering Information


Type No.	Application	Package Code (Previous Code)
HA17902PJ	Car use	PRDP0014AB-A (DP-14)
HA17902FPJ		PRSP0014DF-B (FP-14DAV)
HA17902FPK		PRSP0014DF-B (FP-14DAV)

Not recommended
for new designs

Pin Arrangement

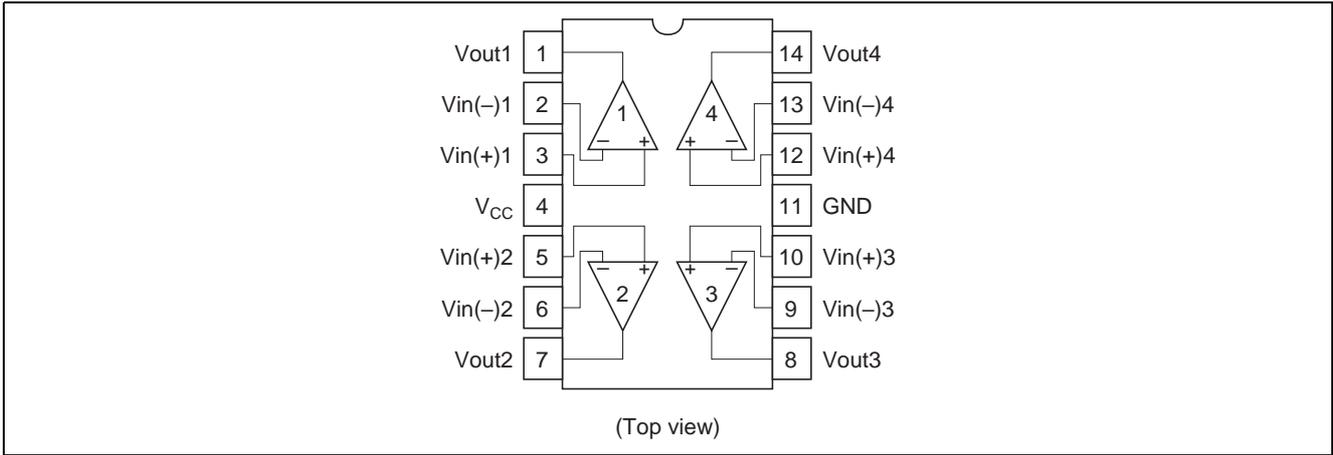

Circuit Structure (1/4)

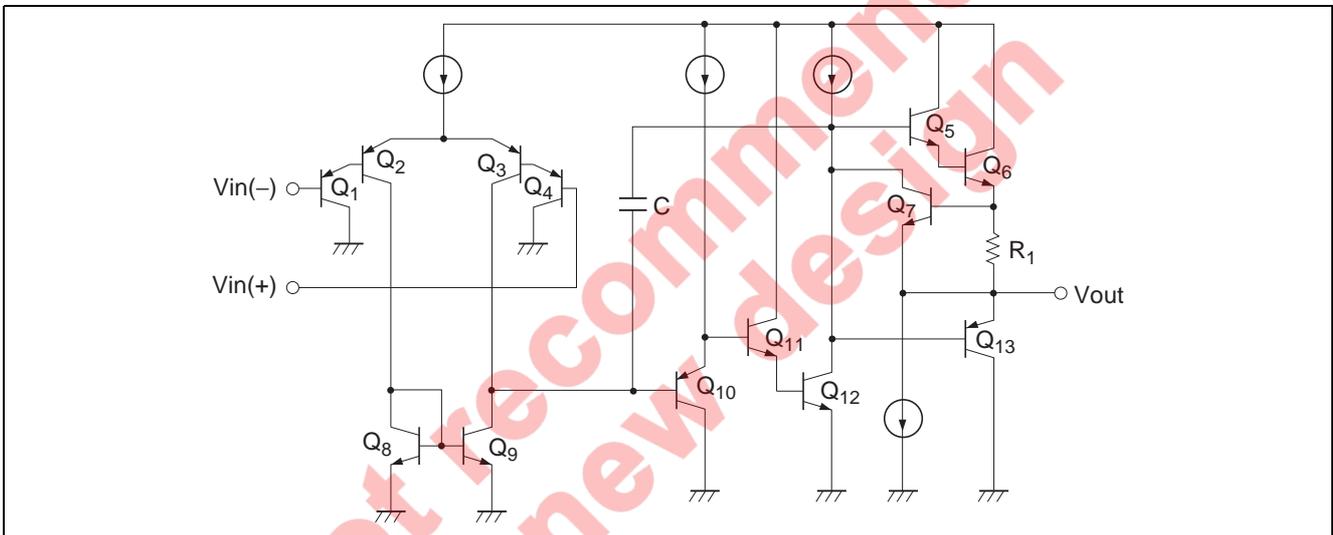

Absolute Maximum Ratings

(Ta = 25°C)

Item	Symbol	HA17902PJ	HA17902 FPJ	HA17902FPK	Unit
Power supply voltage	V _{CC}	28	28	28	V
Sink current	I _{o sink}	50	50	25	mA
Allowable power dissipation	P _T	625* ¹	625* ²	625* ²	mW
Common-mode input voltage	V _{CM}	-0.3 to V _{CC}	-0.3 to V _{CC}	-0.3 to V _{CC}	V
Differential-mode input voltage	V _{in(diff)}	±V _{CC}	±V _{CC}	±V _{CC}	V
Operating temperature	Topr	-40 to +85	-40 to +85	-40 to +125	°C
Storage temperature	Tstg	-55 to +125	-55 to +125	-55 to +150	°C

Notes: 1. These are the allowable values up to Ta = 50°C. Derate by 8.3mW/°C above that temperature.

2. See notes on SOP Package Usage in Reliability section.

Electrical Characteristics 1

(V_{CC} = +15V, Ta = 25°C)

Item	Symbol	Min	Typ	Max	Unit	Test Conditions
Input offset voltage	V _{IO}	—	3	8	mV	V _{CM} = 7.5V, R _S = 50Ω, R _f = 5kΩ
Input offset current	I _{IO}	—	5	50	nA	I _{IO} = I _{I-} - I _{I+} , V _{CM} = 7.5V
Input bias current	I _{IB}	—	30	500	nA	V _{CM} = 7.5V
Power-supply rejection ratio	PSRR	—	93	—	dB	f = 100Hz, R _S = 1kΩ, R _f = 100kΩ
Voltage gain	A _{VD}	75	90	—	dB	R _S = 1kΩ, R _f = 100kΩ, R _L = ∞
Common-mode rejection ratio	CMR	—	80	—	dB	R _S = 50Ω, R _f = 5kΩ
Common-mode input voltage range	V _{CM}	-0.3	—	13.5	V	R _S = 1kΩ, R _f = 100kΩ, f = 100Hz
Maximum output voltage amplitude	V _{OP-P}	—	13.6	—	V	f = 100Hz, R _S = 1kΩ, R _f = 100kΩ, R _L = 20kΩ
Output voltage	V _{OH1}	13.2	13.6	—	V	I _{OH} = -1mA
	V _{OH2}	12	13.3	—	V	I _{OH} = -10mA
	V _{OL1}	—	0.8	1	V	I _{OL} = 1mA
	V _{OL2}	—	1.1	1.8	V	I _{OL} = 10mA
Output source current	I _{o source}	15	—	—	mA	V _{OH} = 10V
Output sink current	I _{o sink}	3	9	—	mA	V _{OL} = 1V
Supply current	I _{CC}	—	0.8	2	mA	V _{in} = GND, R _L = ∞
Slew rate	SR	—	0.19	—	V/μs	f = 1.5kHz, V _{CM} = 7.5V, R _L = ∞
Channel separation	CS	—	120	—	dB	f = 1kHz


Electrical Characteristics 2

(V_{CC} = +15V, Ta = -40 to 125°C)

Item	Symbol	Min	Typ	Max	Unit	Test Conditions
Input offset voltage	V _{IO}	—	—	8	mV	V _{CM} = 7.5V, R _S = 50Ω, R _f = 5kΩ
Input offset current	I _{IO}	—	—	200	nA	V _{CM} = 7.5V, I _{IO} = I _{I-} - I _{I+}
Input bias current	I _{IB}	—	—	500	nA	V _{CM} = 7.5V
Common-mode input voltage range	V _{CM}	0	—	13.0	V	R _S = 1kΩ, R _f = 100kΩ, f = 100Hz
Output voltage	V _{OH}	13.0	—	—	V	I _{OH} = -1mA
	V _{OL}	—	—	1.3	V	I _{OL} = 1mA
Supply current	I _{CC}	—	—	4	mA	V _{in} = GND, R _L = ∞

Test Circuits

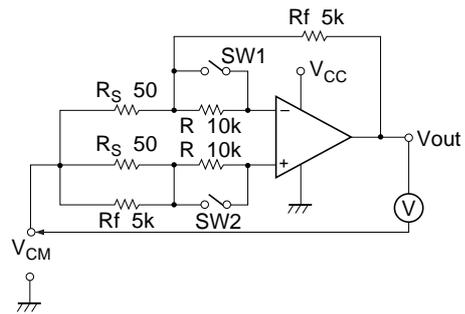1. Input offset voltage (V_{IO}), input offset current (I_{IO}), and Input bias current (I_{IB}) test circuit



SW1	SW2	V_O
On	On	V_{O1}
Off	Off	V_{O2}
On	Off	V_{O3}
Off	On	V_{O4}

$$V_{CM} = \frac{1}{2} V_{CC}$$


$$V_{IO} = \frac{V_{O1}}{1 + R_f / R_S} \quad (\text{mV})$$

$$I_{IO} = \frac{V_{O2} - V_{O1}}{R(1 + R_f / R_S)} \quad (\text{nA})$$


$$I_{IB} = \frac{|V_{O4} - V_{O3}|}{2 \cdot R(1 + R_f / R_S)} \quad (\text{nA})$$

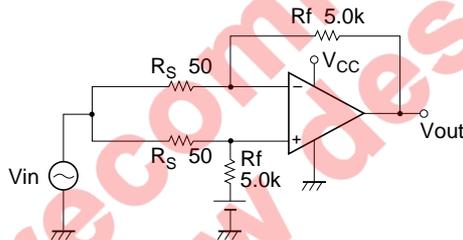2. Common-mode rejection ratio (CMR) test circuit


$$\text{CMR} = 20 \log \frac{V_{IN} \cdot R_f}{V_O \cdot R_S} \quad (\text{dB})$$



3. Supply current (I_{CC}) test circuit

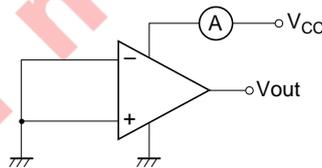

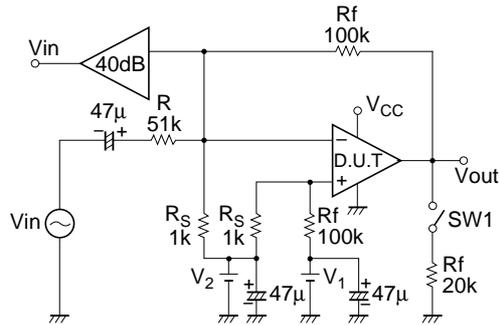
4. Voltage gain (A_{VD}), slew rate (SR), common-mode input voltage range (V_{CM}), and maximum output voltage amplitude (V_{OP-P}) test circuit.



- (1) A_{VD} : $R_S = 1k\Omega$, $R_f = 100k\Omega$, $R_L = \infty$, $V_1 = V_2 = 1/2 V_{CC}$

$$A_{VD} = 20 \log \frac{V_O}{V_{IN}} + 40 \quad (\text{dB})$$

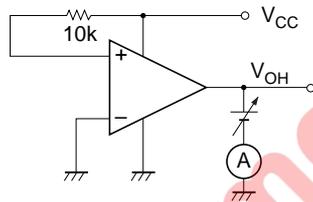- (2) SR: $f = 1.5kHz$, $R_L = \infty$, $V_1 = V_2 = 1/2 V_{CC}$



- (3) V_{CM} : $R_S = 1k\Omega$, $R_f = 100k\Omega$, $f = 100Hz$, $V_1 = 1/2 V_{CC}$, $R_L = \infty$, and the value of V_2 just slightly prior to the point where the output waveform changes.
 (4) V_{OP-P} : $R_S = 1k\Omega$, $R_f = 100k\Omega$, $R_L: 20k\Omega$, $f = 100Hz$, $V_{OP-P} = V_{OH} \leftrightarrow V_{OL} [V_{P-P}]$


5. Output source current (I_{source}) test circuit

$I_{o \text{ source}}$: $V_{OH} = 10V$













6. Output sink current (I_{sink}) test circuit

$I_{o \text{ sink}}$: $V_{OL} = 1V$

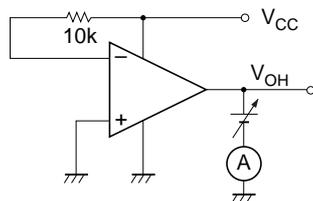

Characteristics Curve

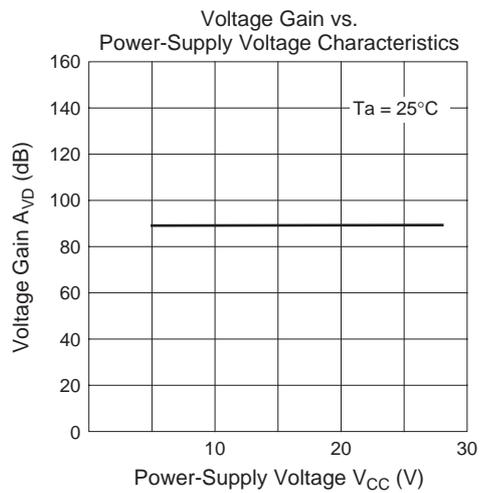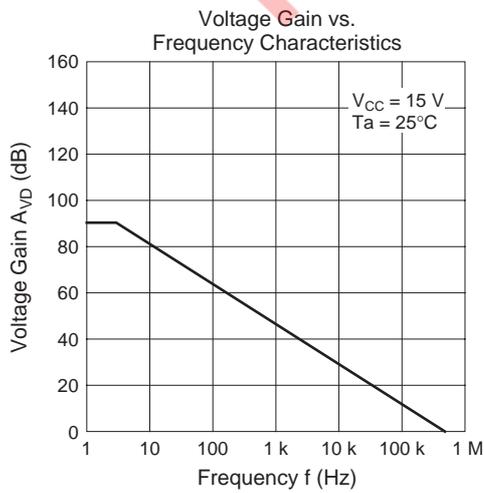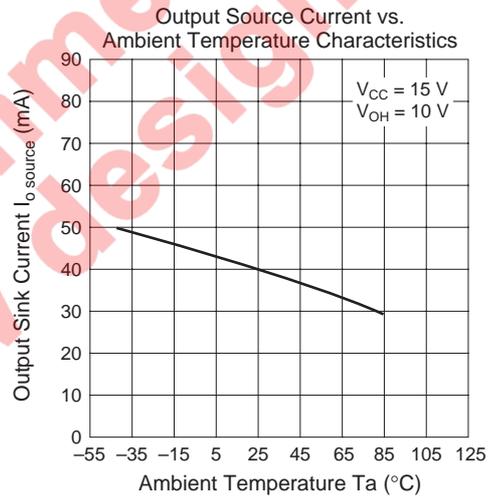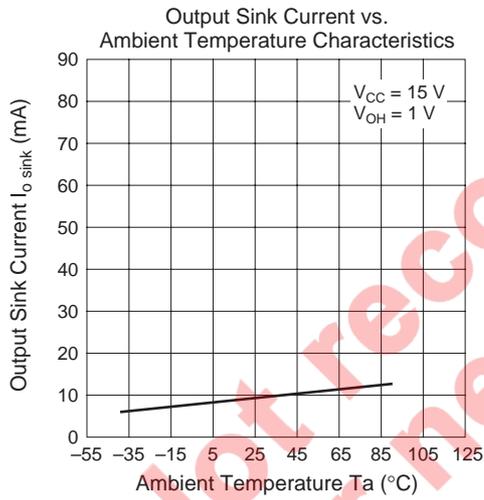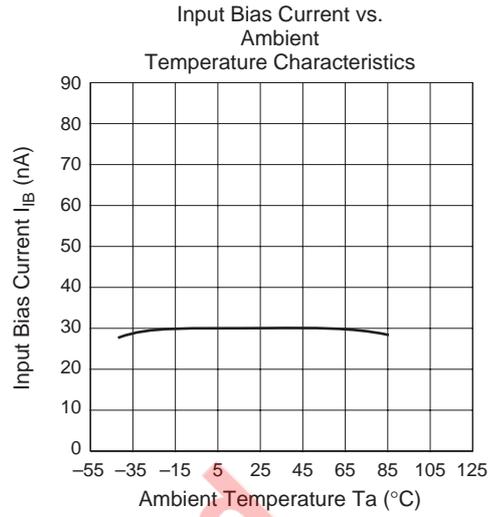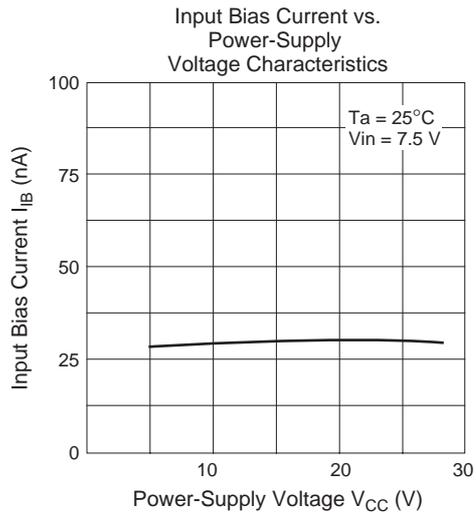

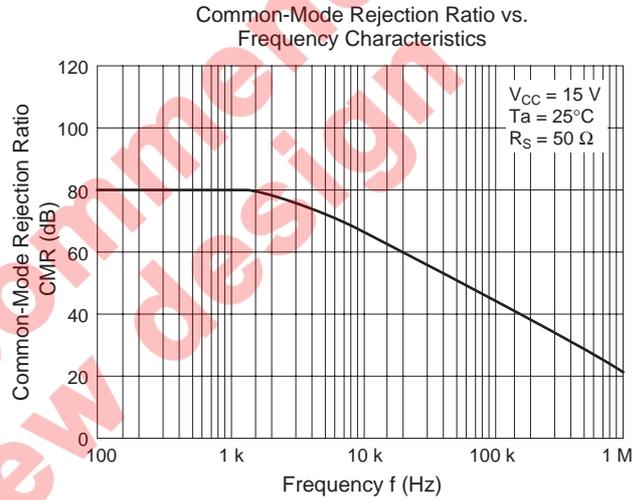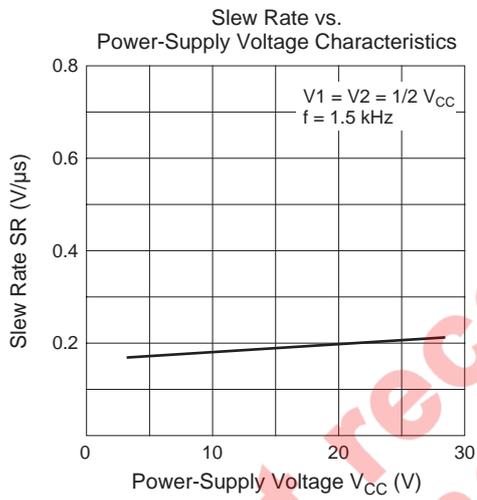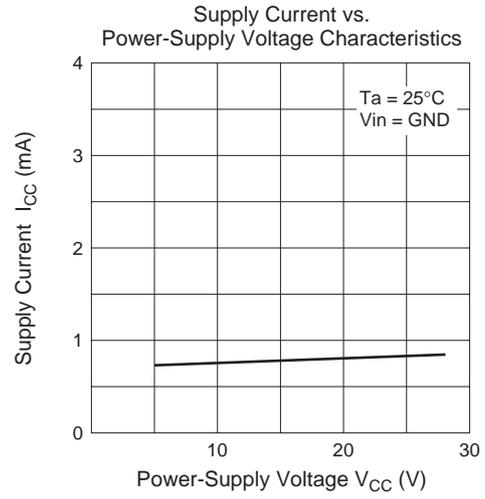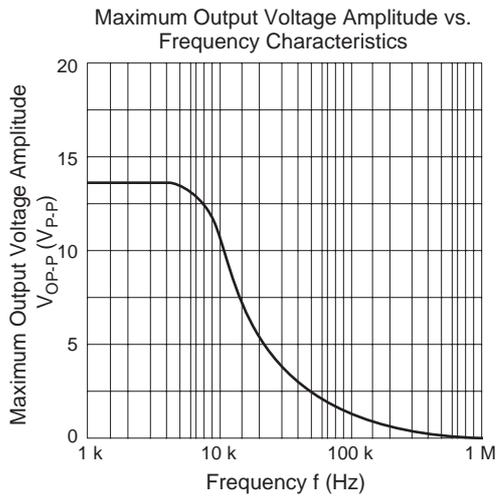

Not recommended for new design

HA17902 Application Examples

The HA17902 is a quad operational amplifier, and consists of four operational amplifier circuits and one bias current circuit. It features single-voltage power supply operation, internal phase compensation, a wide zero-cross bandwidth, a low input bias current, and a high open-loop gain. Thus the HA17902 can be used in a wide range of applications. This section describes several applications using the HA17902.

1. Noninverting Amplifier

Figure 1 shows the circuit diagram for a noninverting amplifier. The voltage gain of this amplifier is given by the following formula.

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$

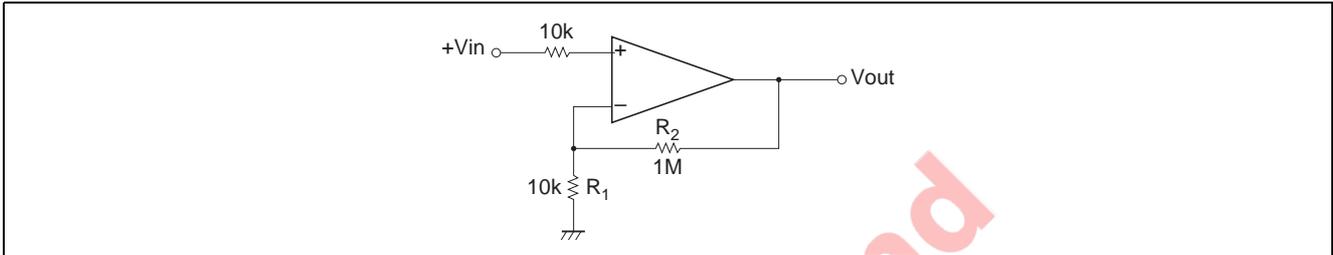


Figure 1 Noninverting Amplifier

2. Summing Amplifier

Since the circuit shown in figure 2 applies $+V_1$ and $+V_2$ to the noninverting input and $+V_3$ and $+V_4$ to the inverting input, the total output will be $V_{out} = V_1 + V_2 - V_3 - V_4$.

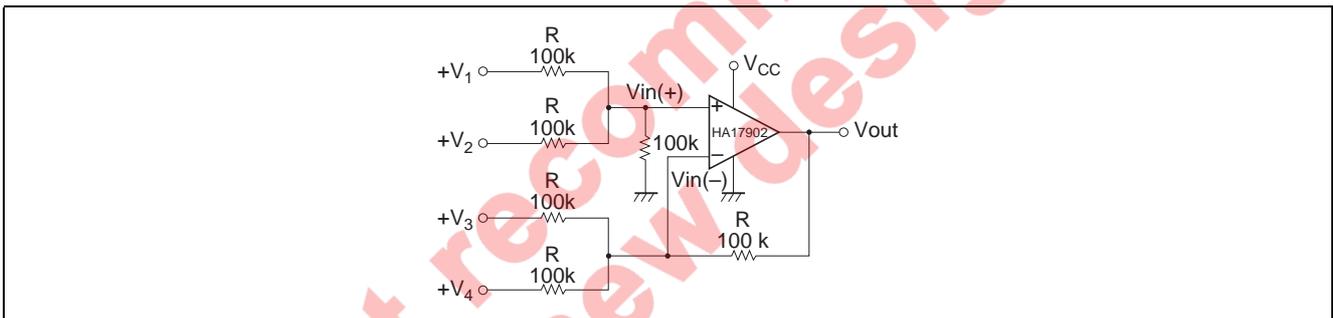


Figure 2 Summing Amplifier

3. High Input Impedance DC Differential Amplifier

The circuit shown in figure 3 is a high input impedance DC differential amplifier. This circuit's common-mode rejection ratio (CMR) depends on the matching between the R_1/R_2 and R_4/R_3 resistance ratios. This amplifier's output is given by the following formula.

$$V_{out} = \left(1 + \frac{R_4}{R_3}\right) (V_2 - V_1)$$

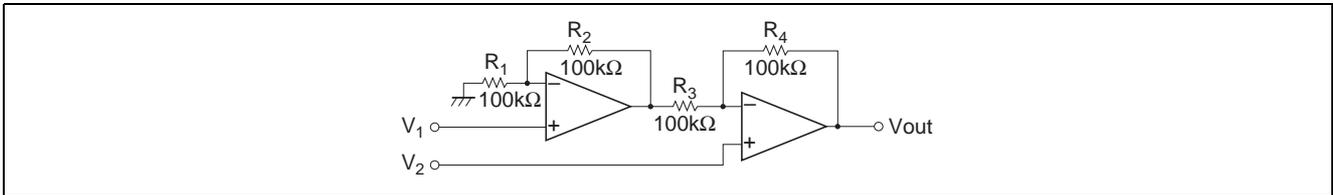


Figure 3 High Input Impedance DC Differential Amplifier

4. Voltage Controlled Oscillator

Figure 4 shows an oscillator circuit in which the amplifier A_1 is an integrator, the amplifier A_2 is a comparator, and transistor Q_1 operates as a switch that controls the oscillator frequency. If the output V_{out1} is at the low level, this will cut off transistor Q_1 and cause the A_1 inverting input to go to a higher potential than the noninverting input. Therefore, A_1 will integrate this negative input state and its output level will decrease. When the A_1 integrator output becomes lower than the A_2 comparator noninverting input level ($V_{CC}/2$) the comparator output goes high. This turns on transistor Q_1 causing the integrator to integrate a positive input state and for its output to increase. This operation generates a square wave on V_{out1} and a triangular wave on V_{out2} .


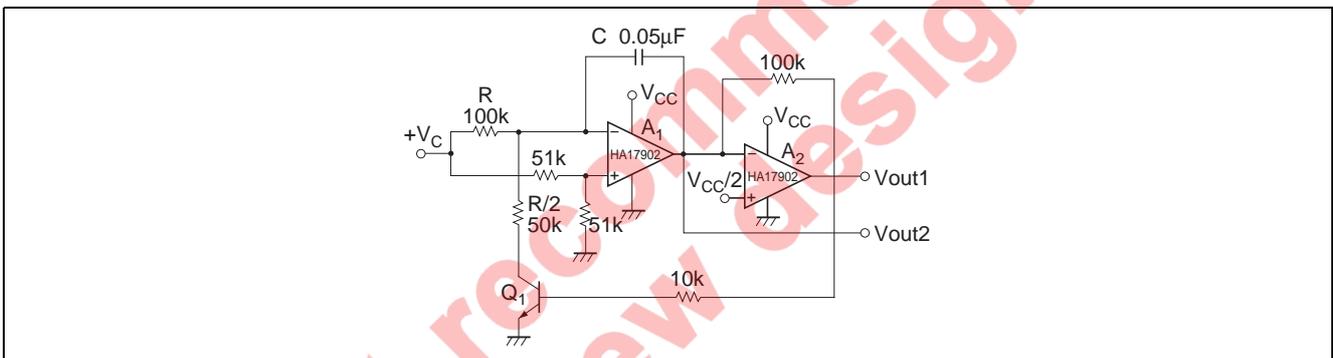
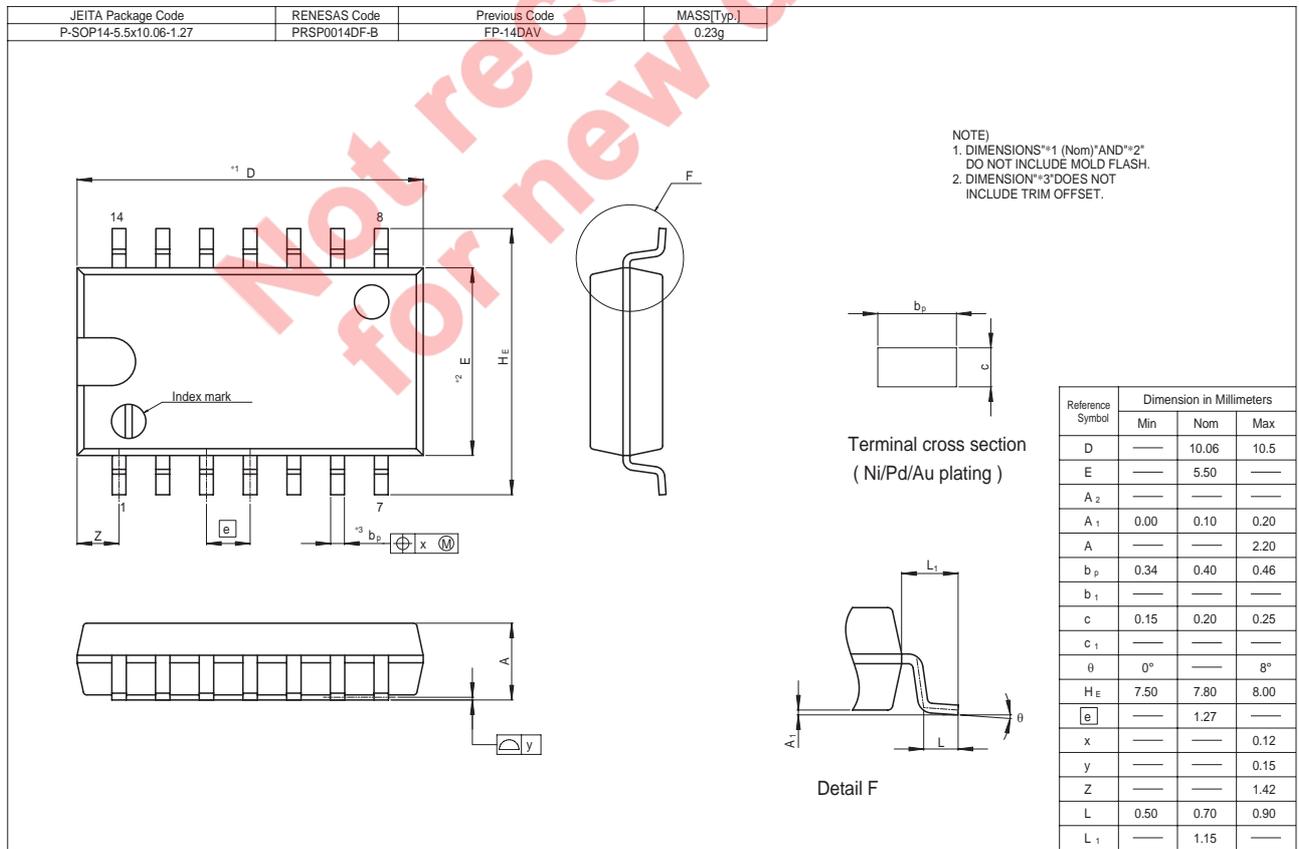


Figure 4 Voltage Controlled Oscillator

Package Dimensions

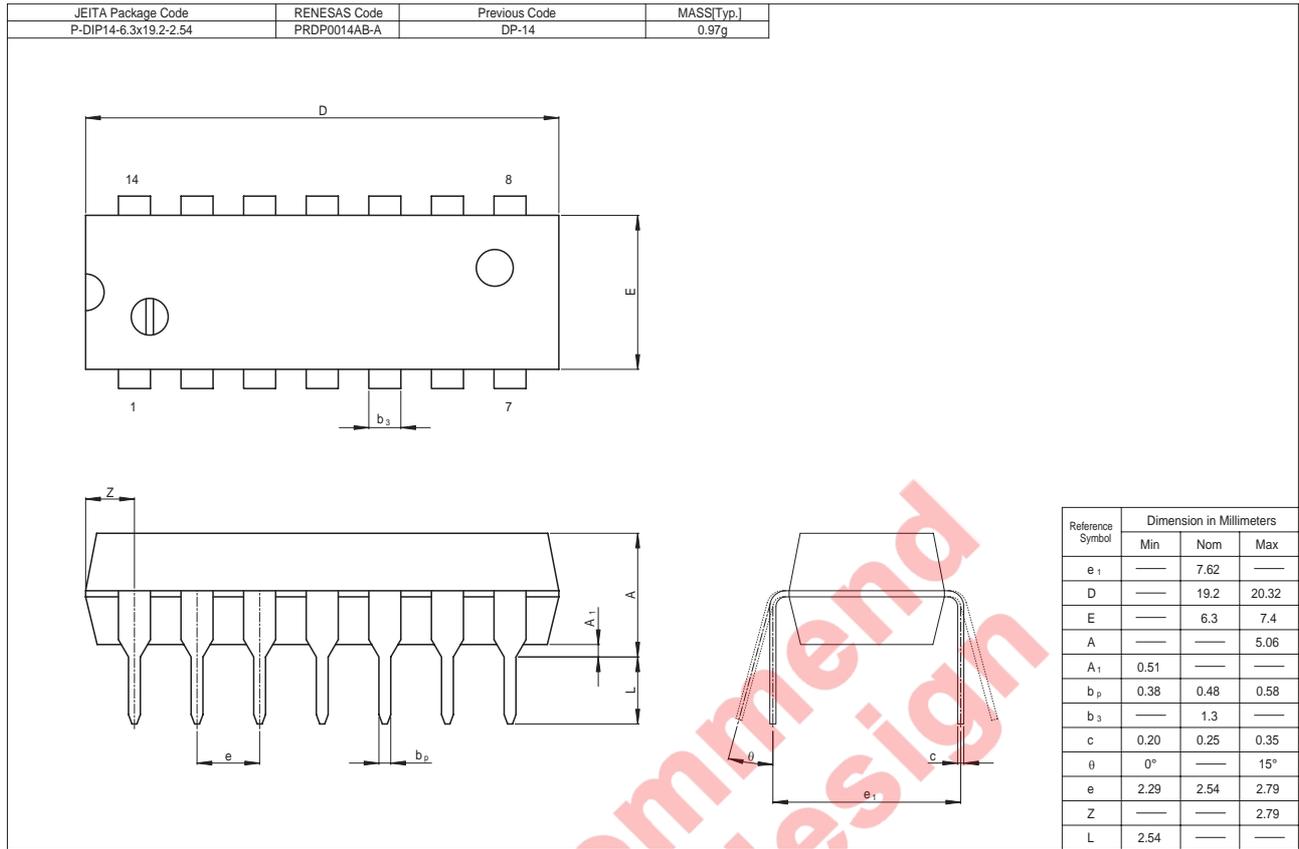

Renesas Technology Corp. Sales Strategic Planning Div. Nippon Bldg., 2-6-2, Ohte-machi, Chiyoda-ku, Tokyo 100-0004, Japan

Keep safety first in your circuit designs!

1. Renesas Technology Corp. puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage.
Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of nonflammable material or (iii) prevention against any malfunction or mishap.

Notes regarding these materials

1. These materials are intended as a reference to assist our customers in the selection of the Renesas Technology Corp. product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Renesas Technology Corp. or a third party.
2. Renesas Technology Corp. assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.
3. All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Renesas Technology Corp. without notice due to product improvements or other reasons. It is therefore recommended that customers contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor for the latest product information before purchasing a product listed herein.
The information described here may contain technical inaccuracies or typographical errors.
Renesas Technology Corp. assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors.
Please also pay attention to information published by Renesas Technology Corp. by various means, including the Renesas Technology Corp. Semiconductor home page (<http://www.renesas.com>).
4. When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Renesas Technology Corp. assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.
5. Renesas Technology Corp. semiconductors are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.
6. The prior written approval of Renesas Technology Corp. is necessary to reprint or reproduce in whole or in part these materials.
7. If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination.
Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
8. Please contact Renesas Technology Corp. for further details on these materials or the products contained therein.



RENESAS SALES OFFICES

<http://www.renesas.com>

Refer to "<http://www.renesas.com/en/network>" for the latest and detailed information.

Renesas Technology America, Inc.
450 Holger Way, San Jose, CA 95134-1368, U.S.A
Tel: <1> (408) 382-7500, Fax: <1> (408) 382-7501

Renesas Technology Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.
Tel: <44> (1628) 585-100, Fax: <44> (1628) 585-900

Renesas Technology Hong Kong Ltd.
7th Floor, North Tower, World Finance Centre, Harbour City, 1 Canton Road, Tsimshatsui, Kowloon, Hong Kong
Tel: <852> 2265-6688, Fax: <852> 2730-6071

Renesas Technology Taiwan Co., Ltd.
10th Floor, No.99, Fushing North Road, Taipei, Taiwan
Tel: <886> (2) 2715-2888, Fax: <886> (2) 2713-2999

Renesas Technology (Shanghai) Co., Ltd.
Unit2607 Ruijing Building, No.205 Maoming Road (S), Shanghai 200020, China
Tel: <86> (21) 6472-1001, Fax: <86> (21) 6415-2952

Renesas Technology Singapore Pte. Ltd.
1 Harbour Front Avenue, #06-10, Keppel Bay Tower, Singapore 098632
Tel: <65> 6213-0200, Fax: <65> 6278-8001