Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: http://www.renesas.com

April 1st, 2010 Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (http://www.renesas.com)

Send any inquiries to http://www.renesas.com/inquiry.



Notice

- 1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
- Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights
 of third parties by or arising from the use of Renesas Electronics products or technical information described in this document.
 No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights
 of Renesas Electronics or others.
- 3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
- 4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
- 5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
- 6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
- 7. Renesas Electronics products are classified according to the following three quality grades: "Standard", "High Quality", and "Specific". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as "Specific" without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as "Specific" or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is "Standard" unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - "Specific": Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
- 8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
- 9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
- 10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
- 11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics
- 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



HA17431VPJ/PJ/PAJ/FPJ/FPAJ/PNAJ/UPA, HA17432UPA

Shunt Regulator

REJ03D0892-0100 Rev.1.00 Apr 03, 2007


Description

The HA17431 series is temperature-compensated variable shunt regulators. The main application of these products is in voltage regulators that provide a variable output voltage. The on-chip high-precision reference voltage source can provide $\pm 1\%$ accuracy in the V versions, which have a V_{KA} max of 16 volts.


Features

- The V versions provide 2.500 V $\pm 1\%$ at Ta = 25°C
- The reference voltage has a low temperature coefficient
- The UPAKV miniature packages are optimal for use on high mounting density circuit boards

Block Diagram

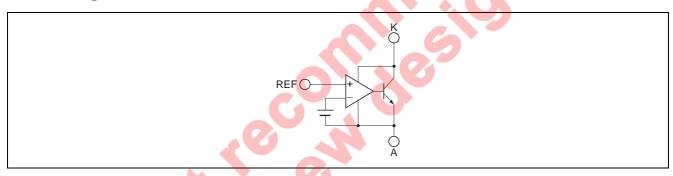


Application Circuit Example

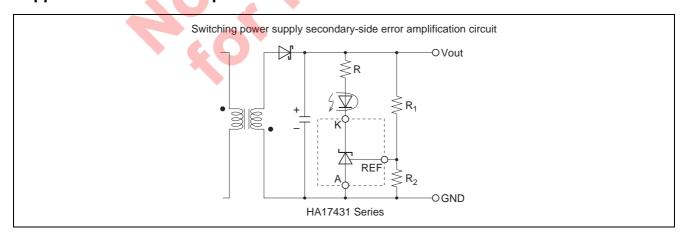

Ordering Information

		Refere	nce voltage (at 2			
ltem		Normal Version ±4% 2.395V to 2.495V to 2.595V	A Version ±2.2% 2.440V to 2.495V to 2.550V	V Version ±1% 2.475V to 2.500V to 2.525V	Package Code (Package Name)	Operating Temperature Range
	HA17431FPAJ		0		PRSP0008DE-B (FP-8DGV)	
	HA17431FPJ	0			PRSP0008DE-B (FP-8DGV)	
Car use	HA17431PAJ		0		PRSS0003DC-A (TO-92MODV)	-40 to +85°C
Cai use	HA17431PJ	0			PRSS0003DC-A (TO-92MODV)	-40 to +65 C
	HA17431PNAJ		0		PRSS0003DA-A (TO-92V)	
	HA17431VPJ			0	PRSS0003DA-A (TO-92V)	
Industrial	HA17431UPA		0		PLZZ0004CA-A (UPAKV)	-20 to +85°C
use	HA17432UPA		0		PLZZ0004CA-A (UPAKV)	-20 to +65 C

Pin Arrangement

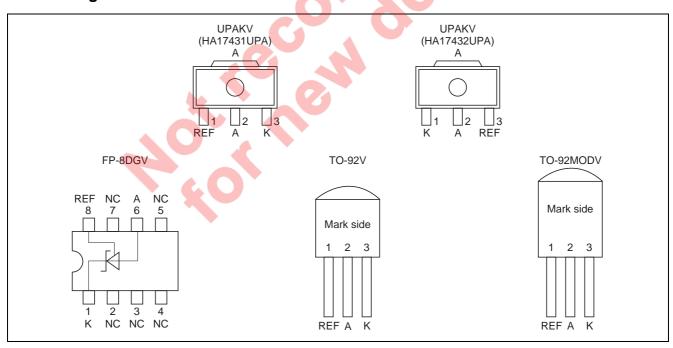

Absolute Maximum Ratings

 $(Ta = 25^{\circ}C)$

Item	Symbol	HA17431VPJ	HA17431UPA	HA17432UPA	Unit	Notes
Cathode voltage	V _{KA}	16	40	40	V	1
Continuous cathode current	I _K	-50 to +50	-100 to +150	-100 to +150	mA	
Reference input current	Iref	-0.05 to +10	-0.05 to +10	-0.05 to +10	mA	
Power dissipation	P _T	500 * ²	800 * ⁵	800 *5	mW	2, 5
Operating temperature range	Topr	-40 to +85	-20 to +85	-20 to +85	°C	
Storage temperature	Tstg	-55 to +150	-55 to +150	-55 to +150	°C	

		Ratings				
Item	Symbol	HA17431PNAJ	HA17431PJ/PAJ	HA17431FPJ/FPAJ	Unit	Notes
Cathode voltage	V _{KA}	40	40	40	V	1
Continuous cathode current	I _K	-100 to +150	-100 to +150	-100 to +150	mA	
Reference input current	Iref	-0.05 to +10	-0.05 to +10	-0.05 to +10	mA	
Power dissipation	P _T	500 * ²	800 * ³	500 * ⁴	mW	2, 3, 4
Operating temperature range	Topr	-40 to +85	-40 to +85	-40 to +85	°C	
Storage temperature	Tstg	-55 to +150	-55 to +150	-55 to +125	°C	

Notes: 1. Voltages are referenced to anode.

- 2. Ta \leq 25°C. If Ta > 25°C, derate by 4.0 mW/°C.
- 3. Ta \leq 25°C. If Ta > 25°C, derate by 6.4 mW/°C.
- 4. 50 mm \times 50 mm \times 1.5mmt glass epoxy board (5% wiring density), Ta \leq 25°C. If Ta > 25°C, derate by 5 mW/°C.
- 5. 15 mm \times 25 mm \times 0.7mmt alumina ceramic board, Ta \leq 25°C. If Ta > 25°C, derate by 6.4 mW/°C.

Electrical Characteristics

HA17431VPJ

 $(Ta = 25^{\circ}C, I_K = 10 \text{ mA})$


Item	Symbol	Min	Тур	Max	Unit	Test Conditions	Notes
Reference voltage	Vref	2.475	2.500	2.525	V	V _{KA} = Vref	
Reference voltage	Vref(dev)	_	10	_	mV	V _{KA} = Vref,	1
temperature deviation						Ta = -20 °C to $+85$ °C	
Reference voltage	∆Vref/∆Ta	_	±30		ppm/°C	V _{KA} = Vref,	
temperature coefficient						0°C to 50°C gradient	
Reference voltage regulation	$\Delta Vref/\Delta V_{KA}$		2.0	3.7	mV/V	V _{KA} = Vref to 16 V	
Reference input current	Iref	_	2	6	μΑ	$R_1 = 10 \text{ k}\Omega, R_2 = \infty$	
Reference current	Iref(dev)	_	0.5	_	μΑ	$R_1 = 10 \text{ k}\Omega, R_2 = \infty,$	
temperature						Ta = -20 °C to $+85$ °C	
deviation							
Minimum cathode current	Imin	_	0.4	1.0	mA	V _{KA} = Vref	2
Off state cathode current	loff	_	0.001	1.0	μΑ	V _{KA} = 16 V, Vref = 0 V	
Dynamic impedance	ZKA	_	0.2	0.5	Ω	V _{KA} = Vref,	
						$I_K = 1 \text{ mA to } 50 \text{ mA}$	

HA17431PJ/PAJ/FPJ/FPAJ/PNAJ/UPA, HA17432UPA

 $(Ta = 25^{\circ}C, I_K = 10 \text{ mA})$

					*		(14 25 C, 1 _K	10 1111 1)
Item	Symbol	Min	Тур	Max	Unit	Tes	t Conditions	Notes
Reference voltage	Vref	2.440	2.495	2.550	V	V_{KA} = Vref	V _{KA} = Vref	
		2.395	2.495	2.595				Normal
Reference voltage	Vref(dev)	-(11	(30)	mV	V _{KA} = Vref	Ta =	1, 3, 4
temperature deviation							–20°C to +85°C	
		(4)	5	(17)			Ta = 0°C to +70°C	1, 3, 5
Reference voltage	ΔVref/ΔV _{KA}		1.4	3.7	mV/V	V _{KA} = Vref t	o 10 V	
regulation		_	1	2.2		V _{KA} = 10 V	to 40 V	
Reference input current	Iref	_	3.8	6	μА	$R_1 = 10 \text{ k}\Omega$	$R_2 = \infty$	
Reference current	Iref(dev)	_	0.5	(2.5)	μΑ	$R_1 = 10 \text{ k}\Omega$	$R_2 = \infty$	3
temperature deviation						Ta = 0°C to	+70°C	
Minimum cathode current	Imin		0.4	1.0	mA	V _{KA} = Vref		2
Off state cathode current	loff) —	0.001	1.0	μА	V _{KA} = 40 V,	Vref = 0 V	
Dynamic impedance	ZKA	_	0.2	0.5	Ω	V _{KA} = Vref,		
						$I_K = 1 \text{ mA to}$	100 mA	

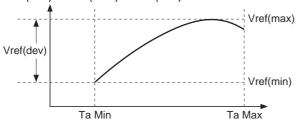
Notes: 1. Vref(dev) = Vref(max) - Vref(min)



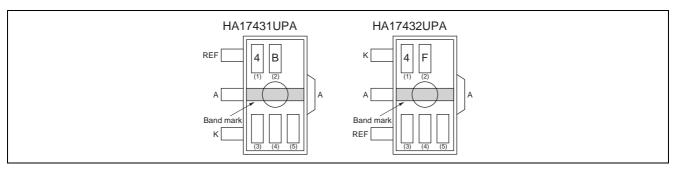- 2. Imin is given by the cathode current at $Vref = Vref_{(IK=10mA)} 15 \text{ mV}$.
- 3. The maximum value is a design value (not measured).
- 4. HA17431PJ/PAJ/FPJ/FPAJ/PNAJ
- 5. HA17431UPA, HA17432UPA

UPAKV Marking Patterns

The marking patterns shown below are used on UPAKV products. Note that the product code and mark pattern are different. The pattern is laser-printed.



Notes: 1. Boxes (1) to (5) in the figures show the position of the letters or numerals, and are not actually marked on the package.

2. The letters (1) and (2) show the product specific mark pattern.

Product	(1)	(2)
HA17431UPA	4	В
HA17432UPA	4	F


- 3. The letter (3) shows the production year code (the last digit of the year).
- 4. The letter (4) shows the production month code (see table below).


Production month	Jan.	Feb.	Mar.	Apr.	May.	Jun.	Jul.	Aug.	Sep.	Oct.	Nov.	Dec.
Marked code	Α	В	С	D	ш	E	G	Ŧ	J	K	L	М

5. The letter (5) shows manufacturing code.


Characteristics Curves


HA17431VPJ

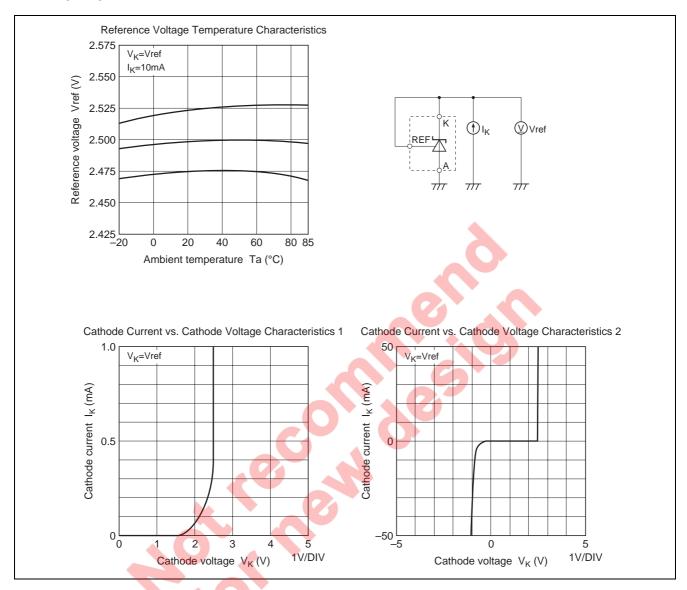


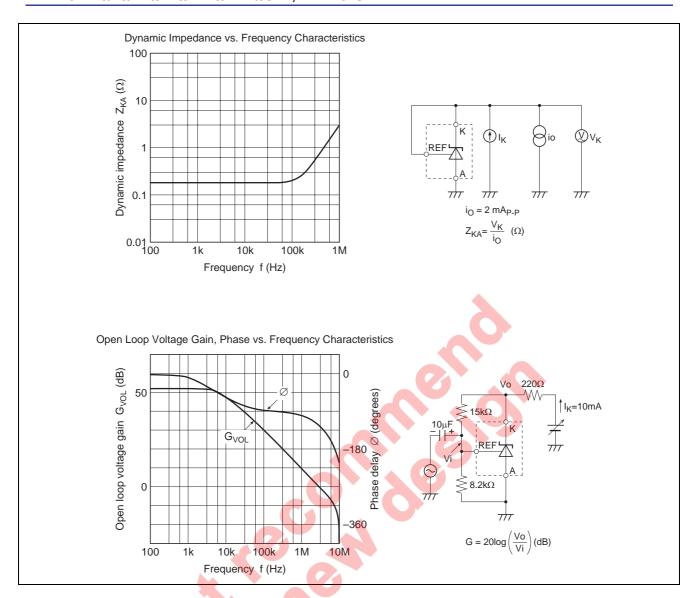

HA17431PJ/PAJ/FPAJ/PNAJ/UPA, HA17432UPA

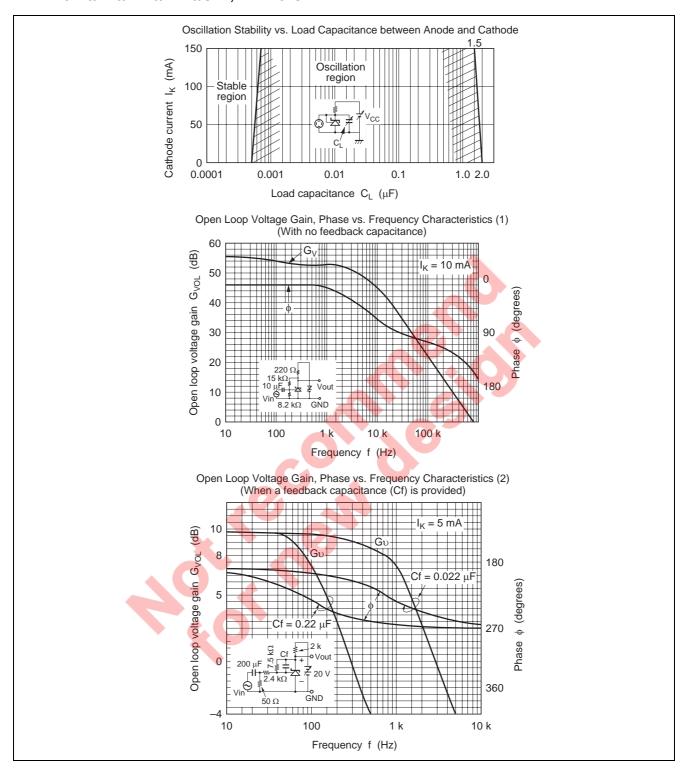

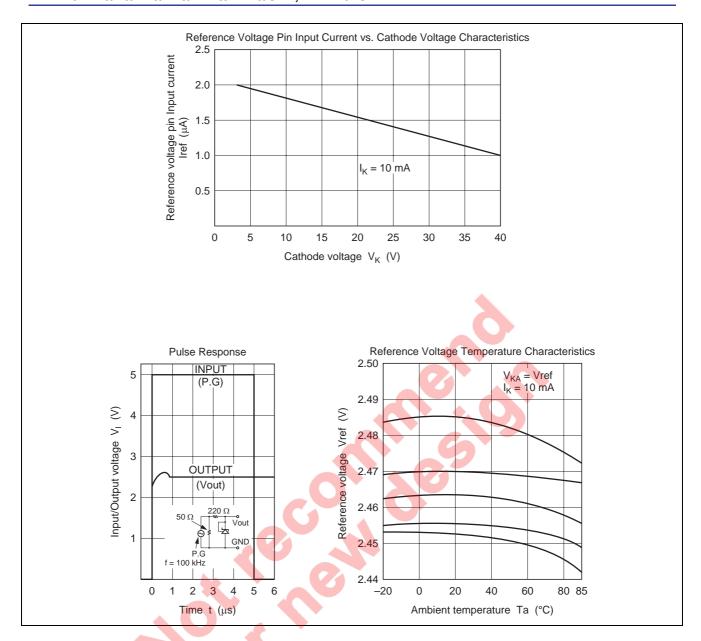

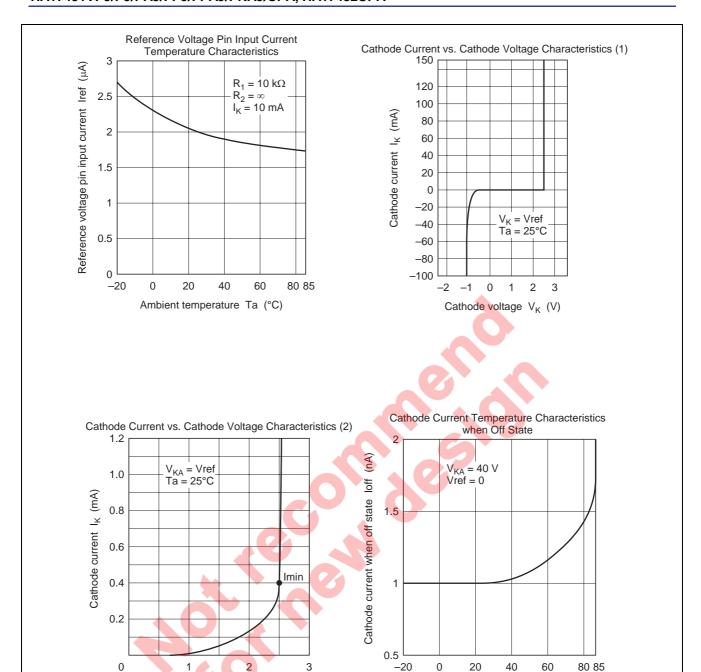

Cathode voltage V_K (V)

Ambient temperature Ta (°C)

Application Examples

As shown in the figure on the right, this IC operates as an inverting amplifier, with the REF pin as input pin. The open-loop voltage gain is given by the reciprocal of "reference voltage deviation by cathode voltage change" in the electrical specifications, and is approximately 50 to 60 dB. The REF pin has a high input impedance, with an input current Iref of 3.8 μ A Typ (V version: Iref = 2 μ A Typ). The output impedance of the output pin K (cathode) is defined as dynamic impedance Z_{KA} , and Z_{KA} is low (0.2 Ω) over a wide cathode current range. A (anode) is used at the minimum potential, such as ground.

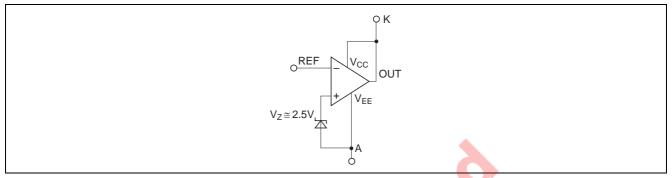


Figure 1 Operation Diagram

Application Hints

No.	Application Example	Description
1	Reference voltage generation circuit Vin O Vout REF A CL GND O GND	This is the simplest reference voltage circuit. The value of the resistance R is set so that cathode current $I_K \geq 1$ mA. Output is fixed at Vout $\cong 2.5$ V. The external capacitor C_L ($C_L \geq 3.3~\mu F)$ is used to prevent oscillation in normal applications.
2	Variable output shunt regulator circuit VinO R R R R R REF A CL R GNDO OGND	This is circuit 1 above with variable output provided. Here, Vout $\cong 2.5 \text{ V} \times \frac{(R_1+R_2)}{R_2}$ Since the reference input current Iref = 3.8 μ A Typ (V version: Iref = 2 μ A Typ) flows through R ₁ , resistance values are chosen to allow the resultant voltage drop to be ignored.

Application Hints (cont.)

	cation mits (cont.)	
No.	Application Example	Description
3	Single power supply inverting comparator circuit OVCC RL VINO VINO REF A GND OGND	This is an inverting type comparator with an input threshold voltage of approximately 2.5 V. Rin is the REF pin protection resistance, with a value of several $k\Omega$ to several tens of $k\Omega$. $R_{L} \text{ is the load resistance, selected so that the cathode current } I_{K} \geq 1 \\ \text{mA when Vout is low.} \\ \hline \frac{\text{Condition Vin}}{\text{C1}} \frac{\text{Vout}}{\text{C2}} \frac{\text{IC}}{\text{C3}} \\ \hline \frac{\text{C1}}{\text{C2}} 2.5 \text{ V or more} \text{Approx. 2 V (V_{OL})} \text{ON} \\ \hline \\ $
4	AC amplifier circuit $ \begin{array}{c c} Cf & & & & & & \\ \hline & & & & & \\ \hline & & & & &$	This is an AC amplifier with voltage gain $G = -R_1 / (R_2//R_3)$. The input is cut by capacitance Cin, so that the REF pin is driven by the AC input signal, centered on 2.5 V_{DC} . R_2 also functions as a resistance that determines the DC cathode potential when there is no input, but if the input level is low and there is no risk of Vout clipping to V_{CC} , this can be omitted. To change the frequency characteristic, Cf should be connected as indicated by the dotted line.
5	Switching power supply error amplification circuit Secondary side GND Note: LED: Light emitting diode in photocoupler R3: Bypass resistor to feed IK(>Imin) when LED current vanishes R4: LED protection resistance	This circuit performs control on the secondary side of a transformer, and is often used with a switching power supply that employs a photocoupler for offlining. The output voltage (between V+ and V-) is given by the following formula: $Vout \cong 2.5 \ V \times \frac{(R_1+R_2)}{R_2}$ In this circuit, the gain with respect to the Vout error is as follows: $G = \frac{R_2}{(R_1+R_2)} \times \begin{bmatrix} HA17431 \ open \\ loop\ gain \end{bmatrix} \times \begin{bmatrix} photocoupler \\ total\ gain \end{bmatrix}$ As stated earlier, the HA17431 open-loop gain is 50 to 60 dB.

Application Hints (cont.)

No.	Application Example	Description
6 7	Constant voltage regulator circuit VCC OR1 R1 Q Vout R2 GND OGND Discharge type constant current circuit	This is a 3-pin regulator with a discrete configuration, in which the output voltage $Vout = 2.5 \ V \times \frac{(R_2 + R_3)}{R_3}$ R ₁ is a bias resistance for supplying the HA17431 cathode current and the output transistor Q base current.
	V _{CC} R Q Q Q Q Q Q Q Q Q Q Q Q Q Q Q Q Q Q	Inis circuit supplies a constant current of $I_L\cong \frac{2.5\ V}{R_S}$ [A] into the load. Caution is required since the HA17431 cathode current is also superimposed on I_L . The requirement in this circuit is that the cathode current must be greater than Imin = 1 mA. The I_L setting therefore must be on the order of several mA or more.
8	Induction type constant current circuit VCC R Q Q Q Q Q Q Q Q Q Q Q Q	In this circuit, the load is connected on the collector side of transistor Q in circuit 7 above. In this case, the load floats from GND, but the HA17431 cathode current is not superimposed on I _L , so that I _L can be kept small (1 mA or less is possible). The constant current value is the same as for circuit 7 above: $I_L \cong \frac{2.5 \text{ V}}{\text{R}_S} [\text{A}]$

Design Guide for AC-DC SMPS (Switching Mode Power Supply)

1. Use of Shunt Regulator in Transformer Secondary Side Control

This example is applicable to both forward transformers and flyback transformers. A shunt regulator is used on the secondary side as an error amplifier, and feedback to the primary side is provided via a photocoupler.

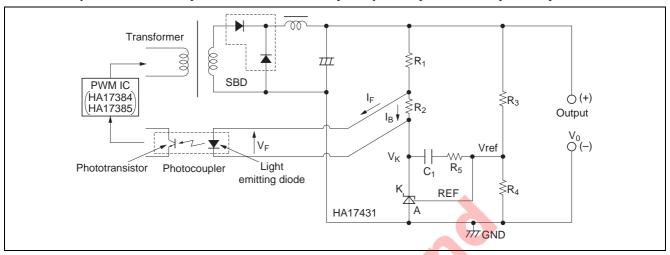


Figure 2 Typical Shunt Regulator/Error Amplifier

- 2. Determination of External Constants for the Shunt Regulator
 - A. DC characteristic determination

In figure 2, R_1 and R_2 are protection resistor for the light emitting diode in the photocoupler, and R_2 is a bypass resistor to feed I_K minimum, and these are determined as shown below. The photocoupler specification should be obtained separately from the manufacturer. Using the parameters in figure 2, the following formulas are obtained:

$$R_1 = \frac{V_0 - V_F - V_K}{I_F + I_B}$$
 , $R_2 = \frac{V_F}{I_B}$

 V_K is the HA17431 operating voltage, and is set at around 3 V, taking into account a margin for fluctuation. R_2 is the current shunt resistance for the light emitting diode, in which a bias current I_B of around 1/5 I_F flows. Next, the output voltage can be determined by R3 and R4, and the following formula is obtained:

$$V_0 = \frac{R_3 + R_4}{R_4} \times Vref, Vref = 2.5 V Typ$$

The absolute values of R_3 and R_4 are determined by the HA17431 reference input current Iref and the AC characteristics described in the next section. The Iref value is around 3.8 μ A Typ. (V version: 2 μ A Typ)

B. AC characteristic determination

This refers to the determination of the gain frequency characteristic of the shunt regulator as an error amplifier. Taking the configuration in figure 2, the error amplifier characteristic is as shown in figure 3.

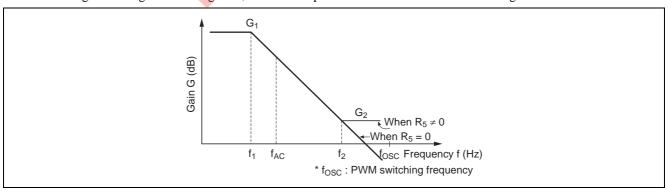


Figure 3 HA17431 Error Amplification Characteristic

HA17431VPJ/PJ/PAJ/FPJ/FPAJ/PNAJ/UPA, HA17432UPA

In Figure 3, the following formulas are obtained:

Gain

 $G_1 = G_0 \approx 50$ dB to 60 dB (determined by shunt regulator)

$$G_2 = \frac{R_5}{R_3}$$

Corner frequencies

$$f_1 = 1/(2\pi C_1 G_0 R_3)$$

$$f_2 = 1/(2\pi C_1 R_5)$$

 G_0 is the shunt regulator open-loop gain; this is given by the reciprocal of the reference voltage fluctuation $\Delta V ref/\Delta V_{KA}$, and is approximately 50 dB.

3. Practical Example

Consider the example of a photocoupler, with an internal light emitting diode $V_F = 1.05$ V and $I_F = 2.5$ mA, power supply output voltage $V_2 = 5$ V, and bias resistance R_2 current of approximately 1/5 I_F at 0.5 mA. If the shunt regulator $V_K = 3$ V, the following values are found.

$$R_1 = \frac{5V - 1.05V - 3V}{2.5 \text{mA} + 0.5 \text{mA}} = 316(\Omega) \ (330\Omega \ \text{from E24 series})$$

$$R_2 = \frac{1.05 \text{V}}{0.5 \text{mA}} = 2.1 (\text{k}\Omega) (2.2 \text{k}\Omega \text{ from E24 series})$$

Next, assume that $R_3 = R_4 = 10 \text{ k}\Omega$. This gives a 5 V output. If $R_5 = 3.3 \text{ k}\Omega$ and $C_1 = 0.022 \mu\text{F}$, the following values are found.


$$G_2 = 3.3 \text{ k}\Omega / 10 \text{ k}\Omega = 0.33 \text{ times (-10 dB)}$$


$$f_1 = 1 / (2 \times \pi \times 0.022 \,\mu\text{F} \times 316 \times 10 \,\text{k}\Omega) = 2.3 \,\text{(Hz)}$$


$$f_2 = 1 / (2 \times \pi \times 0.022 \,\mu\text{F} \times 3.3 \,\text{k}\Omega) = 2.2 \,\text{(kHz)}$$




Package Dimensions

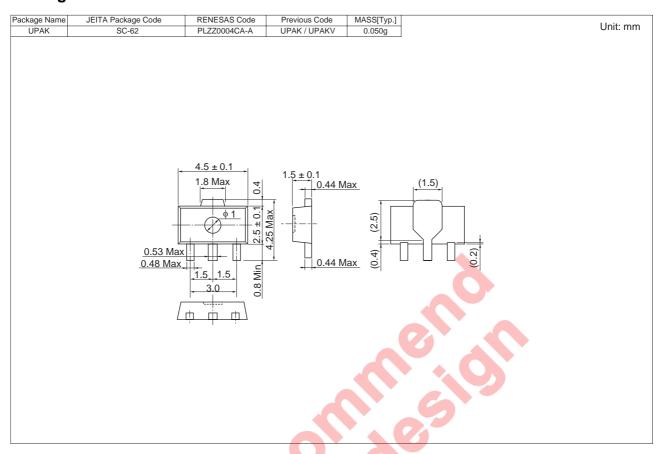

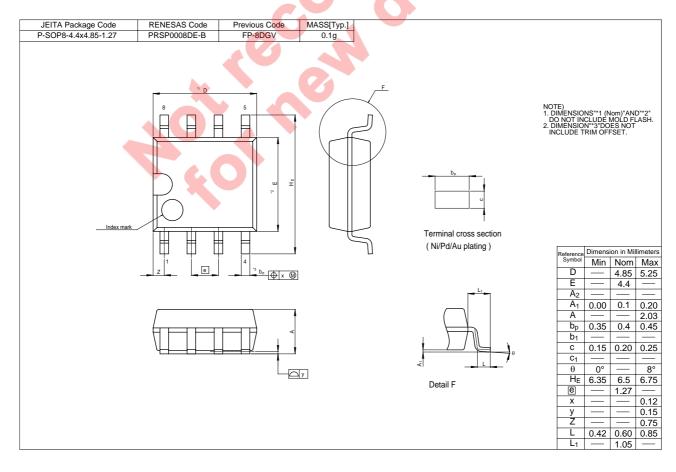

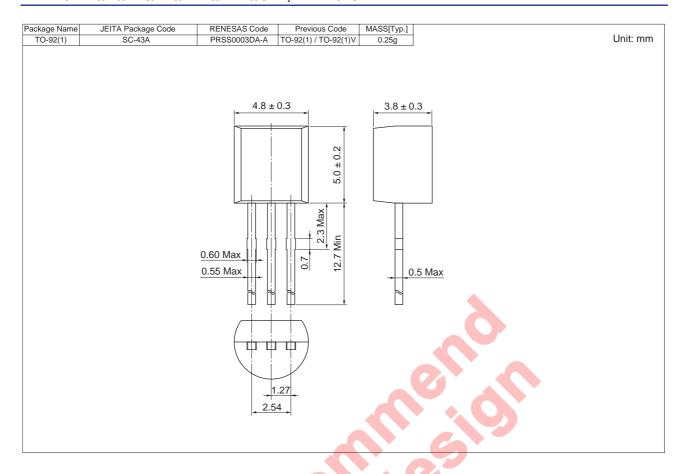

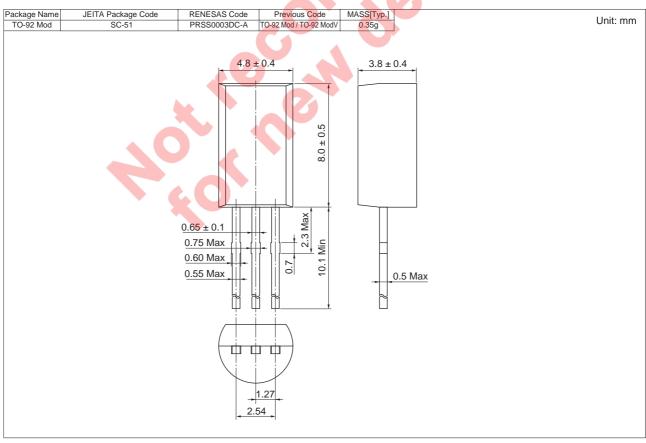

Renesas Technology Corp. Sales Strategic Planning Div. Nippon Bldg., 2-6-2, Ohte-machi, Chiyoda-ku, Tokyo 100-0004, Japan

- Renesas Technology Corp. Sales Strategic Planning Div. Nippon Bldg., 2-6-2, Ohte-machi, Chiyoda-ku, Tokyo 100-0004, Japan

 Notes:

 1. This document is provided for reference purposes only so that Renesas customers may select the appropriate Renesas products for their use. Renesas neither makes warranties or representations with respect to the accuracy or completeness of the information in this document nor grants any license to any intellectual property rights or any other rights of Renesas or any third party with respect to the information in this document.

 2. Renesas shall have no liability for damages or infringement of any intellectual property or other rights arising out of the use of any information in this document, but not timited to, product data, diagrams, charts, programs, algorithms, and application circuit examples.

 3. You should not use the products or the technology described in this document for the purpose of military applications such as the development of weapons of mass and regulations, and procedures required by such laws and regulations and procedures required by such laws and regulations, and procedures required by such laws and regulations.

 4. All information included in this document such as product data, diagrams, charts, programs, algorithms, and application and different information to the disclosed by Renesas such as that disclosed through our website, (http://www.renesas.com/) and continued to a such as the disclosed by Renesas such as that disclosed through our website, (http://www.renesas.com/) and continued the product of the produ



RENESAS SALES OFFICES

http://www.renesas.com

Refer to "http://www.renesas.com/en/network" for the latest and detailed information.

Renesas Technology America, Inc. 450 Holger Way, San Jose, CA 95134-1368, U.S.A Tel: <1> (408) 382-7500, Fax: <1> (408) 382-7501

Renesas Technology Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.
Tel: <44> (1628) 585-100, Fax: <44> (1628) 585-900

Renesas Technology (Shanghai) Co., Ltd.

Unit 204, 205, AZIACenter, No.1233 Lujiazui Ring Rd, Pudong District, Shanghai, China 200120 Tel: <86> (21) 5877-1818, Fax: <86> (21) 6887-7898

Renesas Technology Hong Kong Ltd.
7th Floor, North Tower, World Finance Centre, Harbour City, 1 Canton Road, Tsimshatsui, Kowloon, Hong Kong Tel: <852> 2265-6688, Fax: <852> 2730-6071

Renesas Technology Taiwan Co., Ltd. 10th Floor, No.99, Fushing North Road, Taipei, Taiwan Tel: <886> (2) 2715-2888, Fax: <886> (2) 2713-2999

Renesas Technology Singapore Pte. Ltd.
1 Harbour Front Avenue, #06-10, Keppel Bay Tower, Singapore 098632 Tel: <65> 6213-0200, Fax: <65> 6278-8001

Renesas Technology Korea Co., Ltd. Kukje Center Bldg. 18th Fl., 191, 2-ka, Hangang-ro, Yongsan-ku, Seoul 140-702, Korea Tel: <82> (2) 796-3115, Fax: <82> (2) 796-2145

Renesas Technology Malaysia Sdn. Bhd
Unit 906, Block B, Menara Amcorp, Amcorp Trade Centre, No.18, Jalan Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia Tel: <603> 7955-9390, Fax: <603> 7955-9510

-				
-				
-				
-				
-				
-				
-				
-				
-				
-				
-				